

$$i_{out} = \pm v_{iD} \cdot \sqrt{I_T \left(\frac{W}{L}\right) K_P - \frac{1}{4} \left(\frac{W}{L} K_P\right) v_{iD}^2}$$

$$\Rightarrow \frac{i_{out}}{I_T} = -v_{iD} \left(\frac{W}{L} \frac{K_P}{I_T}\right)^{1/2} \sqrt{1 - \frac{1}{4} \left(\left(\frac{W}{L} \frac{K_P}{I_T}\right)^{1/2} v_{iD}\right)^2} ; \quad x = \left(\frac{W}{L} \frac{K_P}{I_T}\right)^{1/2} v_{iD}$$


$$i = -x \sqrt{1 - \frac{1}{4} x^2}$$

$$i = i_{out}/I_T$$


what x gives $i = 1$; $\frac{1}{-x} = \sqrt{1 - (x/2)^2} \Rightarrow \frac{1}{x^2} = 1 - \left(\frac{x^2}{4}\right)$

$$1 - x^2 + \frac{(x^2)^2}{4} = 0 \Rightarrow z = x^2 \Rightarrow z^2 - 4z + 4 = 0$$


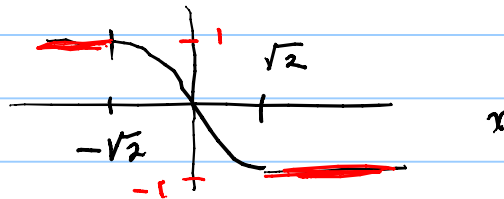
$$z = \frac{4}{2} \pm \frac{1}{2} \sqrt{16 - 4 \times 4} = 2, \quad x = \pm \sqrt{2}$$




differential pair with BJT

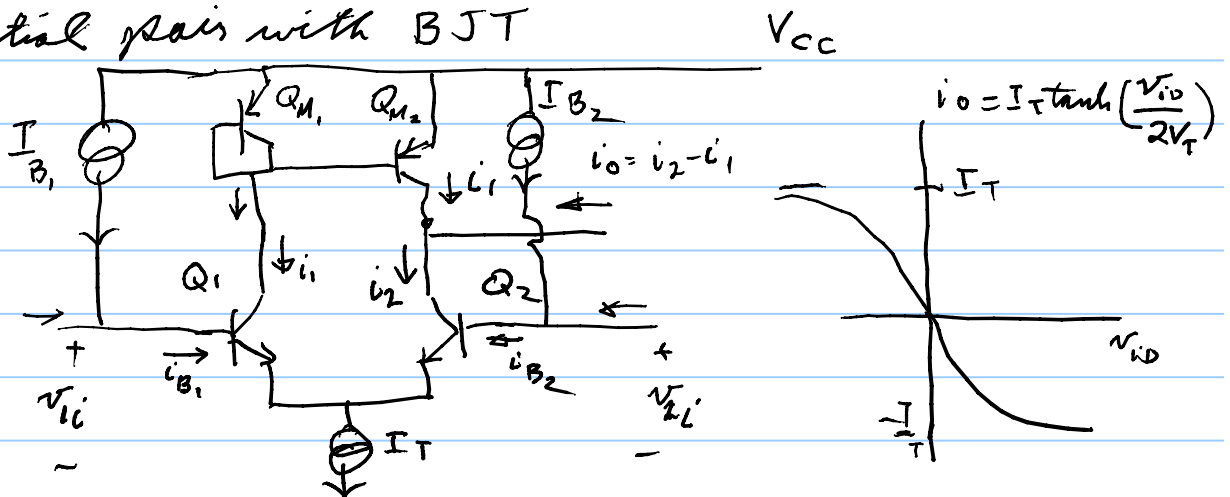

To make I_T

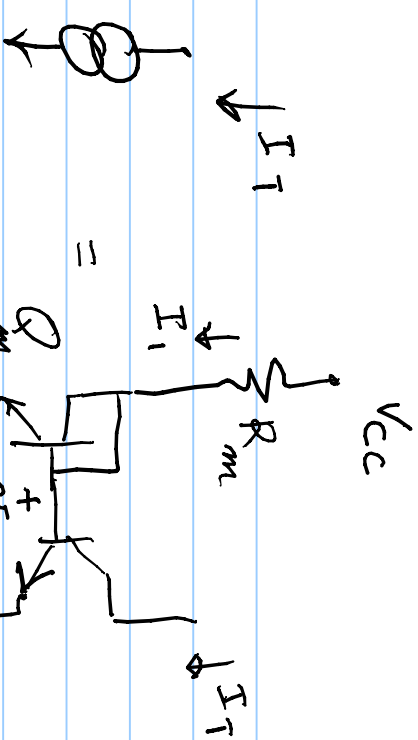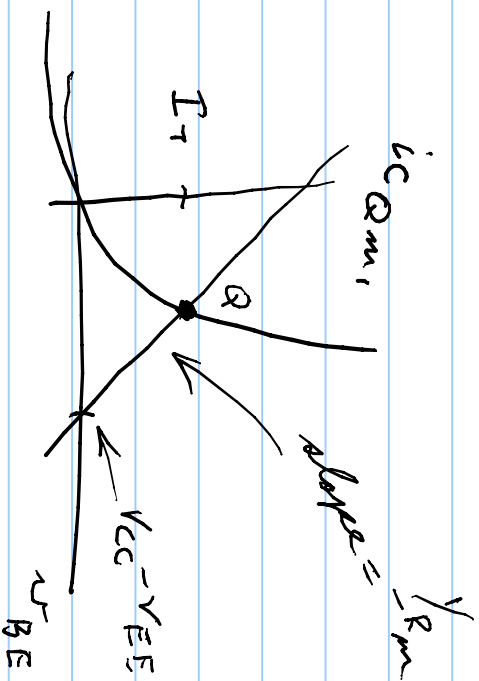

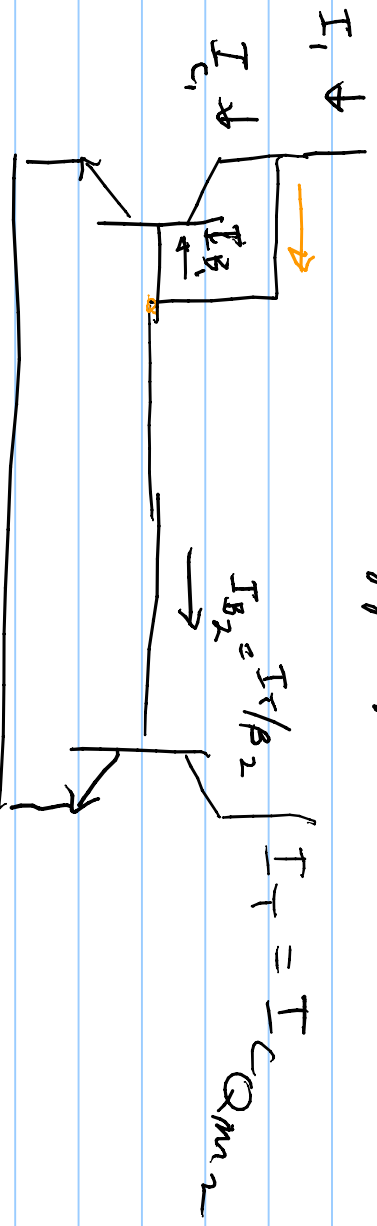ignored base current bigger picture more base current



$$\begin{aligned}
 \text{KCL: } I_1 &= I_{C_1} + (I_{B_1} + I_{B_2}) = I_{C_1} + \frac{I_{C_1}}{\beta_1} + \frac{I_T}{\beta_2} \\
 &= \left(\frac{\beta_1 + 1}{\beta_1} \right) I_{C_1} + \frac{I_T}{\beta_2}
 \end{aligned}$$

By the same voltage, V_{BE} , on both transistors $I_{C_1} = I_T$ if the transistors are equal.

$$\begin{aligned}
 \therefore I_1 &= \left(\frac{\beta_1 + 1}{\beta_1} + \frac{1}{\beta_2} \right) I_T = \left(\frac{1}{\alpha_1} + \frac{1 - \alpha_2}{\alpha_2} \right) I_T = \left(\frac{\alpha_1 + \alpha_2 - \alpha_1 \alpha_2}{\alpha_1 \alpha_2} \right) I_T \\
 &= \left(\frac{2}{\alpha} - 1 \right) I_T \text{ if } \alpha_1 = \alpha_2
 \end{aligned}$$