

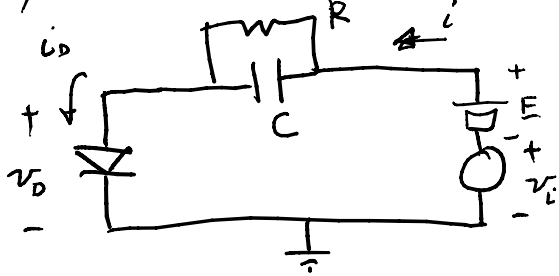


For exam - as on the list

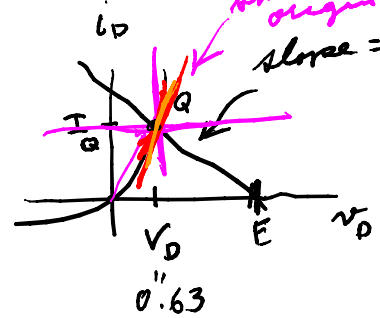

for bias work at DC

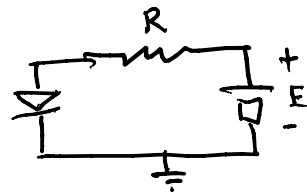C = open;  $v_i \rightarrow 0$   
small signal origin  
slope =  $1/R$



at DC

$$i_D = 10^{-13} (e^{v_D/V_T} - 1)$$

$$\approx I_S e^{v_D/V_T}$$

for  $V_D = 0.63V$  ;  $E = 3V$   
 $T = 100m$   
 $V_T = 26mV$


$$I_Q = 10^{-13} e^{0.63/0.026}$$

$$= 10^{-13} e^{24.23}$$

$$= 3.34 \times 10^{-13} \times 10^{10} = 3.34 mA$$

Then R:  $G = \frac{I_Q}{E - V_D} = \frac{3.34 \times 10^{-3}}{3 - 0.6}$  ;  $R = \frac{1}{G} = \frac{2.4}{3.34} k\Omega = 719\Omega$

For small signals

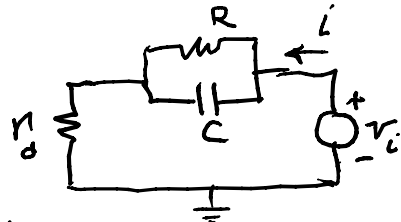

$$g_d = \left. \frac{di_D}{dv_D} \right|_Q = \frac{I_S}{V_T} \cdot e^{v_D/V_T} = \frac{I_Q}{V_T}$$

$$r_d = \frac{1}{g_d} = \frac{V_T}{I_Q} = \frac{0.026}{3.34 \times 10^{-3}}$$

$$= \frac{26}{3.34} \times 10^{-3} \times 10^3 = 7.78 \Omega$$

let  $C = 0.1 nF_d = 0.1 \times 10^{-9} f_d$

If desire small signal current, use admittance

$$Y(s) = \frac{I(s)}{V_i(s)} = \frac{1}{Z(s)} = \frac{1}{r_d + \frac{1}{G + Cs}} = \frac{G + Cs}{(r_d G + 1) + r_d Cs}$$

$$Y(s) = \frac{C(s + G/C)}{r_d C (s + \frac{1+r_d G}{r_d C})} = \frac{1}{r_d} \frac{(s + G/C)}{(s + \frac{1+r_d G}{r_d C})}$$

$$Y(s) = \frac{1}{7.78} \left( \frac{s + z_n}{s + p_d} \right), \quad z_n = \frac{1}{719 \times 0.1 \times 10^{-6}} = \frac{1}{0.0719} \times 10^4 = 1.39 \times 10^4$$

$$p_d = \frac{1 + 7.78 \times \frac{1}{719}}{7.78 \times 0.1 \times 10^{-6}} = \frac{1.011}{0.778 \times 10^{-7}} = 1.30 \times 10^7 = 13 \times 10^6$$

$$Y(s) = 0.13 \left( \frac{s + 1.39 \times 10^4}{s + 13 \times 10^6} \right)$$

Choose  $v_i(t) = 2 \times 10^{-6} \sin(2\pi \times 10^6 t)$        $f = 1 \text{ MHz}$

$$Y(j\omega) \Big|_{\omega_i = 2\pi \times 10^6} = 0.13 \left( \frac{j2\pi \times 10^6 + 1.39 \times 10^4}{j2\pi \times 10^6 + 13 \times 10^6} \right) = |Y(j\omega_i)| e^{j\phi} Y(j\omega_i)$$

$$\omega_i = 2\pi \times 10^6 \quad i(t) = |Y(j\omega_i)| \cdot (2 \times 10^{-6}) \sin(2\pi \times 10^6 t + \phi + Y(j\omega_i))$$

$$|Y(j\omega)| = 0.13 \frac{|1.39 \times 10^4 + j2\pi \times 10^6|}{|13 \times 10^6 + j2\pi \times 10^6|} = 0.13 \times 10^{-2} \frac{|1.39 + j200\pi|}{|13 + j2\pi|}$$

$$\approx \frac{0.13 \times 10^{-2} \times 200\pi}{\sqrt{(13)^2 + (2\pi)^2}} \approx \frac{0.13}{13.7} \times 6.28 = 0.06$$

$$|i(t)| = 2 \times 10^{-6} \times 6 \times 10^{-2} = 1.2 \times 10^{-7} = 0.12 \text{ pA}$$

$$\text{phase} = \left. \begin{array}{l} \text{numerator} = \pi/2 = 90^\circ \\ \text{denominator} = \tan^{-1}\left(\frac{2\pi}{13}\right) = 25.8^\circ \end{array} \right\} (90 - 25.8)^\circ = 64.2^\circ$$

$$i(t) = 0.12 \times 10^{-6} \sin(2\pi \times 10^6 t + 64.2^\circ)$$