

File: E:/courses/spring2007/303/hmwrk1.doc RWN 01/24/07


Homework Set 1 due Friday 02/02/07

If not yet done, download the bicos12 files and the 4007 (=RCA36000) CMOS models (in Spice model file ANL_MISC.lib) to use in your Spice programs. For grading purposes submit your circuit diagrams as well as requested plots.

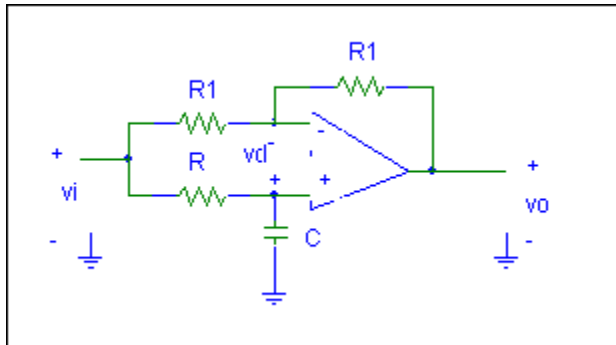1. [50 points] (analysis and transfer function of an op-amp circuit)

For the following calculate the transfer function $T(s)=V_o/V_i$ under the two conditions:

- The op amp is ideal. Also sketch the frequency response magnitude of $T(j\omega)$.
- The op amp is linear and described by $V_o(s)=[K/(1+(s/\omega_o)))]V_d(s)$



2. [50 points] (use of DC sweeps with parameters for NMOS transistors)

Set up the following two circuits in Spice using mnmosis transistors (from the bicos12 library) and then do dc runs. For part a) fix $V_{bias1}=V_{bias2}=2V$ and vary V_{dd1} and V_{dd2} from 0 to 8V in DC sweeps.

- For each circuit plot the drain current, I_D , versus the drain voltage measured with respect to ground (that is the indicated V_{dd}).
- Use V_{bias1} as a nested DC sweep from -4V to +4V in 2V steps, and repeat part a) for the left circuit.
- Choose the channel width, W , as a parameter, varying it from 5u to 20u in 5u steps (giving four curves on a plot) and repeat part a). Then also repeat part b) with W still a parameter.

