
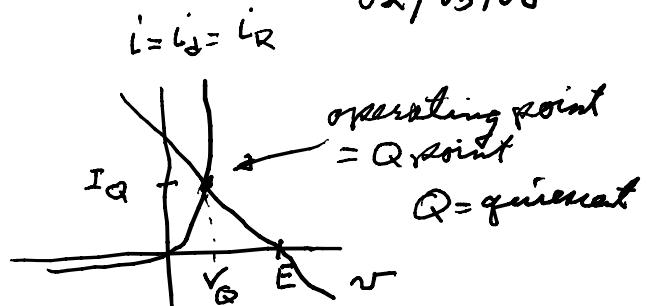


EE 303
02/05/08


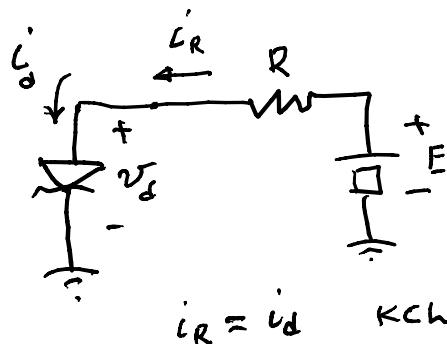


$$\text{KVL: } v = v_d = E - Ri \Rightarrow i = \frac{1}{R}(E - v) = -Gv + GE, \quad G = 1/R$$

$$i_d = I_s(e^{v_d/V_T} - 1) = -Gv + GE \quad \text{desire to solve}$$

$$= I_s(e^{v/V_T} - 1) = -Gv + GE$$

$$Gv + I_s e^{v/V_T} = GE + I_s$$

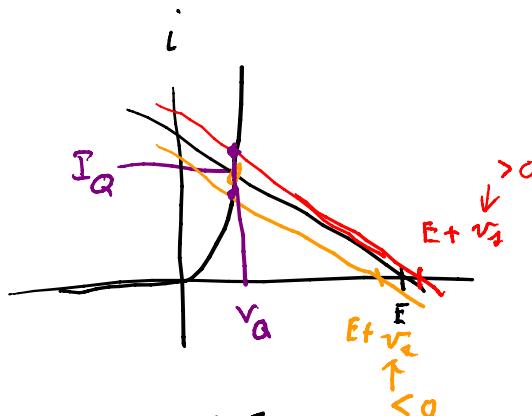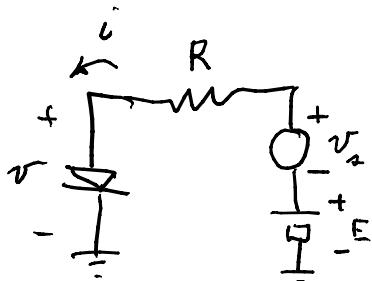

$$i_D = f(v_d) = I_D + \frac{df(v_d)}{dv_d} \Big|_{V_Q} (v_d - V_Q) + \frac{1}{2} \frac{df^2(v_d)}{dv_d^2} \Big|_{V_Q} (v_d - V_Q)^2 + \dots$$

= Taylor series expansion about Q point

$$\approx I_D + \frac{df(v_d)}{dv_d} \Big|_Q (v_d - V_Q) \quad \text{if} \quad |v_d - V_Q|^2 \ll |v_d - V_Q|$$


"
 $g = \text{conductance}$

$$i_d = i_D - I_D = g(v_d - V_Q) \Rightarrow \Delta i_d = g \Delta v_d$$

$$= g v_d$$

$$i_D = I_S (e^{V_D/V_T} - 1); \quad \frac{d i_D}{d V_D} \Big|_{V_Q} = \frac{I_S \cdot 1}{V_T} e^{\frac{V_D}{V_T}} \Big|_{V_Q} = \frac{I_S}{V_T} e^{\frac{V_D}{V_T}}$$

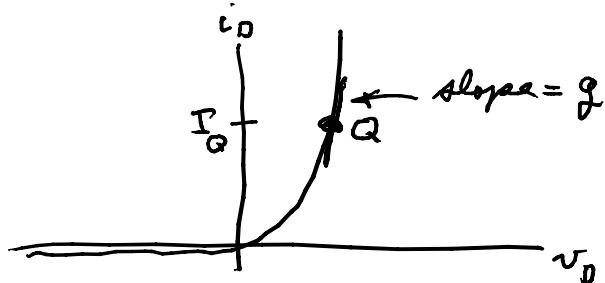for $V_D > 0$, $i_D \approx I_S e^{\frac{V_D}{V_T}}$



$$V_T = \frac{kT}{q} \approx 25 \text{ mV} @ \text{room T}$$

