

appendix B - 2-port network parameters

EE 303


02/19/08




$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

Y matrix
linear equations

Equivalent circuit

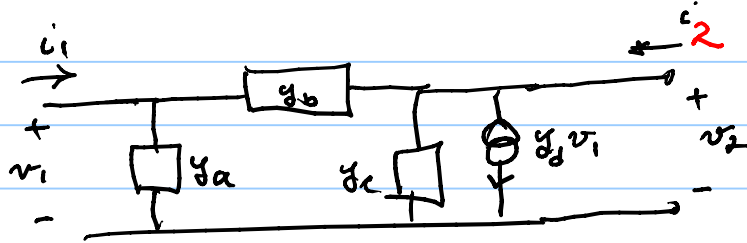


$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0}$$

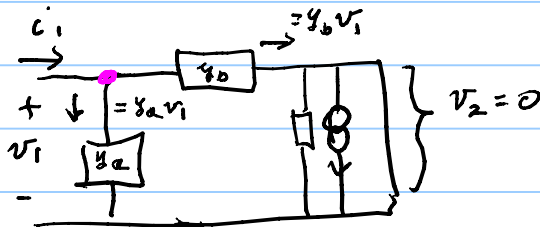

$$i_1 = y_a v_1 + y_b v_1$$

$$y_{11} = y_a + y_b$$

$$y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0}$$

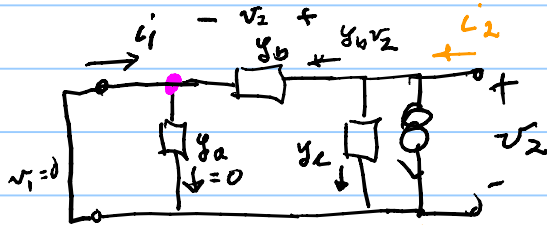

$$i_1 = -y_b v_2$$


$$y_{12} = -y_b$$

$$y_{22} = \left. \frac{i_2}{v_2} \right|_{v_1=0}$$

$$i_2 = y_b v_2 + y_c v_2$$

$$y_{22} = y_b + y_c$$

$$y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0}$$

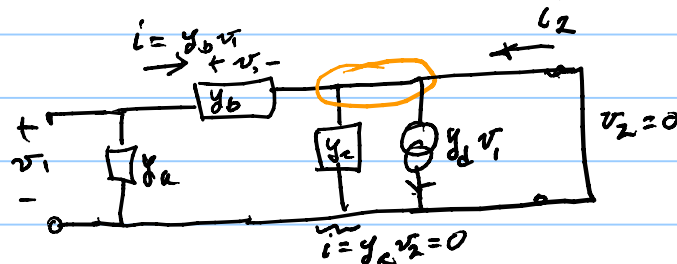



$$i_2 = -y_b v_1 + y_d v_1$$

$$y_{21} = -y_b + y_d$$

$$Y = \begin{bmatrix} y_a + y_b & -y_b \\ -y_b + y_d & y_b + y_c \end{bmatrix} = \begin{bmatrix} y_b & -y_b \\ -y_b & y_b \end{bmatrix} + \begin{bmatrix} y_a & 0 \\ y_d & y_c \end{bmatrix}$$


here $y_{12} = -y_b$ $y_{11} = y_a + y_b \Rightarrow y_a = y_{11} + y_{12}$
 $\Rightarrow y_b = -y_{12}$ $y_{22} = y_c + y_b \Rightarrow y_c = y_{22} + y_{12}$
 $y_{21} = y_d - y_b \Rightarrow y_d = y_{21} + y_b = y_{21} - y_{12}$

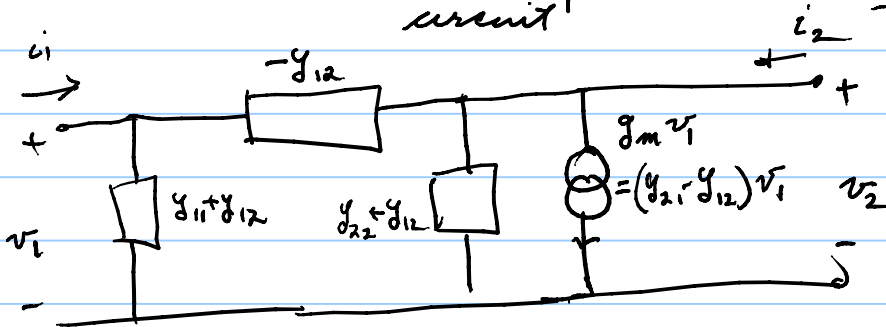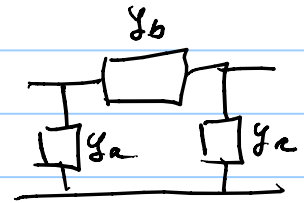If $Y = Y^T$ (i.e. $y_{12} = y_{21}$) then $y_d = 0$ & we get the π equivalent circuit




total small signal bias
 ↓ ↓ ↓

$i_G = i_g + I_G$

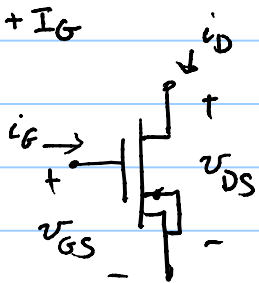


total

$i_D = i_d + I_D$

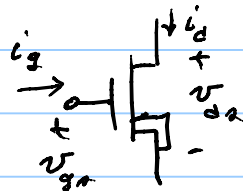

small signal

$v_{GS} = v_{gs} + V_{GS}$

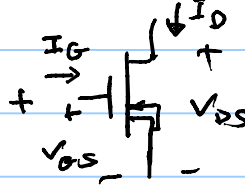


bias

$v_{DS} = v_{ds} + V_{DS}$

uses linear term in Taylor series expansion & use Y matrix to describe

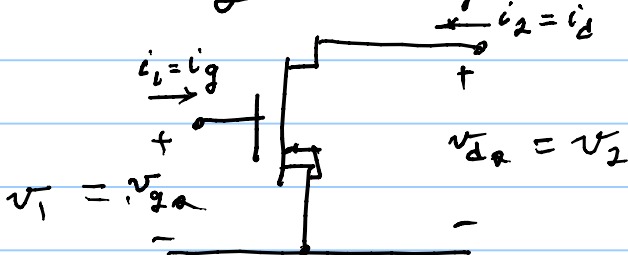here usually use the grounded source Y matrix



at low freq. $i_g = 0$ $y = \begin{bmatrix} 0 & 0 \end{bmatrix}$

If in saturation at Q point then $i_D = \frac{K_P W}{2 L} (V_{GS} - V_{TO})^2 (1 + \lambda V_{DS})$

$$i_D = I_D + \frac{\partial i_D}{\partial V_{GS}} \Big|_Q (V_{GS} - V_{GS}) + \frac{\partial i_D}{\partial V_{DS}} \Big|_Q (V_{DS} - V_{DS}) + \text{(Terms of higher order ignore for now)}$$

$$i_1 = i_D - I_D = \frac{\partial i_D}{\partial V_{GS}} \Big|_Q v_{gs} + \frac{\partial i_D}{\partial V_{DS}} \Big|_Q v_{ds} \Rightarrow i_2 = \underbrace{\left(\frac{\partial i_D}{\partial V_{GS}} \right)}_{g_{m1}} v_1 + \underbrace{\left(\frac{\partial i_D}{\partial V_{DS}} \right)}_{g_{m2}} v_2$$


for our transistor in saturation

$$\frac{\partial i_D}{\partial V_{GS}} \Big|_Q = \frac{K_P W}{2 L} [2(V_{GS} - V_{TO})(1 + \lambda V_{DS})] \Big|_Q = g_{m1} = K_P \cdot \frac{W}{L} (V_{GS} - V_{TO})(1 + \lambda V_{DS}) = g_m$$


$$\frac{\partial i_D}{\partial V_{DS}} \Big|_Q = \frac{K_P W}{2 L} (V_{GS} - V_{TO})^2 \cdot \lambda \Big|_Q = I_D \cdot \frac{\lambda}{1 + \lambda V_{DS}} = g_{m2} = g_d$$

$$Y = \begin{bmatrix} 0 & 0 \\ g_m & g_d \end{bmatrix} \Rightarrow \begin{array}{c} i_i \\ + \\ v_i \end{array} \begin{array}{c} b \\ q \\ g_d \\ g_m v_i \end{array} = \begin{array}{c} o \\ t \\ f \\ e \\ t \end{array}$$

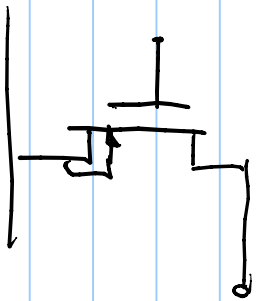at higher frequency we see gate capacitances; add C_{gd} , C_{gs}




\equiv

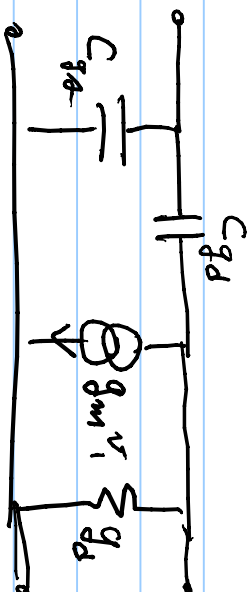

small signal

i_D

i_D

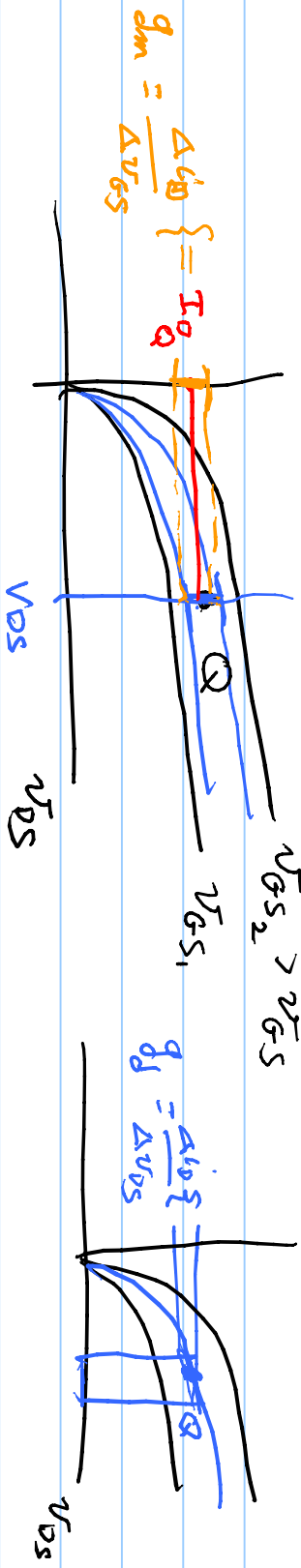

Deriv BST

