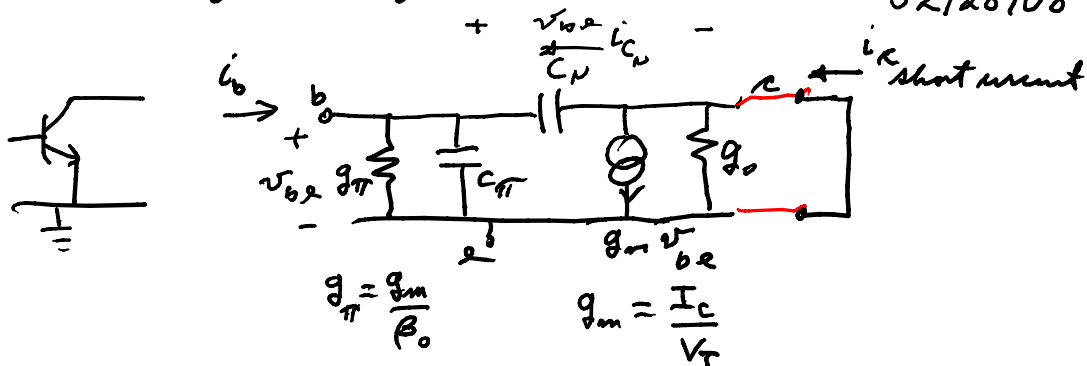


f_T = transition frequency

EE 303
02/28/08



$$\frac{i_c}{i_b} = \beta(\omega)$$

$$i_c = g_m v_{be} + (-sC_{\mu} v_{be}) = (g_m - sC_{\mu}) v_{be}$$


$$i_b = g_{\pi} v_{be} + sC_{\pi} v_{be} + sC_{\mu} v_{be}$$

$$= \frac{g_m - sC_{\mu}}{g_{\pi} + s(C_{\pi} + C_{\mu})}$$

$$= [g_{\pi} + s(C_{\pi} + C_{\mu})] v_{be}$$

$$= \frac{g_m}{g_{\pi}} \left[\frac{1 - s(C_{\mu}/g_m)}{1 + s(C_{\pi} + C_{\mu})/g_{\pi}} \right]$$
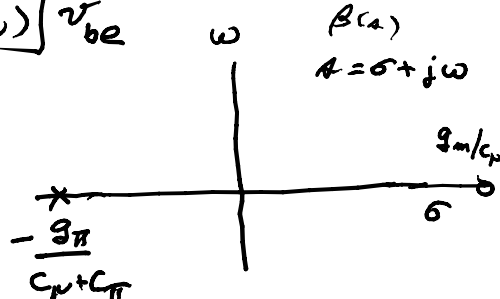
$$= \beta_0 \left[\frac{1 - s/\omega_0}{1 + s/\omega_p} \right] \approx \frac{\beta_0}{1 + s \left[\frac{C_{\pi} + C_{\mu}}{g_{\pi}} \right]}$$



$$\beta(\omega) = \frac{\beta_0}{1 + s/\omega_p} ; \quad \beta(j\omega) = \frac{\beta_0}{1 + j\frac{\omega}{\omega_p}} \Rightarrow \beta(j\omega_p) = \frac{\beta_0}{1 + j1}$$

$$|\beta(j\omega_p)| = \frac{\beta_0}{\sqrt{2}}$$

ω_T is where $|\beta(j\omega_T)| = 1$

$$|\beta(j\omega)| = \frac{\beta_0}{\sqrt{1 + (\frac{\omega}{\omega_p})^2}} \Rightarrow 1 \approx \frac{\beta_0}{\left(\frac{\omega_T}{\omega_p}\right)} \Rightarrow \omega_T = \beta_0 \times \omega_p = \beta_0 \cdot \frac{g_m}{C_{\pi} + C_{\mu}}$$


$$f_T = \frac{1}{2\pi} \times \beta_0 \times \frac{g_m}{C_{\pi} + C_{\mu}} = \frac{1}{2\pi} \frac{\beta_0 \cdot g_m}{\beta_0 (C_{\pi} + C_{\mu})} = 2\pi f_T$$

$$= \frac{1}{2\pi} \cdot \frac{|I_C|/V_T}{C_{\pi} + C_{\mu}} ; \quad \text{Ex: } I_C = 2 \text{ mA}, C_{\pi} = 18 \text{ pF}, C_{\mu} = 2 \text{ pF}$$

$$V_T = 26 \text{ mV}$$




$$f_T = \frac{1}{2\pi} \times \frac{2 \times 10^{-3}}{26 \times 10^{-3}} \times \frac{1}{20 \times 10^{-12}} \approx \frac{10^{12}}{80 \times 20} = \frac{1}{1.6} \times 10^{11} \text{ Hz}$$

This is where β falls to 1 in magnitude
 $20 \log_{10} |\beta(j\omega)|$

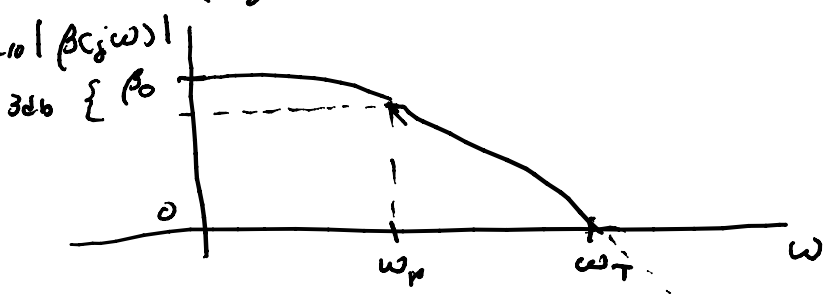

$\beta_0 = h_{FE} = (2, 1)$ entry of the H parameters for a "grounded" emitter in the "forward" direction

Biassing

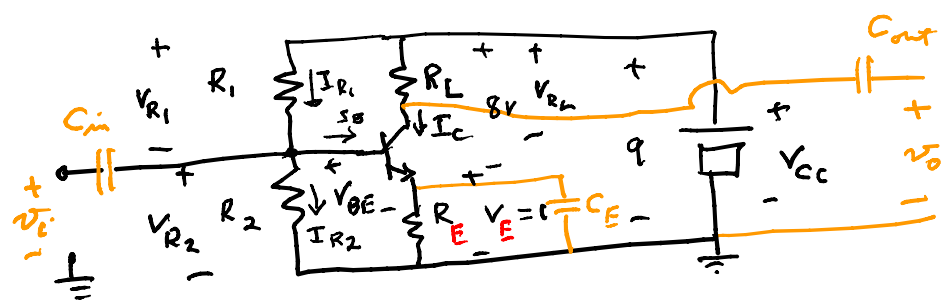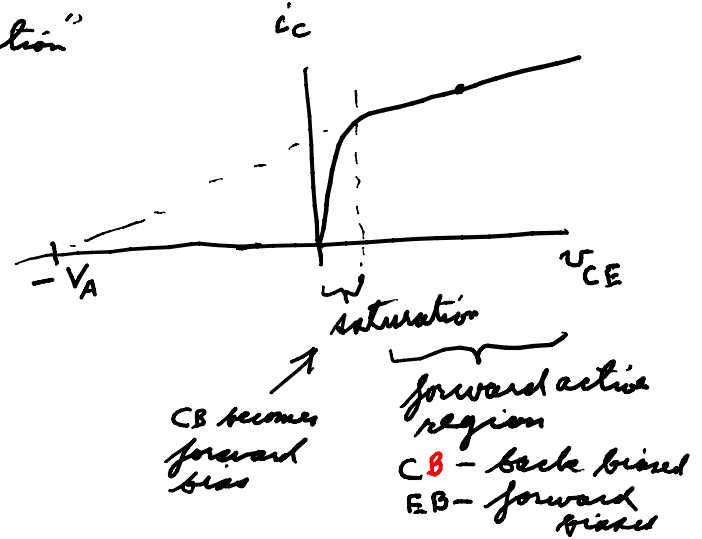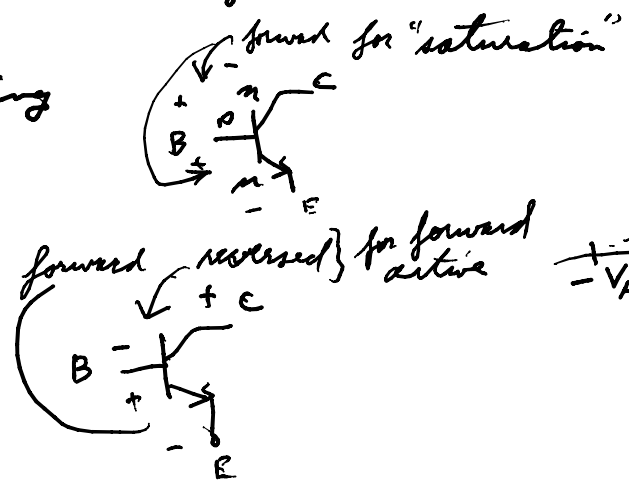

1st choice $g_m = \frac{I_C}{V_T}$; $\alpha = \frac{\beta_0}{\beta_0 + 1}$; $|I_E| \approx I_C$; $I_C = -\alpha I_E$

fix R_C to give $V_E \approx 1V$; $V_{R2} = V_{BE} + V_E = 0.7 + V_E$

$V_{R1} = V_{CC} - V_{R2}$; if we know β_0 & I_C we know I_B
 $I_B \approx I_C / \beta_0$

$$I_C = 2 \text{ ma}, \beta_0 = 100 \Rightarrow I_B = \frac{2 \times 10^{-3}}{101} = 20 \times 10^{-6} = 20 \mu\text{amp}$$

$$I_{R_1} = I_B + I_{R_2}, \quad V_{R_2} = 0.7 + V_E; \text{ choose } V_E = 1.3 \text{ V}$$

$$\alpha = \frac{\beta}{1+\beta} = \frac{100}{101} \approx 1 \quad R_E = \frac{V_E}{|I_{E1}|} = \frac{1.3 \text{ V}}{2 \text{ ma}} = 0.65 \text{ k}\Omega = 650 \Omega$$

$$V_{R_2} = 0.7 + 1.3 = 2 \text{ V}$$

Choose V_{CC} a battery of 9V

$$V_{R_1} = V_{CC} - V_{R_2} = 9 - 2 = 7 \text{ V}$$

$$\text{choose } R_2 = 1 \text{ MEG } \Omega; \quad I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{2 \text{ V}}{1 \text{ MEG}} = 2 \times 10^{-6} \text{ A}$$

$$I_{R_1} = 2 \times 10^{-6} + 20 \times 10^{-6} = 22 \mu\text{amp}$$

$$V_{R_1} = 7 \text{ V} \Rightarrow R_1 = \frac{7}{22 \mu\text{A}} = \frac{70 \times 10^{-1}}{22 \times 10^{-6}} \approx 3 \times 10^5 = 30 \text{ k}\Omega$$

$$\text{choose } I_C = 2 \text{ ma}, \quad g_m = \frac{I_C}{V_T} = \frac{2 \times 10^{-3}}{26 \times 10^{-3}} = \frac{1}{13}$$

$$\frac{V_o}{V_i} = G = \text{Voltage gain} \approx -g_m R_L = -\frac{1}{13} R_L \quad \text{if } G = -10 \Rightarrow R_L = 130$$

$$V_{R_L} = R_L \times I_C = 130 \times 2 \times 10^{-3} = 260 \times 10^{-3} = 0.26 \text{ V}$$

$$V_{CE} = V_{CC} - V_E - V_{R_L} = 9 - 0.26 = 8.74$$

