

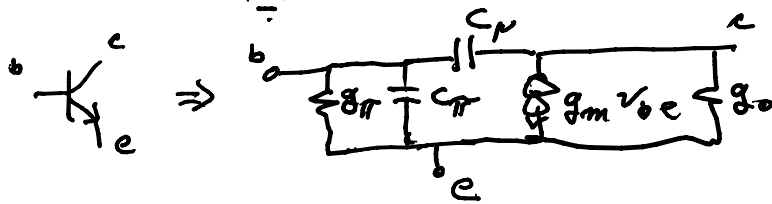
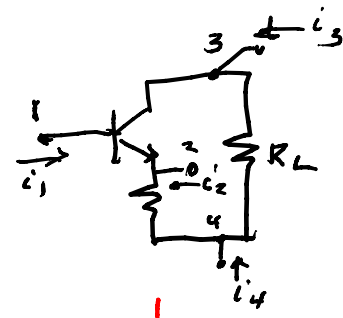


EE303  
03/04/08

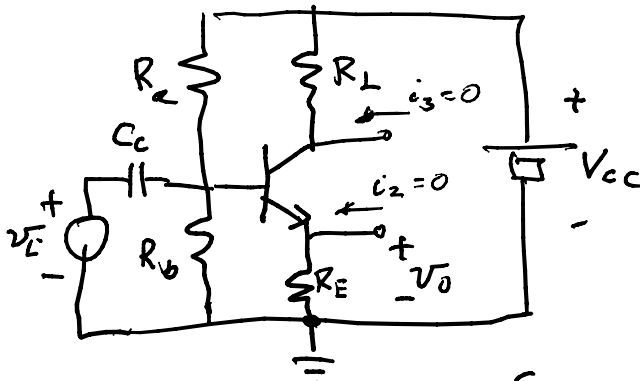
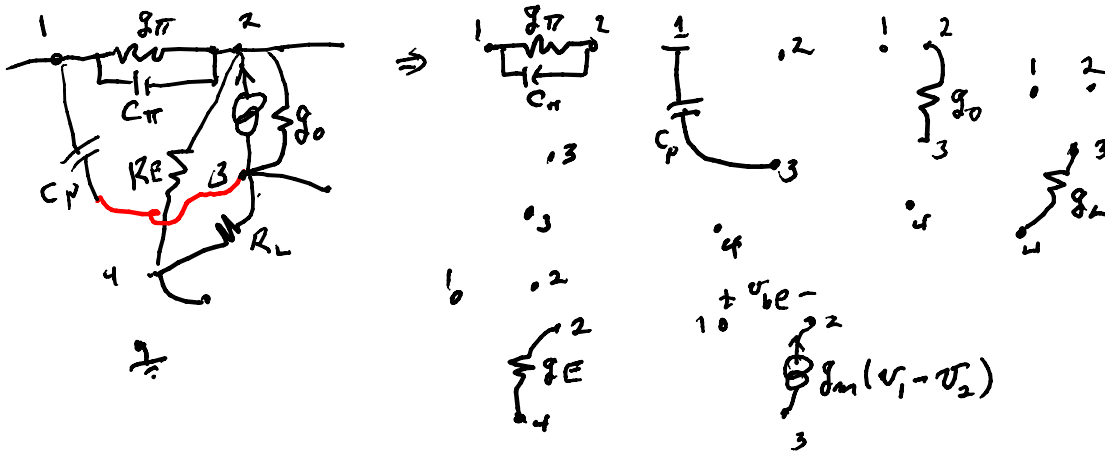
$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = Y_{ind} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} \rightarrow 0$$




$$Y_{ind} = \begin{bmatrix} g_\pi + sC_\pi & -(g_\pi + sC_\pi) & 0 & 0 \\ -(g_\pi + sC_\pi) & g_\pi + sC_\pi & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} + \begin{bmatrix} sC_\pi & 0 & -sC_\pi & 0 \\ 0 & 0 & 0 & 0 \\ -sC_\pi & 0 & sC_\pi & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & g_o & -g_o & 0 \\ 0 & -g_o & g_o & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & g_L & -g_L \\ 0 & 0 & -g_L & g_L \end{bmatrix}$$

$$\pm \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & g_E & 0 & -g_E \\ 0 & 0 & 0 & 0 \\ 0 & -g_E & 0 & g_E \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 & 0 \\ -g_m & g_m & 0 & 0 \\ g_m & -g_m & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix} = \begin{bmatrix} g_\pi + s(C_\pi + C_\pi) & -g_\pi - sC_\pi & -sC_\pi & 0 \\ -g_\pi - sC_\pi & g_\pi + g_o + g_E + g_m + sC_\pi & -g_o & -g_E \\ -sC_\pi + g_m & -g_o - g_m & sC_\pi + g_o + g_L & -g_L \\ 0 & -g_E & -g_L & g_E + g_L \end{bmatrix}$$

can ignore  $i_4$  when set  $v_4 = 0 \Rightarrow$  delete 4th row & column

$$Y_{nodal} = \begin{bmatrix} g_\pi + s(C_\pi + C_\pi) & -g_\pi - sC_\pi & -sC_\pi \\ -g_\pi - sC_\pi - g_m & g_o + g_\pi + g_m + g_E + sC_\pi & -g_o \\ +g_m - sC_\pi & -g_o - g_m & g_o + g_L + sC_\pi \end{bmatrix} \Rightarrow \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = Y_{nodal} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix}$$

Roughly

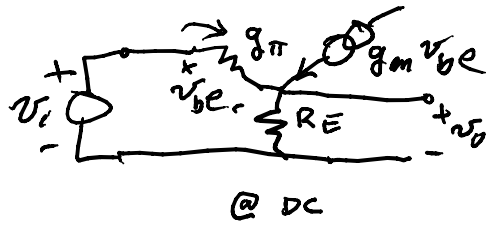

$$1) v_o = R_E (g_m + g_\pi) v_{be}$$

$$2) v_i = v_{be} + v_o \Rightarrow v_{be} = v_i - v_o$$

$$2) \rightarrow 1) \rightarrow v_o = R_E (g_m + g_\pi) [v_i - v_o]$$

$$\frac{v_o}{v_i} = \frac{(g_m + g_\pi) R_E}{1 + R_E (g_m + g_\pi)} < 1$$

$$i_3 = 0 = \begin{bmatrix} g_m - \alpha C_p & -g_o - g_m \\ -g_\pi - \alpha C_p & g_o + g_m + g_\pi + g_E + \alpha C_p \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + (g_o + g_L + \alpha C_p) v_3$$

$$v_3 = \frac{1}{g_o + g_L + \alpha C_p} \begin{bmatrix} g_m - \alpha C_p & -g_o - g_m \\ -g_\pi - \alpha C_p & g_o + g_m + g_\pi + g_E + \alpha C_p \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$Y_{2-port} = \begin{bmatrix} g_\pi + \alpha(C_p + C_n) & -g_\pi + \alpha C_n \\ -g_\pi - \alpha C_p & g_o + g_m + g_\pi + g_E + \alpha C_p \end{bmatrix} \begin{bmatrix} -1 \\ \frac{g_o + g_L}{\alpha C_p} \end{bmatrix} \begin{bmatrix} -\alpha C_p [g_m - \alpha C_p & -g_o - g_m] \\ -g_o \end{bmatrix}$$

$$= \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \quad \left. \begin{array}{l} \frac{v_2}{v_1} \\ i_2 = 0 \\ (= \text{no load}) \end{array} \right| \Rightarrow 0 = y_{21} v_1 + y_{22} v_2 \Rightarrow \frac{v_2}{v_1} = -\frac{y_{21}}{y_{22}}$$

$$\frac{v_2}{v_1} = \frac{v_o}{v_i} = \frac{(-g_\pi - \alpha C_p)(g_o + g_L + \alpha C_p) + g_o (g_m - \alpha C_p)}{(g_o + g_m + g_\pi + g_E + \alpha C_p)(g_o + g_L + \alpha C_p) - g_o (g_o + g_m)}$$


$$\frac{v_o}{v_i} \Big|_{\alpha=0} = \frac{(-g_\pi)(g_o + g_L) + g_o g_m}{(g_o + g_m + g_\pi + g_E)(g_o + g_L) - g_o (g_o + g_m)}$$

$$\text{for } g_o \rightarrow 0 = \frac{-g_\pi g_L}{(g_m + g_\pi + g_E) g_L} =$$

$$g_L \rightarrow \infty = \frac{-(g_\pi + g_m)}{g_m + g_\pi + g_E} \Rightarrow \frac{v_o}{v_i}(\infty) = \frac{(g_\pi + g_m)/g_E}{1 + (g_m + g_\pi)/g_E} < 1$$

note the sign

---  
Differential pairs:

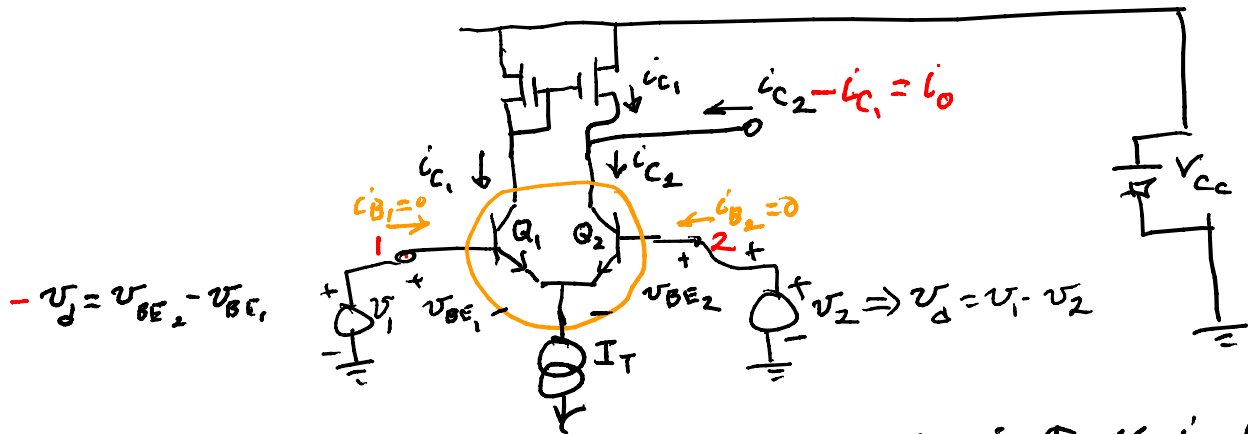


$I_T = i_{C1} + i_{C2}$   
 " tail current

if  $I_T = \text{fixed}$ , when  $i_{C1} \uparrow$  then  $i_{C2} \downarrow$

with BJT

$i_o = I_T \tanh\left(\frac{v_d}{2V_T}\right)$

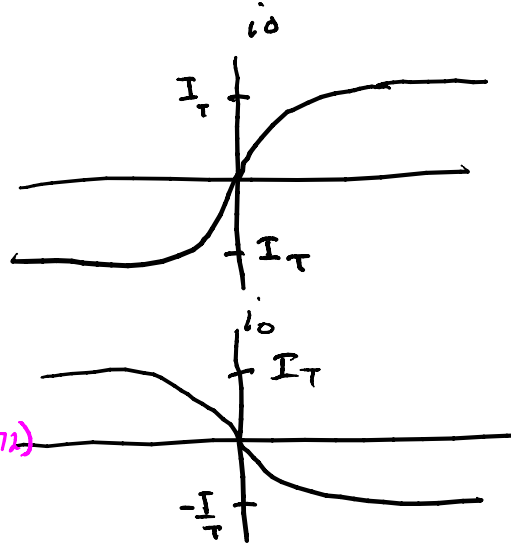see p. 707 of text  
after combine (7.73) - (7.72)



$v_{BE2} - v_{BE1} = -v_d$   
 " input  
 $v_d = \text{difference}$

$v_1 - v_2 = v_d$