

$$-V_1 + V_{GS1} - V_{GS2} + V_2 = 0 \text{ KVL}$$

$$V_{GS1} - V_{GS2} = V_1 - V_2 = V_{id}$$

$$\text{KCL } I_1 + I_2 - I_T = 0 \text{ (@ DC)}$$

$I_1, I_2$  assume  $M_1 = M_2$  in saturation & Early effect negligible

$$I_1 = \frac{K_P W}{2 L} (V_{GS1} - V_{TH})^2 \quad , \quad I_2 = \frac{K_P W}{2 L} (V_{GS2} - V_{TH})^2 \quad , \quad V_{TH} = V_{TO} \quad , \quad \beta = \beta = S$$

$$+ \sqrt{\frac{I_1}{\frac{K_P W}{2 L}}} = V_{GS1} - V_{TH}$$

$$+ \sqrt{\frac{I_2}{\frac{K_P W}{2 L}}} = V_{GS2} - V_{TH}$$

$$V_{id} = V_{GS1} - V_{GS2} = \frac{1}{\sqrt{\frac{K_P W}{2 L}}} (\sqrt{I_1} - \sqrt{I_2})$$

$$I_1 + I_2 - 2\sqrt{I_1 I_2} = \frac{K_P W}{2 L} V_{id}^2 \Rightarrow \sqrt{I_1 I_2} = \frac{I_T}{2} - \frac{K_P W}{4 L} V_{id}^2$$

$$I_1 I_2 = I_1 (I_T - I_1) = -I_1^2 + I_T I_1 = \frac{1}{4} \left( I_T - \frac{K_P W}{2 L} V_{id}^2 \right)^2$$

$$I_1^2 - I_T I_1 + \frac{1}{4} \left( I_T - \frac{K_P W}{2 L} V_{id}^2 \right)^2 = 0$$

$$I_1 = \frac{I_T}{2} \pm \frac{1}{2} \sqrt{I_T^2 - \left( I_T^2 - 2 I_T \frac{K_P W}{2 L} V_{id}^2 + \left( \frac{K_P W}{2 L} \right)^2 V_{id}^4 \right)}$$

$$= \frac{I_T}{2} \pm \frac{1}{2} V_{id} \sqrt{2 I_T \frac{K_P W}{2 L} - \left( \frac{K_P W}{2 L} \right)^2 V_{id}^2}$$

$$= \frac{I_T}{2} \pm \frac{1}{2} V_{id} \frac{K_P W}{2 L} \sqrt{\frac{2 I_T}{\frac{K_P W}{2 L}} - V_{id}^2}$$

$$I_2 \text{ by symmetry: } I_2 = \frac{I_T}{2} - \frac{1}{2} V_{id} \left( \frac{K_P W}{2 L} \right) \sqrt{\frac{2 I_T}{\frac{K_P W}{2 L}} - V_{id}^2}$$

We know  $I_1$  vs  $V_{id}$  is nondecreasing (& monotonic)

$I_T$  increases to increase when  $I_T = I_T$   
 $\therefore$  look for  $V_{id} \rightarrow 0$  for which

$$\rightarrow \frac{V_{id}}{2} \frac{K_{PM}}{2} \sqrt{2 I_T / \frac{K_{PM}}{2}} - V_{id}^2 = \frac{I_T}{2}$$

$$V_{id}^2 \left( \frac{K_{PM}}{2} \right)^2 \cdot \left( 2 I_T / \frac{K_{PM}}{2} \right) - V_{id}^2 = I_T^2 \quad \text{Let } x = V_{id}^2, \quad b = \frac{K_{PM}}{2}$$


$$-x^2 \cdot b^3 + 2 I_T b \cdot x - I_T^2 = 0$$

$$x^2 - 2 I_T b + (I_T/b)^2 = 0$$


$$x = \frac{I_T b}{2} \pm \frac{1}{2} \sqrt{4 I_T^2 - 4 (I_T/b)^2} = \frac{I_T}{b} \pm \frac{I_T}{b} \sqrt{0}$$

$$V_{id}^2 = I_T/b = I_T / \frac{K_{PM}}{2} \quad ; \quad V_{id} = \pm \sqrt{I_T / \frac{K_{PM}}{2}}$$
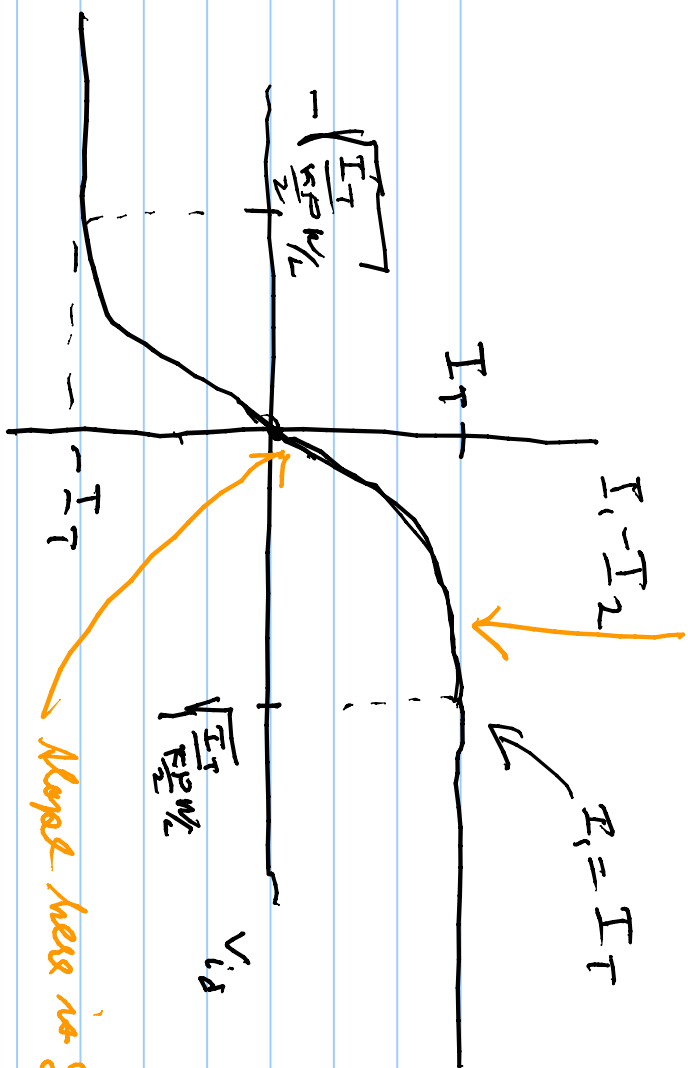
$$I_1 - I_2 = V_{id} \left( \frac{K_{PM}}{2} \right) \sqrt{2 \frac{I_T}{\left( \frac{K_{PM}}{2} \right)}} - V_{id}^2$$



To create the tail current:

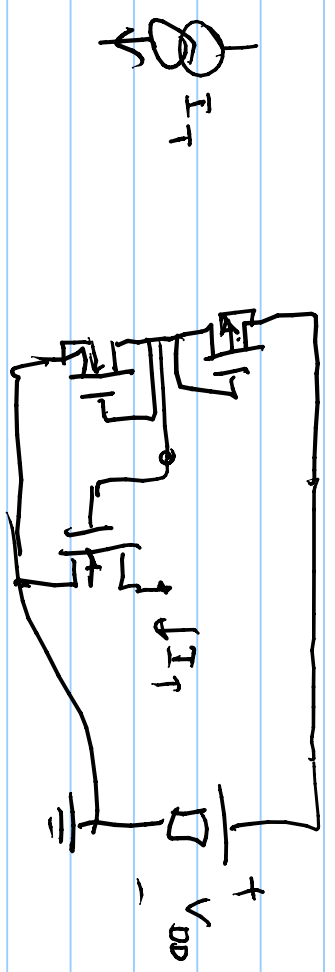

$$\begin{aligned}
 &= \frac{C_1 - C_2}{V_{id}} \\
 &= \frac{k_p W}{2L} \sqrt{\frac{2I_T}{k_p W / 2L}} \\
 &= \sqrt{2I_T \cdot \frac{k_p W}{2L}}
 \end{aligned}$$



