

File: E:/courses/spring2008/303/hmwrk1.doc RWN 02/05/08

Homework Set 1 due Thursday 02/14/08

If not yet done, download the bimos12 files, the 4007 (=RCA36000) CMOS models (in Spice model file ANL_MISC.lib), and the npn Q2n3904 and the pnp Q2n3906 (both in model file eval.lib) to use in your Spice programs. For grading purposes submit your circuit diagrams as well as requested plots.

1. [50 points] (diode characteristics and load line.)

In Spice connect the collector to the base of a 2n3904 to make a pn diode.

- Plot the current versus voltage for this diode.
- Connect a 5v DC source in series with a 1KOhm resistor and plot this load line on the diode characteristic. From this determine the Q point.
- Make the resistance to be a parameter going from 500Ohms to 2KOhms in 500Ohm steps and give the Q point values for each.

2. [50 points] (use of DC sweeps with parameters for PMOS transistors)

Set up the following two circuits in Spice using mpmosis transistors (from the bimos12 library) and then do dc runs. For part a) fix $V_{bias1}=V_{bias2}=2V$ and vary V_{dd1} and V_{dd2} from 0 to 8V in DC sweeps.

- For each circuit plot the drain current, I_D , versus the drain voltage measured with respect to ground (note that I_D should be non-positive).
- Use V_{bias1} as a nested DC sweep from -4V to +4V in 2V steps, and repeat part a) for the left circuit.
- Choose the channel width, W , as a parameter, varying it from 5u to 20u in 5u steps (giving four curves on a plot) and repeat part a). Then also repeat part b) with W still a parameter.

