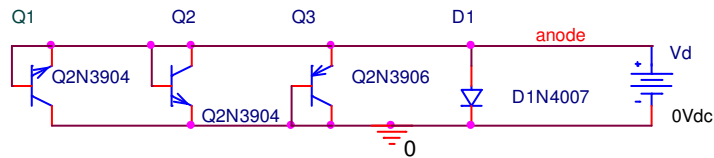
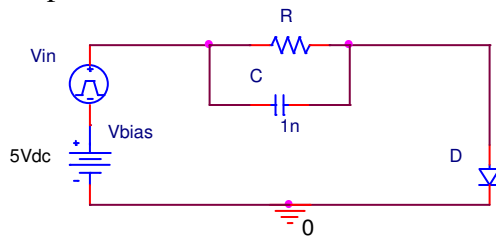


- Set up in Spice the following circuit and compare the diode curves. Plot in one “plot” the transistor diode characteristics and in another the diode’s. Vary V_d from -1V to +0.8V and plot the terminal currents. Also plot the reversed bias currents and compare.



- In the following circuit assume the diode is ideal in that it satisfies the exponential law, $i_D = I_S(\exp(v_D/V_T) - 1)$, but with the saturation current of the 1N4007, that is, $I_S = 14.11 \text{ nA}$.
 - Calculate V_D for $I_D = 3 \text{ mA}$ and with that the resistor value.
 - Draw the small signal equivalent circuit assuming V_{in} is a small signal and set up the first order differential equation for the capacitor voltage.
 - From the small signal equivalent circuit find the small signal current (downward) in the diode when $V_{in}(t)$ is a unit step function of 1 microVolt amplitude.



- Using the mmosis and mpmosis transistors find the width of the mpmosis transistor needed to set the output voltage, V_o , of the following circuit to 2.5V.

