

1. a) Using  $\beta=150$  and an Early voltage of  $|V_A|=\text{infinite}$ , find the voltages in part e) of Problem P. 5.79, pages 525-526 of the text. Discuss the change if  $|V_A|=100$ .  
b) Replace the pnp by an npn with the same parameters (and with collector at the top, emitter at the bottom) and repeat a).
2. In the circuit of Problem P 5.112, page 531 of the text, use  $\beta=100$  and  $|V_A|=150$  with  $C_\pi = 10\text{pFarad}$  (see figure 5.67 with  $C_\mu=0$  and  $r_x=0$ )
  - a) Find the  $f_T$  of the transistor.
  - b) Draw the small signal equivalent circuit.
  - c) Using the collector voltage as output find the voltage gain  $v_o(s)/v_i(s)$ .
3. For the circuit of Problem 4.54 of page 367 assume identical transistors and that  $V_{DD}$  is sufficiently large to allow both transistors to work in the saturation region.
  - a) Work Problem 4.54 of page 367 (here  $V_t=V_{T0}$  of Spice) and draw the small signal equivalent circuit (assume  $V_{GS}=2V_{T0}$  and use 4007 transistor parameters, KP, W, L, VTO and LAMBDA).
  - b) Using the 4007=CA3600 package draw the schematic for the circuit of Figure P4.54 in PSpice and do a DC run with  $V_{DD}=9\text{v}$  and  $0 \leq V_i \leq V_{DD}$ . [due to the substrate connections this will require two 4007 packages; be sure to tie off the transistors not used. Also have PMOS substrates at VDD and NMOs substrates at the lowest potential of the package (=chip)].