
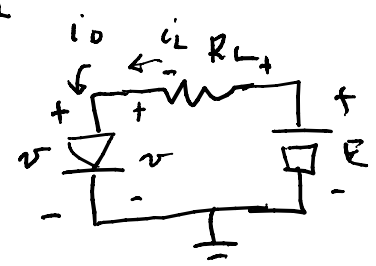


P.212

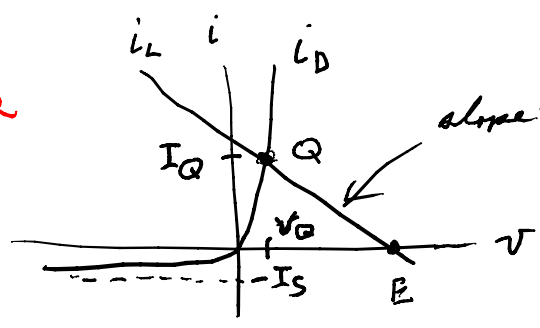

$$i_D = I_S (e^{v/V_T} - 1)$$

$$i_L = G_L (E - v)$$

$$V_T = \frac{kT}{q} \approx 26 \text{ mV @ room T}$$

$$v = E - R_L i_L$$

$$i_L = \frac{E - v}{R_L} = G_L (E - v)$$




V_Q solves this equation

$$i_L = i_D = I_S (e^{v/V_T} - 1) = G_L E - G_L v$$

$$= e^{v/V_T} + \frac{G_L}{I_S} v = 1 + \frac{G_L E}{I_S}$$

at transcendental we use a computer

Now put signal on

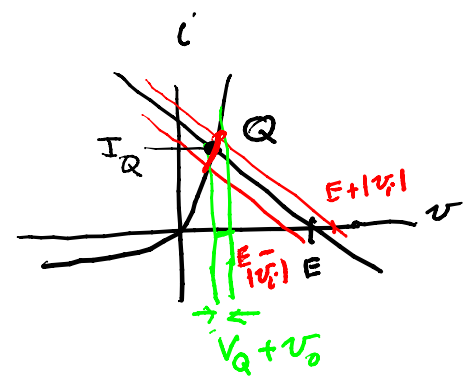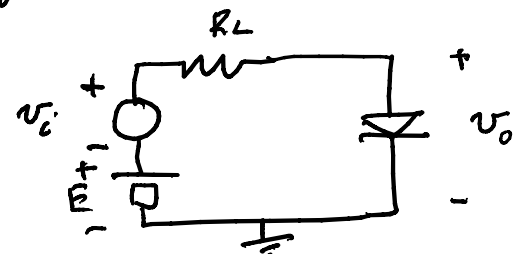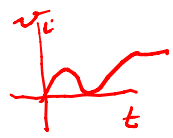

If v_i is small, $v_i(t)$, to find v_o


use a series expansion

$$i_D = i_D(t) = i_D(V_Q) + \left. \frac{\partial i_D}{\partial v_D} \right|_{v_D = V_Q} (v_D(t) - V_Q) + \dots$$


$$i_D(t) - i_D(V_Q) = i_D(t) - I_D = i_D = \text{signal part of diode current}$$

I_D = bias value of diode current
 i_D = total current in the diode


$$i_d = \left. \frac{\partial i_D}{\partial v_D} \right|_Q \cdot \underbrace{(v_D - V_Q)}_{\text{signal } v_d} \Rightarrow i_d^{(+)} = \left. \frac{\partial i_D}{\partial v_D} \right|_Q \cdot v_d^{(+)} \Rightarrow \text{linear equation for the diode operating at the Q point for small signals.}$$
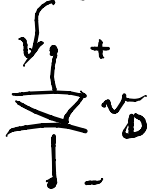
$$i_D = I_S (e^{v_D/V_T} - 1)$$


g_d { diode conductance

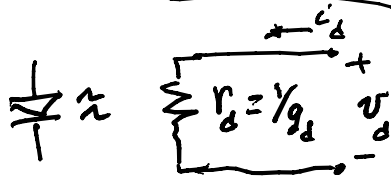

i. for small signal

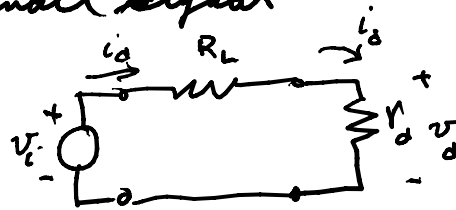

can analyze using linear theory

$$v_i = i_d \cdot R_L + i_d r_d = (R_L + r_d) \cdot i_d = (R_L + r_d) \cdot g_d \cdot v_d$$

here: $\frac{v_d}{v_i} (+) = \frac{1}{(R_L + r_d) \cdot g_d} = \frac{1}{1 + R_L \cdot g_d}$

for g_d : $g_d = \left. \frac{\partial i_D}{\partial v_D} \right|_Q \Rightarrow \left. \frac{\partial i_D}{\partial v_D} \right|_Q = \frac{\partial (I_S [e^{v_D/V_T} - 1])}{\partial v_D} \Big|_Q = \frac{I_S e^{v_D/V_T}}{V_T} \Big|_Q$

$$= \frac{I_S e^{v_Q/V_T}}{V_T}$$

If bias in forward region, $v_D > 0$ $(e^{v_D/V_T} - 1) \approx e^{v_D/V_T}$




$$I_D = I_S (e^{v_D/V_T} - 1) \approx I_S e^{v_D/V_T}$$

$$\Rightarrow g_d = \frac{I_D}{V_T}$$

if $I_D = 1 \text{ mA} = 10^{-3}$
 $\& V_T = 26 \text{ mV} \Rightarrow$

$$g_d = \frac{1}{26} ; r_d = 26 \Omega$$

BJT

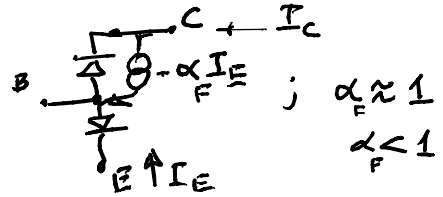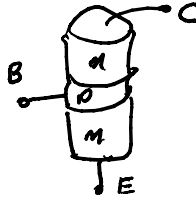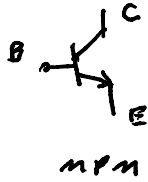

but n portion is very thin

