

defined via β

KCL $i_B + i_C + i_E = 0$ $-i_C = \alpha i_E$ $\alpha \approx 1, \alpha < 1$

$i_B = -i_C - i_E = -(-\alpha + 1)i_E = -(-\alpha + 1)(-\frac{1}{\alpha})i_C$

$i_C = \frac{\alpha}{1-\alpha} \cdot i_B = \beta i_B \Rightarrow \beta = \frac{\alpha}{1-\alpha}$

also $(1-\alpha)\beta = \alpha = \beta - \alpha\beta = \alpha \Rightarrow \beta = (1+\beta)\alpha \Rightarrow \alpha = \frac{\beta}{1+\beta}$


$\alpha = \frac{\beta}{1+\beta}$

$i_C = f(v_{CE}, i_B)$ for small signals

$= f(V_{CE_Q}, I_{B_Q}) + \frac{\partial i_C}{\partial v_{CE}} \Big|_Q (v_{CE} - V_{CE_Q}) + \frac{\partial i_C}{\partial i_B} \Big|_Q (i_B - I_{B_Q}) +$ ignores for small signal

$= I_C + g_{CE} \cdot v_{ce} + \beta \cdot i_b$

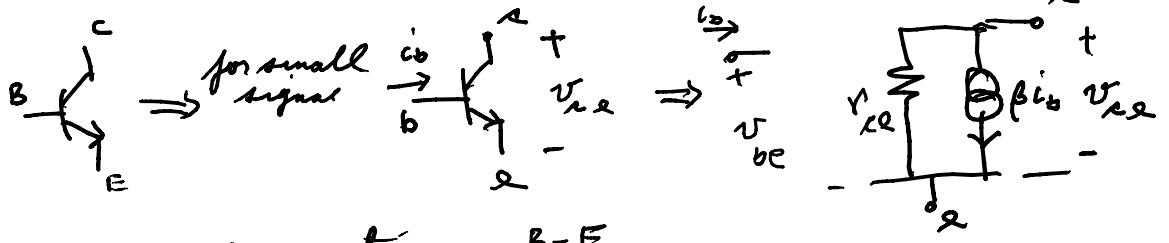
$i_C - I_C = i_c \Rightarrow i_c = \beta i_b + g_{CE} \cdot v_{ce}, v_{ce} = \frac{v_{ce}}{g_{CE}}$



we need information on B-E
am getting an equivalent
circuit for forward active region

a 2-port
appendix B

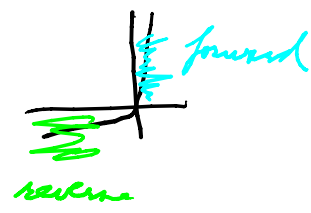here B-E \Rightarrow forward bias
 B-C \Rightarrow reverse bias




for BE: $-i_E = I_S (e^{v_{BE}/V_T} - 1)$
 $\approx I_S e^{v_{BE}/V_T}$

$-\frac{\partial i_E}{\partial v_{BE}} = \frac{I_S e^{v_{BE}/V_T}}{V_T} = \frac{-I_E}{V_T} = \frac{1}{\alpha} \frac{I_C}{V_T} \Rightarrow$ input conductance seen at the emitter


$-I_C = \alpha I_E = -\beta I_B \Rightarrow i_b = -\frac{\alpha}{\beta} \cdot i_c = -(1+\alpha) i_c$
 $-i_c = \alpha i_E = -\beta i_B = \frac{1}{\alpha} \frac{I_C}{V_T} \cdot (1+\alpha) \cdot v_{be}$

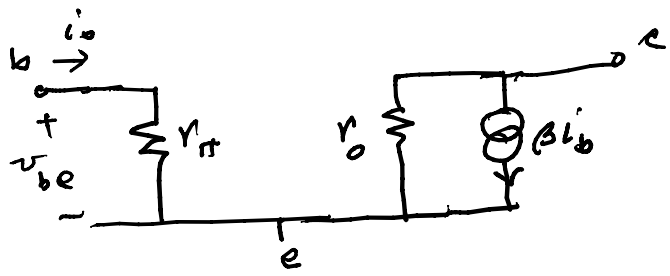$\beta = \frac{\alpha}{\alpha+1} \Rightarrow \frac{1}{\beta} \cdot \frac{I_C}{V_T} \cdot v_{be} \Rightarrow g_{be} = \frac{1}{\beta} \cdot \frac{I_C}{V_T} = g_{\pi}$
 $r_{\pi} = \frac{1}{g_{\pi}} = \frac{V_T}{I_C/\beta}$



$\beta \cdot i_b = \beta \cdot g_{\pi} \cdot v_{be} = \frac{I_C}{V_T} \cdot v_{be}$


see p.457 of text

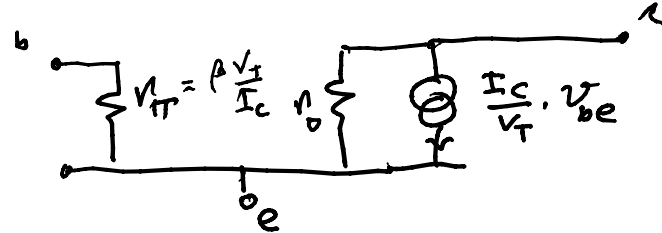

= π equivalent circuit

\therefore given a bias point Q we know the equivalent circuit if we can find r_o

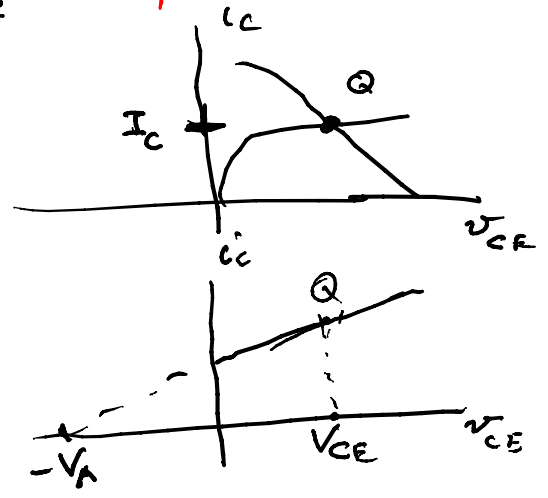$g_o = \frac{\partial I_C}{\partial v_{CE}} = \frac{I_C - 0}{(V_{CE} - (-V_A))}$
 $\approx \frac{I_C}{V_A}$





\therefore knowing the bias I_C & r_o since β & V_A ($\& V_T = \frac{kT}{q}$)

we know the small signal equivalent circuit of a BJT.

To use need to bias

B-E forward
B-C reverse

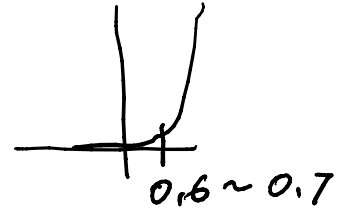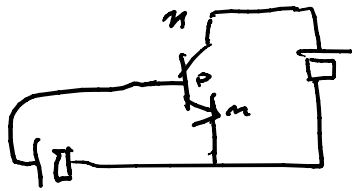

not easy to do with just one battery

For MOS - main lower

