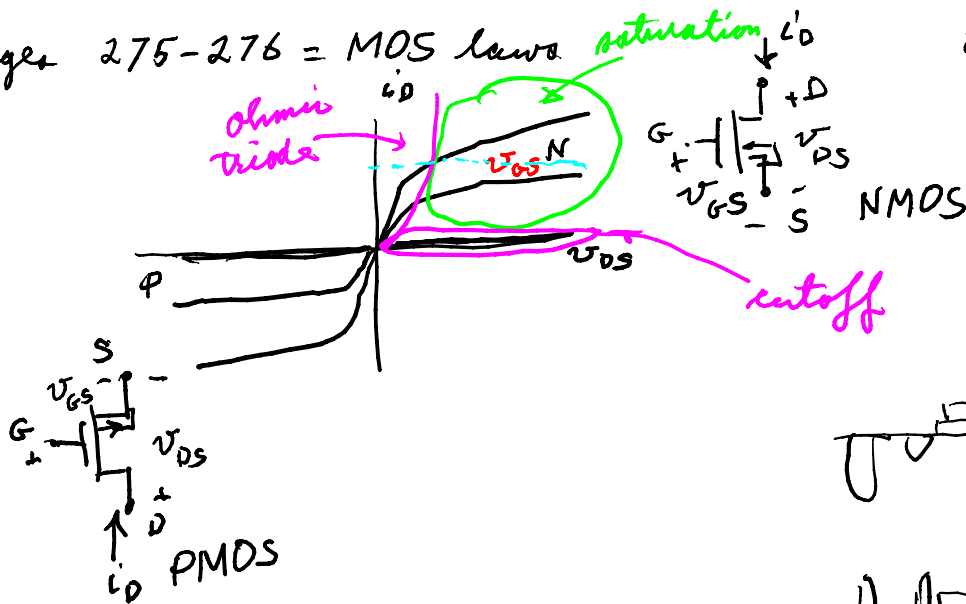


Pages 275-276 = MOS laws

EE 303H
02/10/09




$$i_D = \frac{K_P W}{2 L} \begin{cases} 0 & \text{cutoff; } v_{GS} < V_{T0} \\ (v_{GS} - V_{T0})^2 (1 + \lambda v_{DS}) & \text{saturation; } v_{DS} \geq v_{GS} - V_{T0} \\ 2(v_{GS} - V_{T0})v_{DS} - v_{DS}^2 (1 + \lambda v_{DS}) & \text{ohmic; } v_{DS} \leq v_{GS} - V_{T0} \end{cases}$$

note if v_{DS} is very small $i_D = \left\{ \frac{K_P W}{L} (v_{GS} - V_{T0}) \right\} \cdot v_{DS}$

$$\left(\frac{K_P W}{L} \right) R = \frac{1}{v_{GS} - V_{T0}}$$


in saturation region

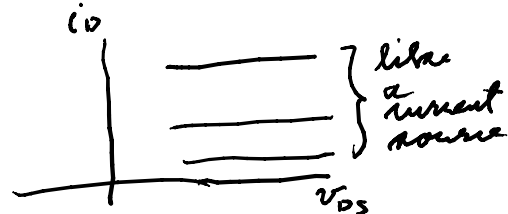
$$i_D = \left(\frac{K_P W}{2 L} \right) (v_{GS} - V_{T0})^2 \quad \text{independent of } v_{DS}$$



$\lambda = \text{LAMBDA}$

actually has an Early effect

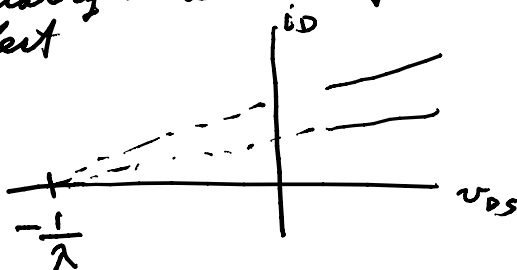

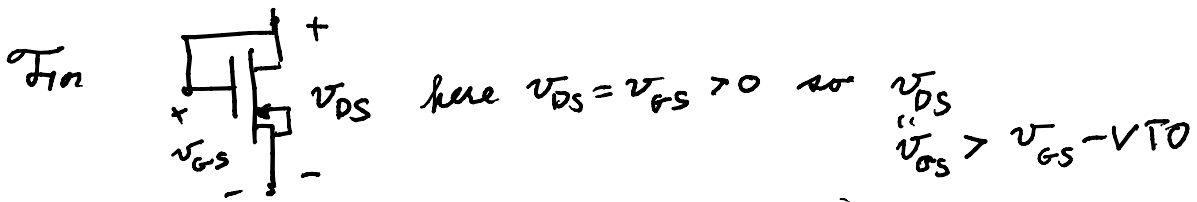


$$i_D \approx \frac{K_P \cdot W}{2 \cdot L} \cdot (V_{DS} - V_{TO})^2 \text{ if } V_{DS} > V_{TO}$$

if $V_{TO} > 0$
(true enhancement mode NMOS)



Example of use:

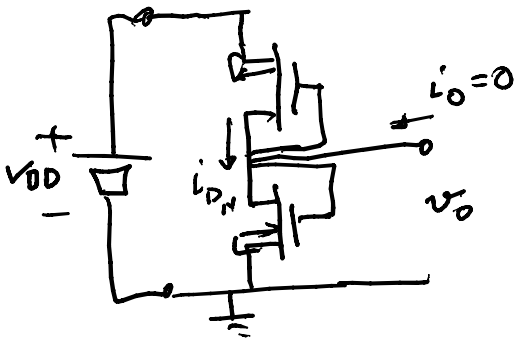

$$i_{Dn} = \left(\frac{K_P W}{2 L} \right)_n (V_{DD} - V_O - V_{TO_n})^2$$


$$= -i_{Dp} = \left(\frac{K_P W}{2 L} \right)_p (V_{DD} - V_O + V_{TO_p})^2$$

solve for $V_O \Rightarrow V_O - V_{TO_n} = \sqrt{\frac{(K_P W/L)_p}{(K_P W/L)_n}} (V_{DD} - V_O + V_{TO_p})$

$$\left(1 + \sqrt{\frac{(K_P)_p (W/L)_p}{(K_P)_n (W/L)_n}} \right) V_O = V_{TO_n} + \sqrt{\frac{(K_P)_p (W/L)_p}{(K_P)_n (W/L)_n}} (V_{DD} + V_{TO_p})$$


or if know V_O desired
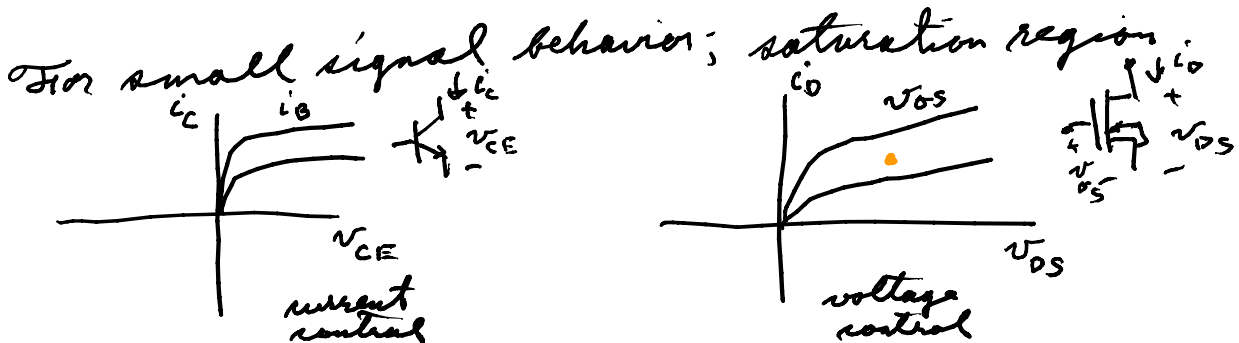
$$\frac{(W/L)_n}{(W/L)_p} = \frac{(V_{DD} - V_O + V_{TO_p})^2}{(V_O - V_{TO_n})^2}$$



$$i_D = I_D + \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q (v_{GS} - V_{GS}) + \left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q (v_{DS} - V_{DS}) + \dots$$

$$(i_D - I_D) = i_d = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_Q v_{gs} + \left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q v_{ds} = g_m v_{gs} + g_o v_{ds}$$

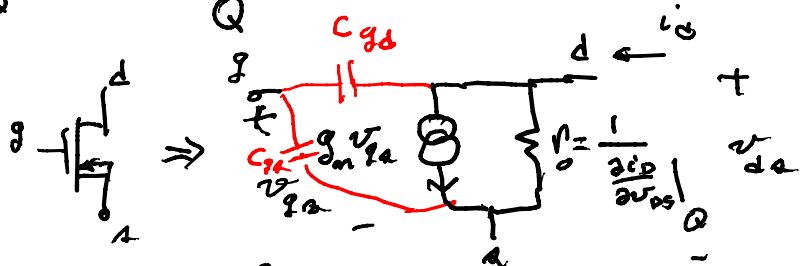

here $\frac{\partial i_D}{\partial v_{GS}} = \frac{\partial}{\partial v_{GS}} \left(\frac{K_P W}{2 L} (v_{GS} - V_{TO})^2 (1 + \lambda v_{DS}) \right)$



$$= \left. \frac{2 i_D}{(v_{GS} - V_{TO})} \right|_Q = \frac{2 I_D}{V_{GS} - V_{TO}} = g_m$$

$$g_o = \frac{1}{r_o} = \left. \frac{\partial i_D}{\partial v_{DS}} \right|_Q = \frac{\partial}{\partial v_{DS}} \left(\frac{K_P W}{2 L} (v_{GS} - V_{TO})^2 (1 + \lambda v_{DS}) \right)$$

$$= \lambda \left. \frac{i_D}{1 + \lambda v_{DS}} \right|_Q = \lambda \frac{I_D}{1 + \lambda V_{DS}} \approx 2 I_D$$

$R_L = \frac{3}{22.5} \text{ M}\Omega$

v_o bias

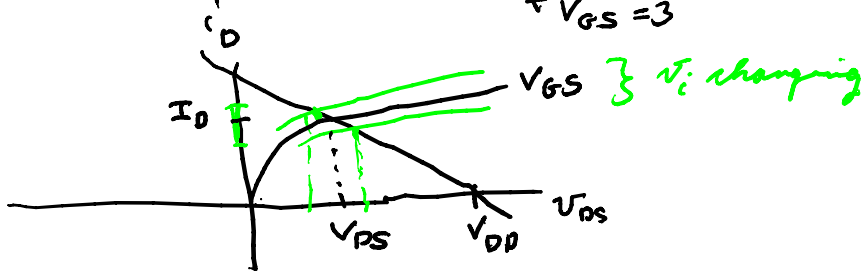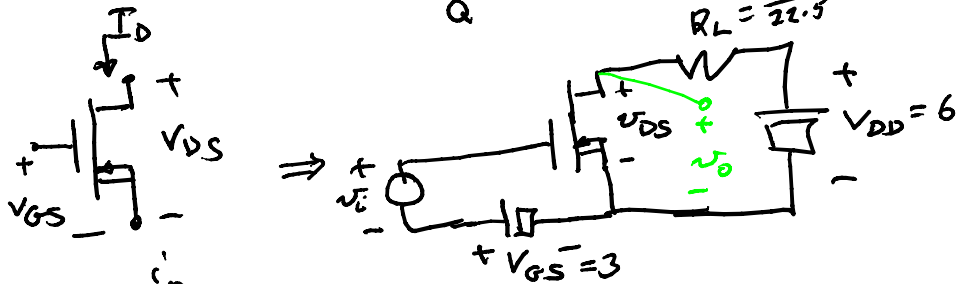

assume: $V_{GS} = 3V$, $V_{TO} = 1.5V$, $K_P = 20 \times 10^{-6} \text{ A/V}^2$
 $\lambda = 10 \text{ m/V}$, $W = 100\mu$, $L = 10\mu$, $V_{DD} = 6$


$$I_D \approx \frac{K_P W}{2 L} (V_{GS} - V_{TO})^2$$

if in saturation

$$= \frac{20 \times 10^{-6}}{2} \cdot \frac{100 \times 10^{-6}}{10 \times 10^{-6}} (3 - 1.5)^2 = 10 \times 10^{-6} \times 10 \times 2.25 \text{ A}$$

$$= 10^{-4} \times 2.25 = 0.0225 \text{ mA} = 22.5 \mu\text{A}$$

$$\frac{1.5}{2.25} = \frac{7.5}{15}$$

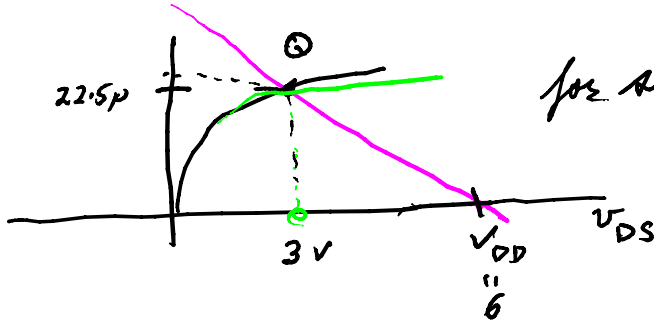

for saturation need $V_{DS} > \underbrace{V_{GS} - V_{TO}}_{3 - 1.5} = 1.5$

$$G_L = \frac{22.5 \times 10^{-6}}{6 - 3} = -\text{slope load line}$$

$$= \frac{22.5 \times 10^{-6}}{3} \Rightarrow R_L = \frac{3}{22.5} \text{ Meg } \Omega$$