
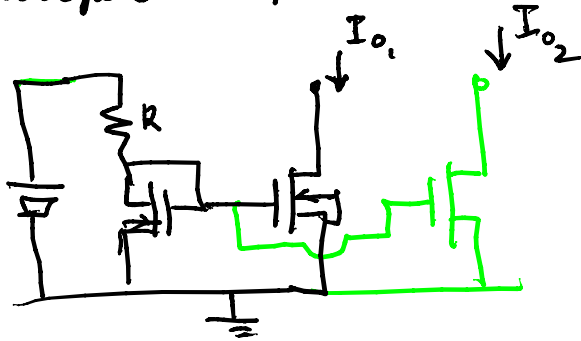


For multiple output


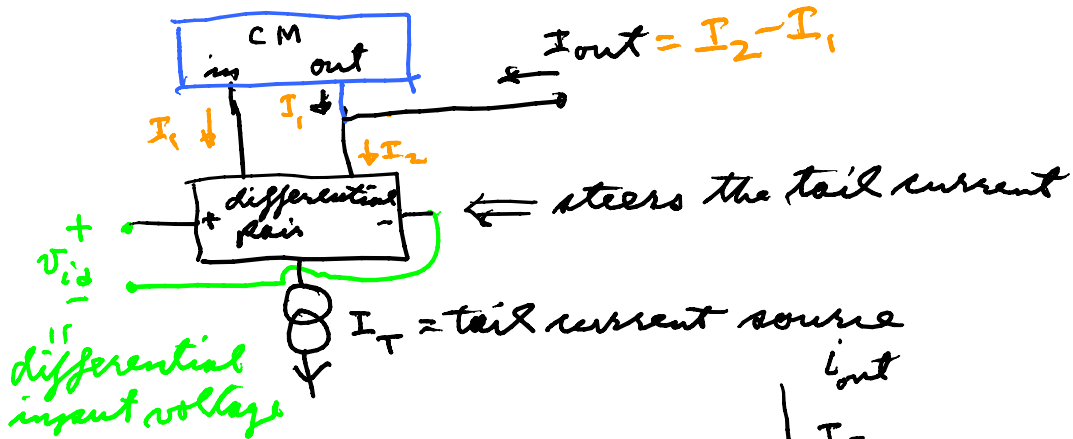


Use these in OTA's ; OTA = operational transconductor amplifiers
= VCCS

use differential pairs
current & current mirrors



For the BJT differential pair:

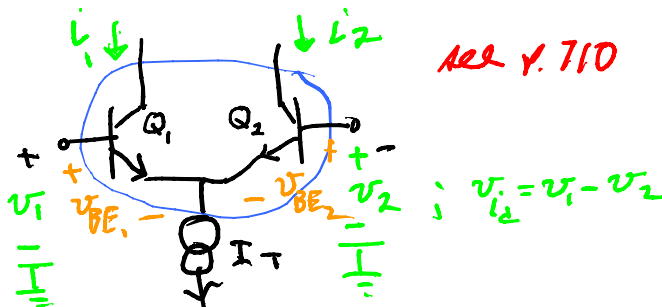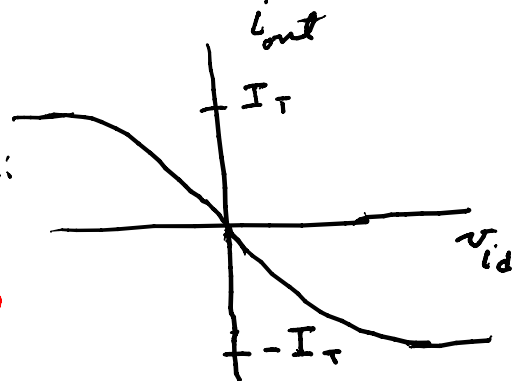

see p. 710

by KCL: ignore base current
 $i_1 + i_2 - I_T = 0$

for an OTA: $i_o = i_2 - i_1$

$$(1) \Rightarrow I_T = i_1 + i_2 = \frac{i_1 + i_2}{\alpha}$$

$$(2) \quad i_o = i_2 - i_1$$

as emitter

derive i_o vs $v_{id} \Rightarrow i_o = -\alpha I_T \tanh(v_{id}/2V_T)$ end result

$$g_m = \left. \frac{di_o}{dv_{id}} \right|_{v_{id}=0} = \text{small signal gain}$$

add (1)+(2): $2i_2 = I_T + i_o$

subtract (1)-(2) $2i_1 = I_T - i_o$

for Q₁ $\Rightarrow i_{E1} = I_S e^{v_{BE1}/V_T}$; $i_{E2} = I_S e^{v_{BE2}/V_T}$ (3), (4)

$v_1 - v_2 + v_{BE2} - v_{BE1} = 0$ by KVL

$v_{id} = v_{BE1} - v_{BE2} \Rightarrow v_{BE2} = v_{BE1} - v_{id}$ (5)

$i_{C1} = \alpha i_{E1} = \alpha I_S e^{v_{BE1}/V_T}$, $i_{C2} = \alpha i_{E2} = \alpha I_S e^{(v_{BE1} - v_{id})/V_T}$
 $= i_1$ " i_2

ratio $\frac{i_o}{I_T} = \frac{i_2 - i_1}{i_2 + i_1} = \frac{\alpha I_S e^{\frac{v_{BE1}}{V_T} - \frac{v_{id}}{V_T}} - \alpha I_S e^{\frac{v_{BE1}}{V_T}}}{\alpha I_S e^{\frac{v_{BE1}}{V_T} - \frac{v_{id}}{V_T}} + \alpha I_S e^{\frac{v_{BE1}}{V_T}}}$
 $= \frac{e^{-v_{id}/V_T} - 1}{e^{v_{id}/V_T} + 1} = -\frac{e^{-v_{id}/2V_T} (e^{v_{id}/2V_T} - e^{-v_{id}/2V_T})}{e^{-v_{id}/2V_T} (e^{v_{id}/2V_T} + e^{-v_{id}/2V_T})}$
 $= -\tanh\left(\frac{v_{id}}{2V_T}\right)$

$\Rightarrow i_o = -I_T \tanh(v_{id}/2V_T)$ as predicted out of α

$\Rightarrow \frac{1}{\alpha} \Rightarrow i_o = -\alpha I_T \tanh(v_{id}/2V_T)$

as have to supply base current