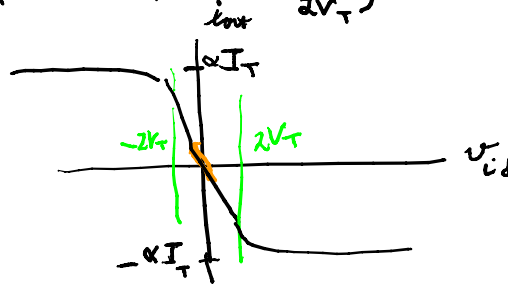


BJT OTA  
*from last time*

$$i_{out} = -\alpha I_T \tanh\left(\frac{v_{id}}{2V_T}\right)$$



$$\begin{aligned} \frac{di_{out}}{dv_{id}} &\approx G_m \\ &= -\alpha I_T \frac{d\left(\tanh\left(\frac{v_{id}}{2V_T}\right)\right)}{dv_{id}} \\ &= -\alpha I_T \left(\frac{1}{2V_T}\right) \left[1 - \tanh^2\left(\frac{v_{id}}{2V_T}\right)\right] \end{aligned}$$

$$\begin{aligned} \tanh x &= \frac{\sinh x}{\cosh x} \\ &= \frac{e^x - e^{-x}}{e^x + e^{-x}} \end{aligned}$$

$$G_m = -\frac{\alpha}{2} \frac{I_T}{V_T} \left(1 - \tanh^2\left(\frac{v_{id}}{2V_T}\right)\right)$$


$$\begin{aligned} \frac{d \tanh x}{dx} &= \frac{e^x - (-e^{-x})}{e^x + e^{-x}} - \frac{(e^x - e^{-x})(e^x + e^{-x})}{(e^x + e^{-x})^2} \\ &= 1 - \frac{e^x - e^{-x}}{e^x + e^{-x}} = 1 - \tanh x \end{aligned}$$

$\Rightarrow$  @  $v_{id} = 0 = -\alpha I_T / 2V_T$   
valid for linear region  
which is small input  $v_{id}$   
 $-2V_T < v_{id} < 2V_T$

$$V_T = 0.026V @ \text{room Temp}$$

MOS OTA via differential pair

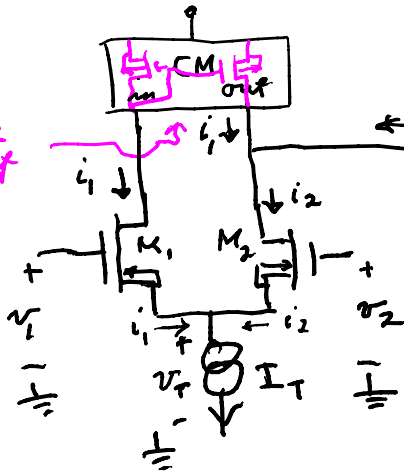
$M_1, M_2$   
not different  
transistor  
loads



$$i_0 + i_1 - i_2 = 0 \text{ KCL}$$

$$i_0 = i_2 - i_1 \quad \& \quad I_T = i_1 + i_2$$

$$v_{id} = v_1 - v_2$$

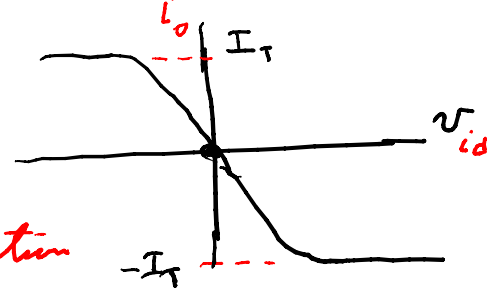

1)  $i_0 = i_2 - i_1$       3)  $v_{id} = v_1 - v_2$

2)  $I_T = i_2 + i_1$       *assume  $M_1 = M_2$  in saturation*

$$4) i_1 = \frac{K_P W}{2 L} (v_{GS1} - V_{T0})^2$$

$$5) i_2 = \frac{K_P W}{2 L} (v_{GS2} - V_{T0})^2$$

6)  $v_{GS1} = v_1 - V_T$

7)  $v_{GS2} = v_2 - V_T$

$$8) v_{GS_1} - v_{GS_2} = v_1 - v_2 = v_{id}$$

$$9) \frac{\sqrt{i_1} - \sqrt{i_2}}{\sqrt{\frac{K_P W}{2L}}} = (v_{GS_1} - V_{TO}) - (v_{GS_2} - V_{TO}) = v_{GS_1} - v_{GS_2} = v_{id}$$

but  $i_2 = i_0 + i_1$  from (1)  $\Rightarrow$  9)

$$10) \sqrt{i_1} - \sqrt{i_0 + i_1} = \sqrt{\frac{K_P W}{2L}} v_{id} \Rightarrow \text{square this}$$

$$i_1 - 2\sqrt{i_0 + i_1} \sqrt{i_1} + i_0 + i_1 = \frac{K_P W}{2L} v_{id}^2$$

square again

$$4(i_0 + i_1)i_1 = \left(\frac{K_P W}{2L} v_{id}\right)^2$$

instead square 9):  $\underbrace{i_1 + i_2}_{I_T} - 2\sqrt{i_1 i_2} = \left(\frac{K_P W}{2L}\right) v_{id}^2$

$i_2 = i_0 + i_1$

$$11) I_T - \left(\frac{K_P W}{2L}\right) v_{id}^2 = 2\sqrt{i_1 i_0 + i_1^2}$$

square gives a quadratic in  $i_1$

$$12) i_1^2 + i_0 i_1 - \frac{1}{4} \left( I_T - \left(\frac{K_P W}{2L}\right) v_{id}^2 \right)^2 = 0$$

$$13) i_1 = -\frac{i_0}{2} \pm \frac{1}{2} \sqrt{i_0^2 + \left( I_T - \left(\frac{K_P W}{2L}\right) v_{id}^2 \right)^2}$$

$$14) i_2 = i_0 + i_1 = +\frac{i_0}{2} \pm \frac{1}{2} \sqrt{i_0^2 + \left( I_T - \left(\frac{K_P W}{2L}\right) v_{id}^2 \right)^2}$$

$\therefore i_0 = i_2 - i_1 = \text{check above} \Rightarrow \text{to } I_T = i_1 + i_2$

$$\Rightarrow 15) I_T = \pm \frac{1}{2} \times 2 \sqrt{i_0^2 + \left( I_T - \left(\frac{K_P W}{2L}\right) v_{id}^2 \right)^2}$$

square again


$$16) I_T^2 = i_0^2 + \left( I_T - 2\left(\frac{K_P W}{2L}\right) v_{id}^2 + \left(\frac{K_P W}{2L}\right)^2 v_{id}^4 \right)^2$$

$$17) i_0 = \pm \sqrt{-\left(\frac{K_P W}{2L} v_{id}^2\right) \left( \left(\frac{K_P W}{2L} v_{id}^2\right) - 2I_T \right)}$$

$$= -v_{id} \sqrt{\left(\frac{K_P W}{2L}\right) (2I_T - \left(\frac{K_P W}{2L}\right) v_{id}^2)}$$

find  $v_{id}$  to give  $i_0 = \pm I_T$
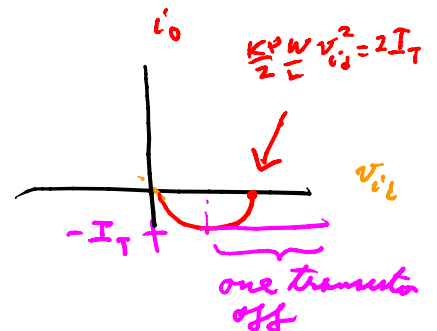
$$I_T^2 = -x^2(x^2 - 2I_T) \text{ where } x = \frac{K_P W}{2L} v_{id}^2$$




$$x^4 - 2I_T x^2 + I_T^2 = 0 \Rightarrow x^2 = I_T \pm \frac{1}{2} \sqrt{4I_T^2 - 4I_T^2}$$

$$\Rightarrow x^2 = I_T \Rightarrow x = \pm \sqrt{I_T}$$

(as  $x$  is real so rule out - sign)
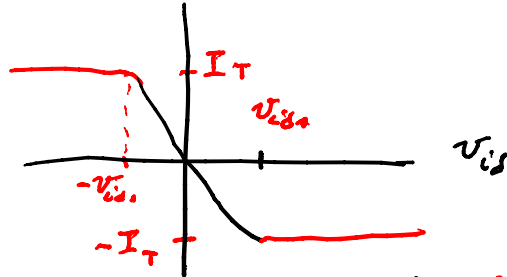
$$\Rightarrow v_{ic_s} = \pm \sqrt{\frac{2L}{WKP}} \sqrt{I_T}$$




To find  $G_m$ :

$$\frac{d i_o}{d v_{ic}} \stackrel{(17)}{=} \frac{d}{d x} \left( \pm \sqrt{x^2(x^2 - 2I_T)} \right) \cdot \frac{d x}{d v_{ic}} ; x^2 = \frac{KPW}{2L} v_{ic}^2$$

$$= \pm \frac{1}{\sqrt{x^2(x^2 - 2I_T)}} \cdot (4x^3 + 4xI_T) \cdot \frac{1}{2} \cdot \sqrt{\frac{KPW}{2L}} \quad (\text{note @ } x=0 \text{ this is } 0/0 \Rightarrow \neq \infty \text{ or } 0)$$
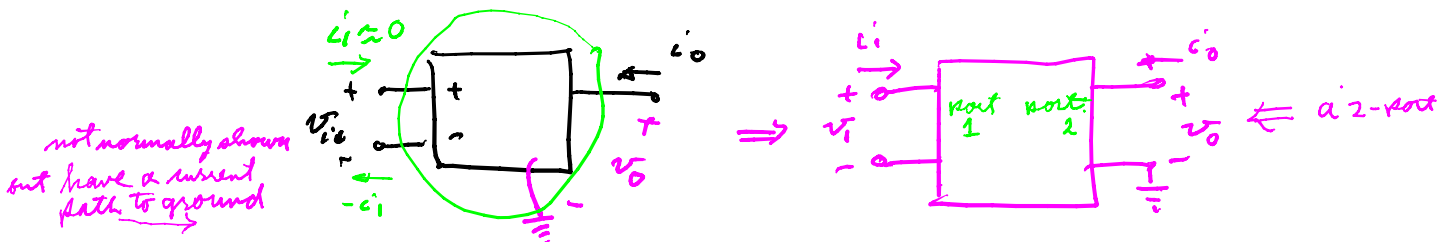
$$= \pm \frac{-4x^2 + 4I_T}{\sqrt{x^2 + 2I_T}} \cdot \sqrt{\frac{KPW}{2L}} = -4 \sqrt{\frac{KPW}{2L}} \left( \frac{I_T - (\frac{KPW}{2L}) v_{ic}^2}{\sqrt{2I_T - (\frac{KPW}{2L}) v_{ic}^2}} \right) \Rightarrow -2 \sqrt{KP \left( \frac{W}{L} \right) I_T} \quad v_{ic} = 0$$



Means around different loading of  $M_1$  &  $M_2$

