


$$\Rightarrow i = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}, v = \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$i = Y v \Rightarrow \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}; Y \Rightarrow 2 \times 2 \text{ admittance matrix}$$

$$i_1 = y_{11} v_1 + y_{12} v_2$$

$$i_2 = y_{21} v_1 + y_{22} v_2$$


describes a linear circuit

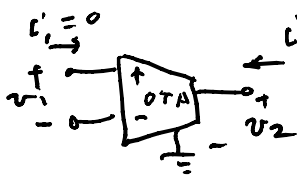


$$i_1 = 0 \cdot v_1 + 0 \cdot v_2$$

$$i_2 = G_m v_1 + 0 \cdot v_2$$
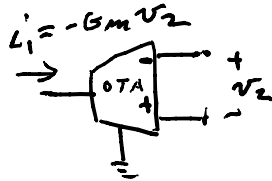
$$\Rightarrow Y_{OTA} = \begin{bmatrix} 0 & 0 \\ G_m & 0 \end{bmatrix}$$


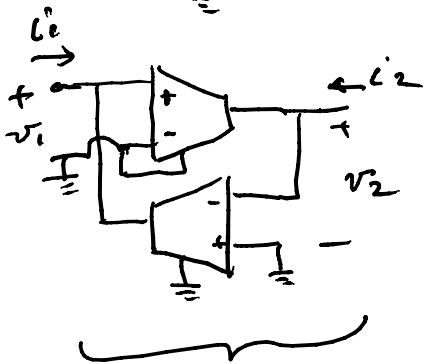
$$Y'_{OTA} = \begin{bmatrix} 0 & -G_m \\ 0 & 0 \end{bmatrix} = Y_{OTA}^{Transpose}$$




here v 's are the same for OTA & OTA' & the currents add

$$Y_{OTA} v + Y'_{OTA} v = i'$$

$$i = (Y_{OTA} + Y'_{OTA}) v$$

$$Y = \begin{bmatrix} 0 & -G_m \\ G_m & 0 \end{bmatrix} = -Y^T = \text{transpose} \Rightarrow \text{a gyrator}$$

is skew symmetric

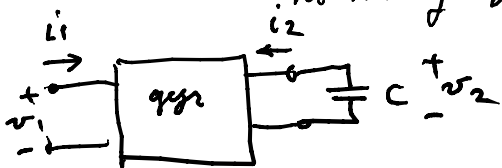


$$1) i_2 = -AC v_2 = v_1 G_m + 0 \cdot v_2$$

$$2) i_1 = -G_m v_2 \Rightarrow v_2 = -\frac{1}{G_m} i_1$$

$$\text{from 1) } v_1 = -\frac{AC}{G_m} v_2 = -\frac{AC}{G_m} \cdot \left(-\frac{1}{G_m}\right) i_1$$

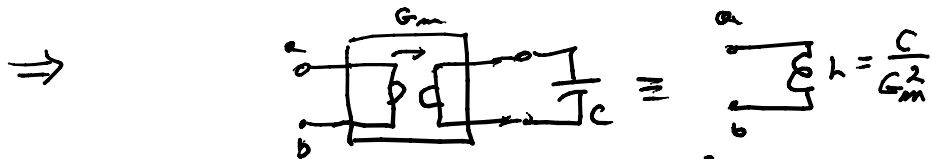
$$v_1 = \left(\frac{AC}{G_m^2}\right) i_1$$



if $C = 1 \text{ pF}$, $G_m = \frac{1}{10^3} \text{ S} = 10^{-3} \text{ S} \Rightarrow L = \frac{10^6}{\frac{1}{10^3} \cdot 10^{-6}} = 1 \text{ H}$

will 12 transistors for 2 OTA + 4 for $I_T = 16$ transistors & 1 cap.

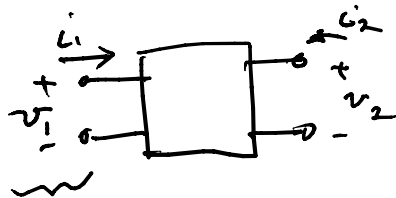⇒ a large inductor but not for large power.



$P_{in1} = v_1(t) \cdot i_1(t)$

$P_{in2} = v_2(t) \cdot i_2(t)$

$P_m(t) = v_1(t) \cdot i_1(t) + v_2(t) \cdot i_2(t)$
2-port
 $= v^T(t) i(t) = P_m(t)$

for the gyrator

$P_{in} = v^T \cdot i = v^T \cdot Y \cdot v(t)$

$= [v_1 \ v_2] \begin{bmatrix} 0 & -G_m \\ G_m & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$

$= [0 \cdot v_1 + G_m v_2, -G_m v_1 + 0 \cdot v_2] \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$


$= [G_m v_1 v_2 - G_m v_1 v_2]$

$= 0$


∴ signal power into a gyrator is zero } is lossless ($P_{in} = 0$)

[for operation we have to bias the transistor & have nonzero bias current in I_T]

For the BJT:

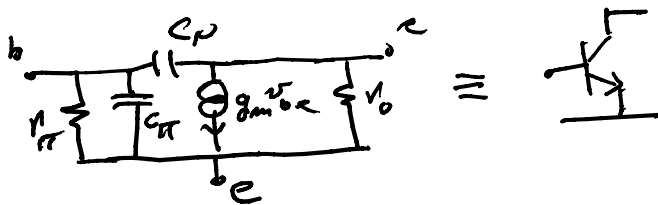

For Y 's in general $I = YV$

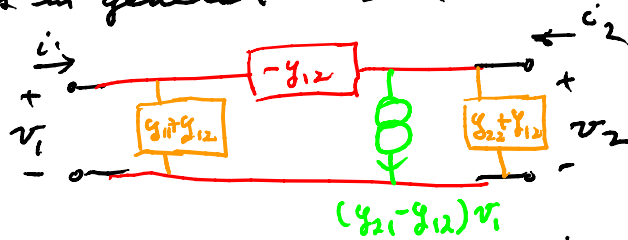

\Rightarrow equivalent circuit for a 2-port with a Y matrix

$$i_1 = y_{11}v_1 + y_{12}v_2$$

$$i_2 = y_{21}v_1 + y_{22}v_2$$

to find $y_{12} = \frac{i_1}{v_2} \Big|_{v_1=0}$ = a short

apply a v_2 & look for i_1



$$y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0}$$
 = a short




input admittance $y_{11} = \parallel$ of two 1-ports

for y_{21} : $i_2 = y_{21}v_1 + y_{22}v_2$

set $v_2 = 0$
by $v_2 = 0$

$$\Rightarrow \frac{i_2}{v_1} \Big|_{v_2=0} = y_{21}$$

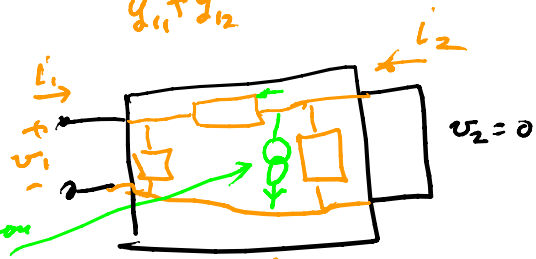

a correction

$$\text{gives } \frac{i_2}{v_1} = y_{12} + (y_{21} - y_{12})$$

a common description for 2-ports is the scattering matrix

$$\begin{bmatrix} v_1^i \\ v_2^i \end{bmatrix} = v^i$$

$$v^n = \begin{bmatrix} v_1^n \\ v_2^n \end{bmatrix}$$

$$2v^i = v + Z_0 i$$

$$2v^n = v - Z_0 i$$

usually normalize $Z_0 = 1$
 $Z_0 = \text{characteristic}$

$$\left. \begin{aligned} 2v^i &= v + i \\ 2v^n &= v - i \end{aligned} \right\} v^n = S \cdot v^i$$

