


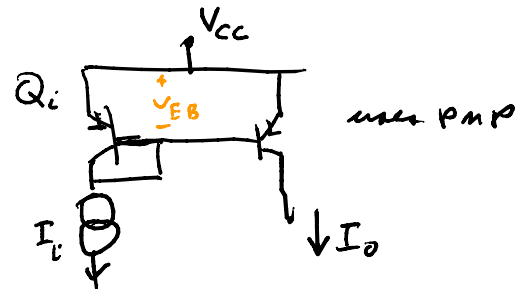
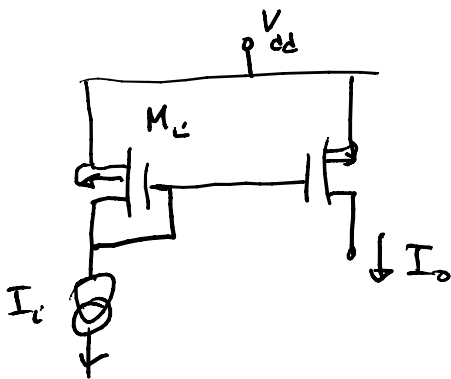
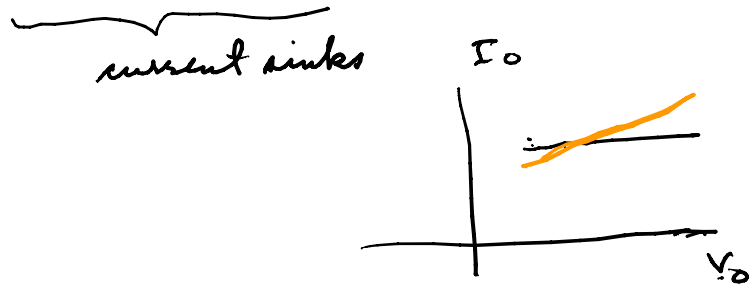
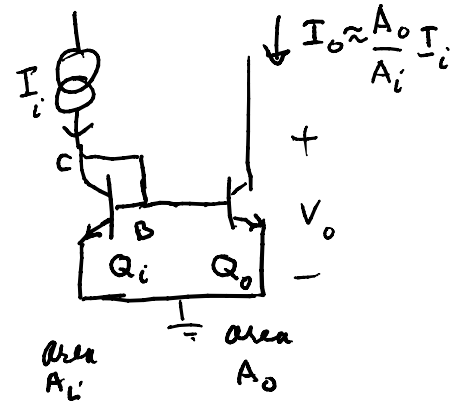
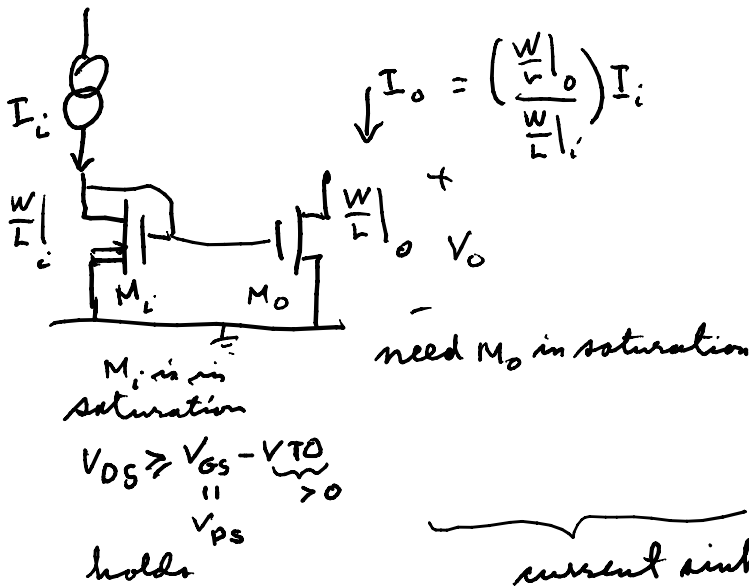
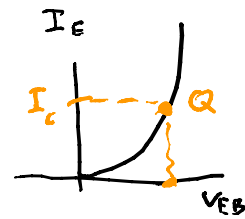
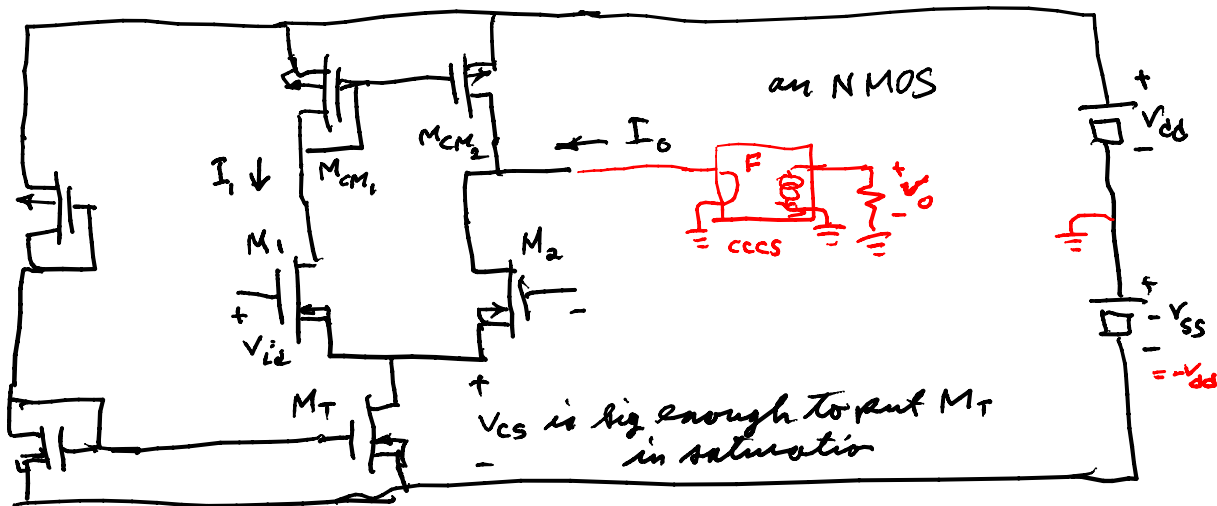


03/03/09
EE303

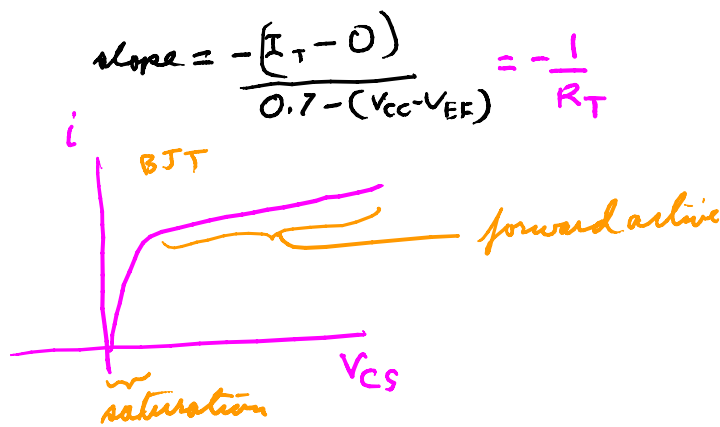


current source

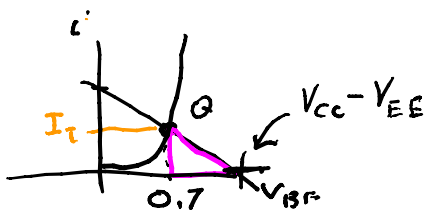


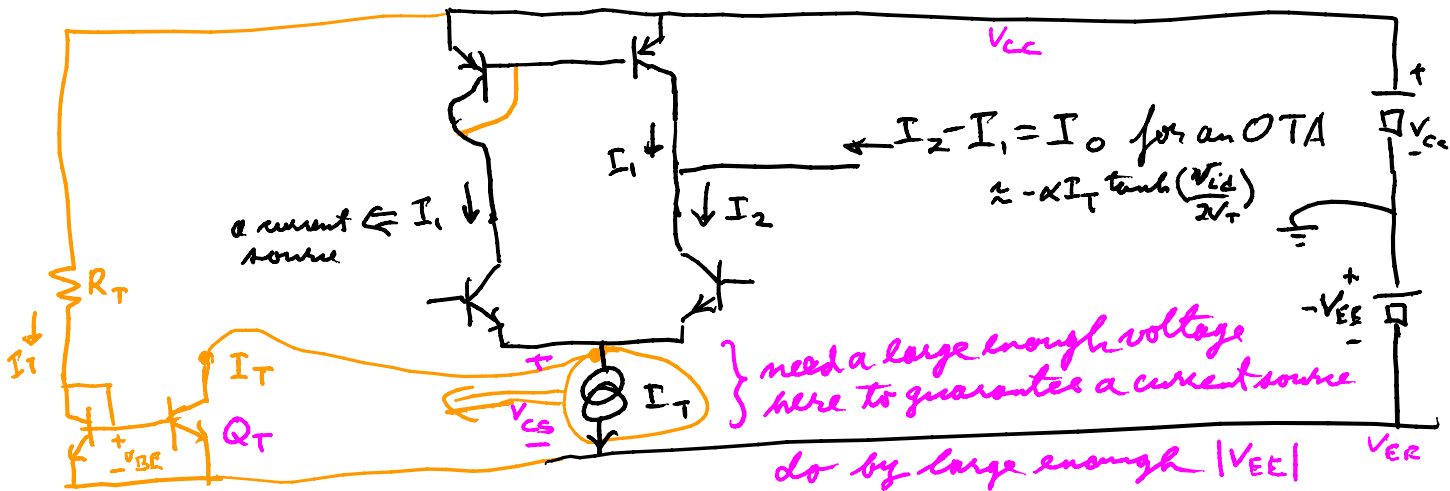

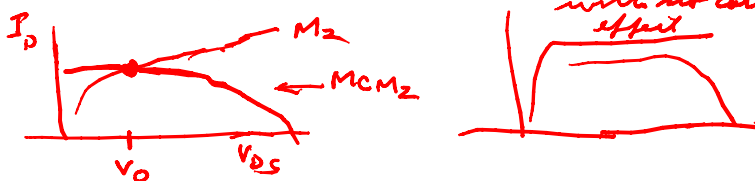
if $I_O = 0$ is held then not an OTA \Rightarrow goes to a VCVS
 here $-I_{D_{M_{CM2}}} = I_{D_{M_2}}$ by the Early effect a voltage is determined with no Early effect





2 PMOS OTA

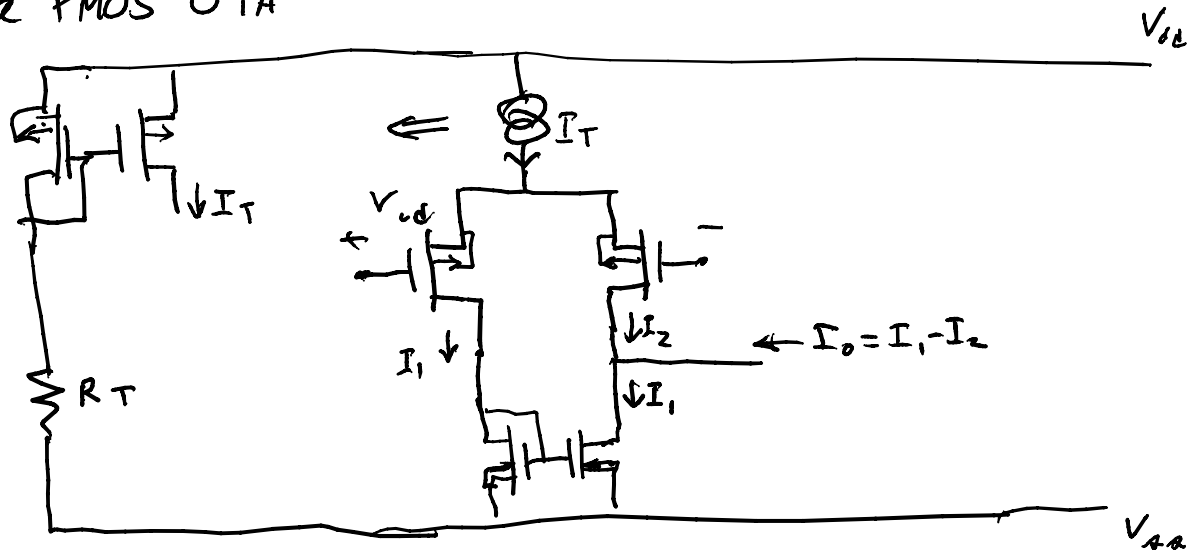

Better current mirrors:

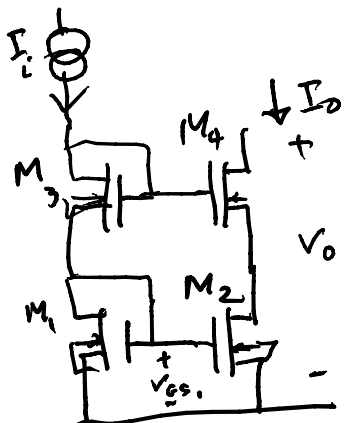


cascode current mirror

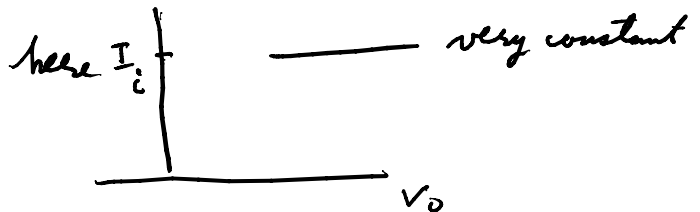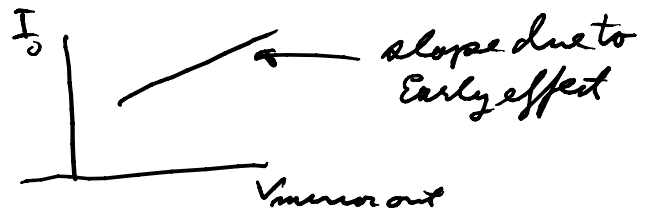


here M_4 absorbs variations in V_O so that M_2 has a constant V_{GS} which guarantees $I_O = I_C$

From BJT diff pair input

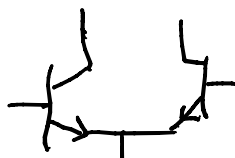

due to the base current we want to minimize the base current we use the Darlington connection

Darlington

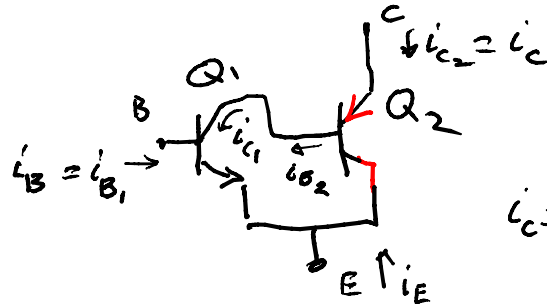

$$i_{c1} = \beta_1 i_{B1} = \beta_1 i_B$$

$$i_c = i_{c2} = \beta_2 i_{B2} = \beta_2 i_{c1}$$


$$= \beta_2 (\beta_1 i_B)$$

$$i_c = \beta_1 \beta_2 \cdot i_B$$

$$\beta = \beta_1 \beta_2$$

if $\beta_1 = \beta_2 = 100$
 $\beta = 10^4$

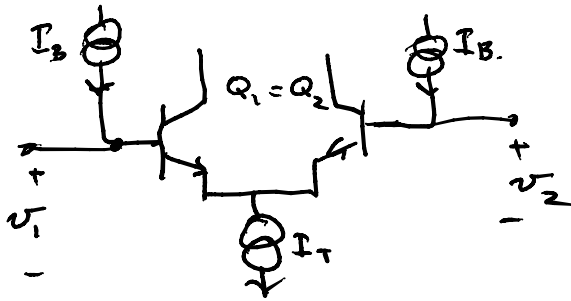For the BJT differential pair we need bias current for the input transistors.



$$v_{id} = v_1 - v_2$$