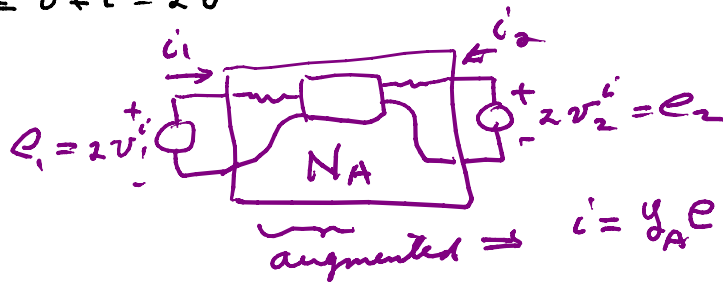


$$2v^n = 2 \begin{bmatrix} v_1^n \\ v_2^n \end{bmatrix} = \begin{bmatrix} v_1 - i_1 \\ v_2 - i_2 \end{bmatrix}, \quad 2 \begin{bmatrix} v_1^i \\ v_2^i \end{bmatrix} = \begin{bmatrix} v_1 + i_1 \\ v_2 + i_2 \end{bmatrix} = 2v^i$$

$$v^n = S v^i$$

a network analyzer measures these \$v^i, v^n\$

$$e = v + i = 2v^i$$




$$i = y_A e$$

$$v = e - i = e - y_A e = (1_2 - y_A) \cdot e$$


$$v - i = 2v^n = (1_2 - y_A) e - y_A e = (1_2 - 2y_A) e = (1_2 - 2y_A) \cdot 2v^i$$

$$v^n = S v^i = (1_2 - 2y_A) \cdot v^i \Rightarrow S = 1_2 - 2y_A$$

Ex:

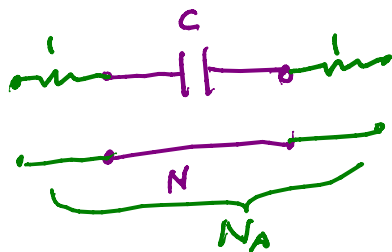

To find \$y_A\$

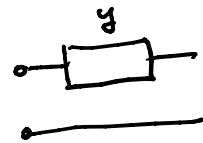


$$\text{here } \frac{2}{z} \cdot \frac{c}{2} \cdot y = \frac{1}{2} = \frac{1}{2 + \frac{1}{ca}} = \frac{ca}{2ca + 1}$$

$$Y_A = \begin{bmatrix} y & -y \\ -y & y \end{bmatrix} = \frac{ca}{2ca+1} \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} \quad \text{a singular matrix (no impedance matrix)}$$

$$S = I_2 - 2Y_A = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} - \frac{ca}{2ca+1} \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} = \begin{bmatrix} \frac{ca+1}{2ca+1} & \frac{+ca}{2ca+1} \\ \frac{ca}{2ca+1} & \frac{ca+1}{2ca+1} \end{bmatrix}$$

Circulator

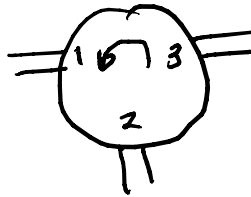

$$\begin{aligned} v_2^n &= v_1^i \\ v_3^n &= v_2^i \\ v_1^n &= v_3^i \end{aligned}$$


$$S = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \end{bmatrix}$$

$$\begin{aligned} v_{2l}^n &= A_2 v_{2l}^i \\ v_3^i &= v_{3l}^n = A_3 v_{3l}^i = A_3 v_3^n = A_3 v_2^i \\ v_{2l}^i &= v_{2l}^n = A_2 v_{2l}^i = A_2 v_2^n = A_2 v_1^i \end{aligned}$$

$l = \text{load}$ but $v_{2l}^i = v_2^n$ (see below)

$$v_1^n = S v_1^i$$
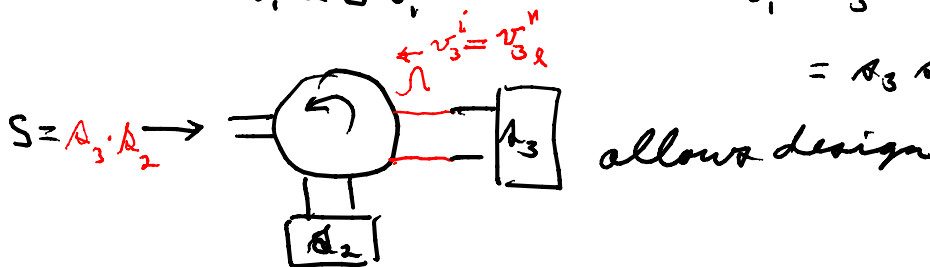
$$\begin{aligned} v_1^n &= v_3^i = A_3 v_2^i = A_3 \cdot A_2 v_2^n \\ &= A_3 A_2 v_1^i \Rightarrow S = A_3 \cdot A_2 \end{aligned}$$



$$\begin{aligned} 2v^i &= v + i = v + yv = (1+y)v \\ 2v^n &= v - i = v - yv = (1-y)v \end{aligned}$$

$$v^n = S v^i = ((1-y)v/2) = S(1+y)v/2$$

$$\Rightarrow S = \frac{1-y}{1+y}$$

$$\begin{aligned} \left[\begin{array}{c} \boxed{1} \\ \boxed{y} \end{array} \right] \quad y = ac \\ S = \frac{1-ac}{1+ac} \end{aligned}$$

$$S^T(-a) S(a) = I_2$$

↑ ↑
Hermiticity conjugate


$$S(a) = \frac{1}{S(-a)} \quad \text{here (lossless condition)}$$

average power in: $P(j\omega) = \text{Re } V^{T*} I$

$$= \frac{V^{T*} I + V^T I^*}{2} = \frac{V^{T*} I + I^{T*} V}{2}$$

$$= \frac{V^{T*} (Y(j\omega) V) + V^T Y^T(j\omega) V}{2}$$
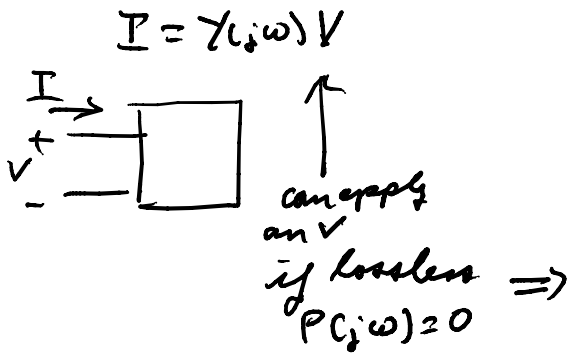
$$= \frac{V^{T*} (Y(j\omega) + Y^T(j\omega)) V}{2}$$



$$Y(j\omega) + Y^T(j\omega) = 0$$

$$\Rightarrow Y(j\omega) + Y^T(-j\omega) = 0 \quad \left. \begin{matrix} n \\ n \end{matrix} \right\} \text{real component}$$

$$\Rightarrow Y(s) + Y^T(-s) = 0 \text{ for } s = j\omega$$

analytic continuation $Y(s) = -Y^T(-s)$ for all $s, s = \sigma + j\omega$


but if have real elements have analytic functions

Ex: $\frac{1}{s} \quad y = cs, \quad y(-s) = -cs = -y(s)$

lossless condition

$$S = (I_n - Y)(I_n + Y) \Rightarrow \text{for lossless } S(-s)S(s) = I_n$$

oscillators

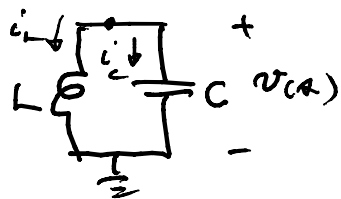

$$i_c(s) = sC \cdot v(s)$$

$$v(s) = sL \cdot i_L(s) \quad i_L = -i_c \text{ by KCL}$$

$$i_c(s) = sC v(s) = -\frac{v(s)}{sL}$$

$$\Rightarrow s^2 LC v(s) + v(s) = 0$$


$$LC \frac{d^2}{dt^2} v(t) + v(t) = 0 \quad \text{needs } v(0) \text{ and } v'(0)$$

has a different solution (for $t \rightarrow \infty$) with different initial.


note: e^{st} satisfies this differential equation for $-\infty < t < \infty$

$$s^2 LC e^{st} + e^{st} = 0 \Rightarrow s^2 LC + 1 = 0$$
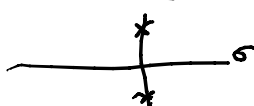
$$s^2 = -\frac{1}{LC} \Rightarrow s = \pm j \frac{1}{\sqrt{LC}} = \pm j\omega_0$$



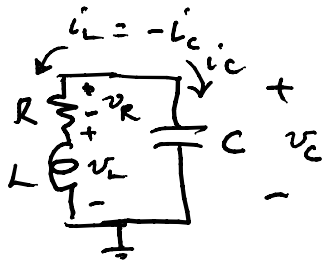interested in a structurally stable oscillator which this LC one is not; also due to losses in practice the oscillations die out



$$i_c = A C v_C$$

$$v_L = A L i_L, \quad v_R = R i_L = R(-i_c)$$

$$v_L = -A L \cdot A C v_C = v_C - v_R$$

$$= v_C + R A C v_C$$

$$(A^2 LC + R A C + 1) v_C = 0$$


$$\left(A^2 + \frac{R}{L} A + \frac{1}{LC}\right) \cdot v_C = 0 ; P(A) = A^2 + \frac{R}{L} A + \frac{1}{LC}$$

$$= A^2 + \frac{\omega_0}{Q} A + \omega_0^2$$

when $R=0 \Rightarrow$ lossless $\Rightarrow Q=\infty$

need to turn to electronic circuits to get $Q=\infty$

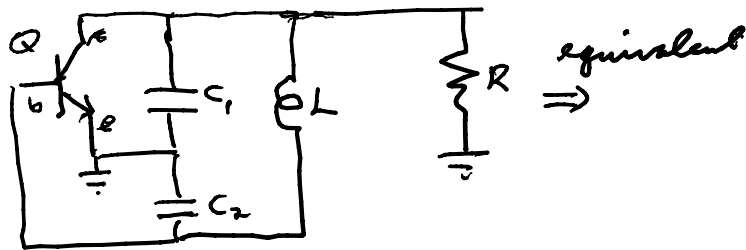- b. 1174 = RC phase shift oscillator \Rightarrow 3rd order to oscillate
- c. 1179 = Colpitts \Rightarrow also 3rd good for generating chaotic signals



- for exam
- load lines - diodes
- Q pts.
- BJT & MOS models
- OTA's & diff. eqs
- current mirrors