
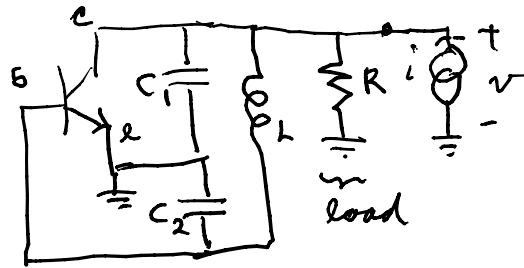


Colpitts

EE303
03/12/09

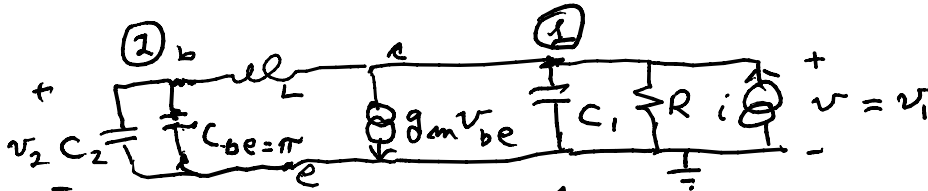

look at input impedance
then set $i=0$
 $v = Z_{in} \cdot i$ if $i=0$ & $v \neq 0$
then $Z_{in} = \infty$



node equations KCL

$$\textcircled{1}: 0 = i - Gv_1 - sC_1v_1 - g_m v_2 + \frac{1}{sL}(v_2 - v_1)$$

$$\textcircled{2}: 0 = -s\hat{C}_2 v_2 - \frac{1}{sL}(v_2 - v_1)$$

$$\begin{bmatrix} i \\ 0 \end{bmatrix} = \begin{bmatrix} G + sC_1 + \frac{1}{sL} & g_m - \frac{1}{sL} \\ -\frac{1}{sL} & s\hat{C}_2 + \frac{1}{sL} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$(s\hat{C}_2 + \frac{1}{sL})v_2 = \frac{1}{sL}v_1 \Rightarrow v_2 = \frac{1}{s^2L\hat{C}_2 + 1}v_1$$

$$i = \left[G + sC_1 + \frac{1}{sL} + (g_m - \frac{1}{sL}) \cdot \frac{1}{s^2L\hat{C}_2 + 1} \right] v_1$$

$$v = \frac{s^2L\hat{C}_2 + 1}{(s^2L\hat{C}_2 + 1)(G + sC_1 + \frac{1}{sL}) + g_m - \frac{1}{sL}} \cdot i$$

$$Z_{in}(s) = \frac{sL(s^2L\hat{C}_2 + 1)}{(s^2L\hat{C}_2 + 1)(s^2L\hat{C}_2 + 1) + g_m sL - 1} = \frac{N(s)}{D(s)}$$

seen at output of Colpitts

here s cancels numerator & denominator \Rightarrow zeros over poles

$$= \frac{sL(s^2L\hat{C}_2 + 1)}{s^4L^2\hat{C}_1\hat{C}_2 + s^3L^2\hat{C}_2G + s^2L\hat{C}_2 + s^2C_1L + sLG + 1 + g_msL - 1}$$

$$= \frac{L(s^2L\hat{C}_2 + 1)}{s^3L^2\hat{C}_1\hat{C}_2 + L^2\hat{C}_2G + L(\hat{C}_2 + C_1)s + L(G + g_m)}$$

as desire an oscillator; as $v \neq 0, i = 0 \Rightarrow$ denominator $\Rightarrow 0$ of $Z_{in}(s)$

then desire $D(j\omega) = 0$ ie $s = j\omega$

$$D(s) = LC_1\hat{C}_2 s^3 + L\hat{C}_2 G s^2 + (C_1 + \hat{C}_2) s + (G + g_m)$$


$$D(j\omega) = -j\omega^3 LC_1\hat{C}_2 - L\hat{C}_2 G \omega^2 + j\omega(C_1 + \hat{C}_2) + (G + g_m) = 0$$

$$= j\omega \underbrace{[-\omega^2 LC_1\hat{C}_2 + [C_1 + \hat{C}_2]]}_{=0} + \underbrace{[G + g_m - L\hat{C}_2 G \omega^2]}_{=0}$$

$\omega^2 = \frac{C_1 + \hat{C}_2}{LC_1\hat{C}_2} \Rightarrow$ this is the parallel combination of C 's resonating with L

$$G + g_m = L\hat{C}_2 G \omega^2 = G \frac{C_1 + \hat{C}_2}{C_1} \Rightarrow g_m = G \left[-1 + 1 + \frac{\hat{C}_2}{C_1} \right] = G \frac{\hat{C}_2}{C_1}$$

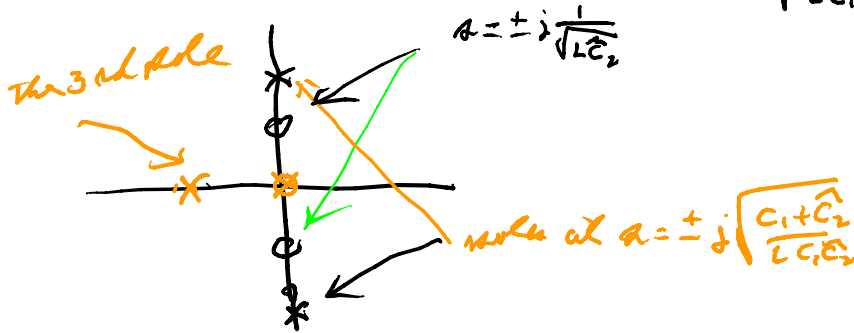now this will oscillate at $\omega_0 = 2\pi f = \sqrt{\frac{C_1 + \hat{C}_2}{LC_1\hat{C}_2}}$




For lossless: $Y(s) + Y(-s) = 0$ matrix

for a 1-port $y(s) = -y(-s)$

then also $\frac{1}{z(s)} = -\frac{1}{z(-s)}$ for $z(s) = \frac{1}{y(s)}$


$$\Rightarrow z(s) = -z(-s)$$

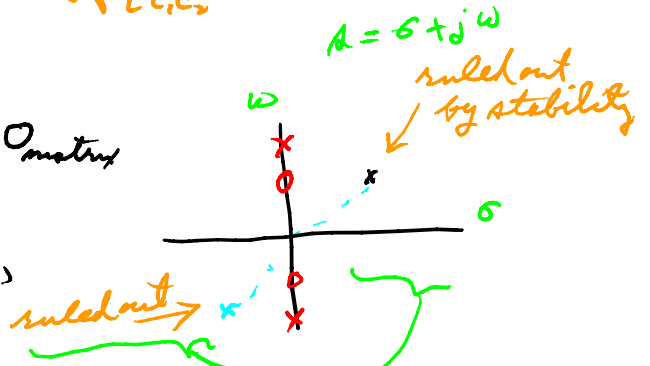


all are simple { requires poles on $j\omega$ axis

$$y(s) = \frac{k_1 s}{s^2 + \omega_1^2} + \frac{k_2 s}{s^2 + \omega_2^2} + \dots$$

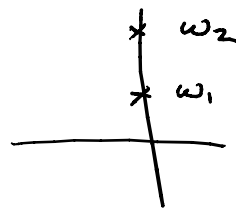allows the circuit to be tuned to several frequencies



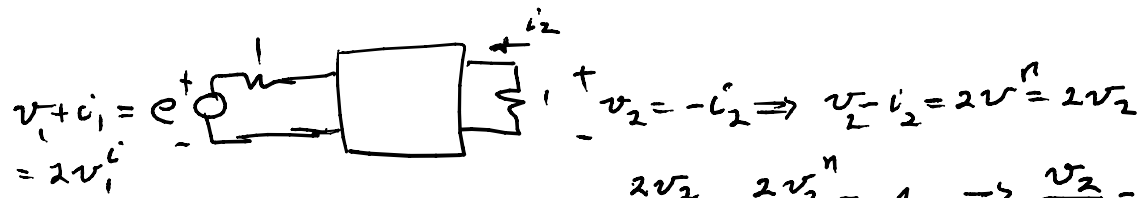

$$\frac{2v_2}{e} = \frac{2v_2^i}{2v_1^i} = A_{21} \Rightarrow \frac{v_2}{e} = \frac{A_{21}}{2}$$

\therefore for
 $v_2 = \frac{-g_m}{(1+g_{ii})(1+g_o)}$