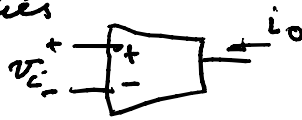


OTA = operational transconductance amplifiers



08/24/09  
EE303

v.728



small signal  $i_o = G_m v_i$

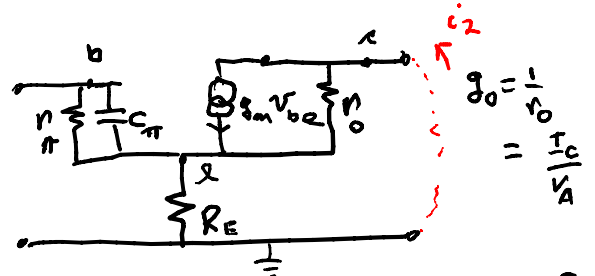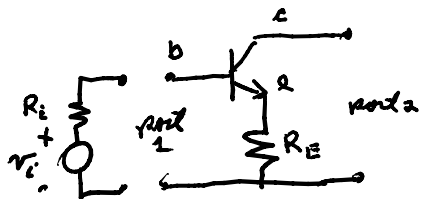Small signal behavior  $\Rightarrow$  linear behavior




desire  $Y$  for this  $\rightarrow$   $y_{11} = \frac{i_1}{v_1} \Big|_{v_2=0}$   
 $I = YV$

$$y_{\pi} = g_{\pi} + sC_{\pi}; \quad g_{\pi} = \frac{1}{r_{\pi}} = \frac{g_m}{\beta}; \quad g_m = \frac{I_C}{V_T}$$

$\Rightarrow i_1 = y_{\pi} v_{be} = G_E' (v_1 - v_{be}) - g_m v_{be}$

$V_T = 0.026$  @ Norm T

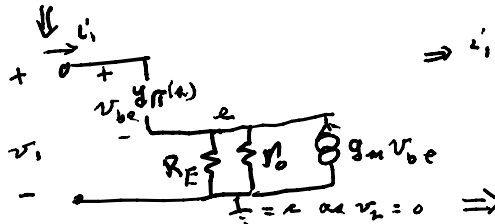let  $R_E' = \frac{1}{G_E + g_o} = \frac{1}{G_E'}$




$$i_1 = \frac{y_{\pi} \cdot G_E'}{y_{\pi} + g_m + G_E'} \cdot v_1 \quad (y_{\pi} + g_m + G_E') v_{be} = G_E' v_1$$

$$y_{11} = y_{input} \text{ when } v_2=0 \text{ port 2 shorted} = \frac{G_E' \cdot y_{\pi}}{y_{\pi} + g_m + G_E'} = \frac{G_E' (sC_{\pi} + g_{\pi})}{sC_{\pi} + (g_{\pi} + g_m + G_E')}$$

$$= \frac{G_E' (s + g_{\pi}/C_{\pi})}{s + (g_{\pi} + [g_m + G_E'])/C_{\pi}} = \frac{G_E' (s - s_0)}{s - s_p} \quad \omega \quad s = \sigma + j\omega$$

zeros:  $s_0 = -g_{\pi}/C_{\pi}$

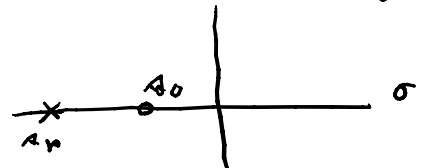
poles:  $s_p = -\frac{g_{\pi}}{C_{\pi}} - \frac{g_m + G_E'}{C_{\pi}}$



$(s - s_p) i_1 = G_E' (s - s_0) v_1 \Rightarrow$  if  $v_1 = 0$  we can have  $i_1 \neq 0$  if  $s = s_p$


$i_1 = I e^{s_p t}$  as look at  $s = \frac{d}{dt}; I = \text{const.}$

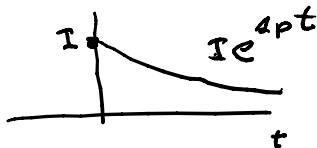$(s - s_p) I e^{s_p t} = 0 \Rightarrow \frac{d I e^{s_p t}}{dt} - s_p I e^{s_p t} = s_p (1 - 1) I e^{s_p t} = 0$



$$i_1 = y_{11} v_1 \Big|_{v_2=0} = \frac{G_E'(a-a_0)}{(a-a_0)} v_1 \Rightarrow (a-a_0) i_1 = G_E'(a-a_0) v_1$$

$$y_{21} = \frac{i_2}{v_1} \Big|_{v_2=0}$$

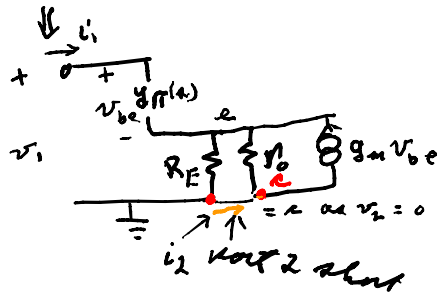

$$i_2 = g_m v_{be} + g_o (-[v_1 - v_{be}])$$

$$= -g_o v_1 + (g_m + g_o) v_{be}$$

but  $\Rightarrow (y_{\pi} + g_m + G_E') v_{be} = G_E' v_1$


$$\therefore i_2 = \left[ -g_o + \frac{[g_m + g_o] G_E'}{y_{\pi} + g_m + G_E'} \right] v_1$$

$$y_{21} = -g_o + \frac{[g_m + g_o] G_E' / C_{\pi}}{a + \frac{[g_{\pi} + g_m + G_E']}{C_{\pi}}}$$

has the same pole as  $y_{11}$

$$= -g_o \left[ \frac{a + \frac{g_{\pi} + g_m + G_E'}{C_{\pi}} + \left[ \frac{g_m}{g_o} + 1 \right] G_E' / C_{\pi}}{a + \frac{[g_{\pi} + g_m + G_E']}{C_{\pi}}} \right]$$

To use  $Y$

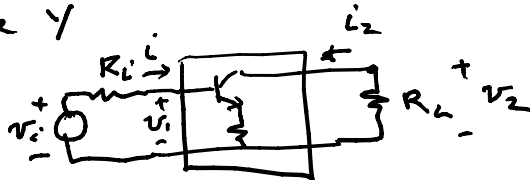

find  $v_2/v_1$

1)

$$i_1 = y_{11} v_1 + y_{12} v_2 = y_{11} [v_1 - R_i i_1] + y_{12} v_2$$

2)

$$-G_L v_2 = i_2 = y_{21} v_1 + y_{22} v_2 = y_{21} [v_1 - R_i i_1] + y_{22} v_2$$

$$1) \rightarrow i_1 \Rightarrow (1 + y_{11} R_i) i_1 = y_{11} v_1 + y_{12} v_2$$

$$i_1 = \frac{y_{11} v_1 + y_{12} v_2}{(1 + y_{11} R_i)}$$

$$-G_L v_2 - y_{22} v_2 = y_{21} v_1 - \frac{R_i}{1 + y_{11} R_i} y_{21} [y_{11} v_1 + y_{12} v_2]$$


$$-(G_L + y_{22} - \frac{R_i y_{12} y_{21}}{1 + y_{11} R_i}) v_2 = \left( y_{21} - \frac{R_i y_{21} y_{11}}{1 + y_{11} R_i} \right) v_1$$

$$\frac{v_2}{v_1} = \text{Voltage gain} = \frac{-(y_{21} + y_{21} y_{11} R_i - y_{12} y_{21} R_i)}{G_L + G_L R_i y_{11} + y_{22} + y_{11} y_{22} R_i - y_{12} y_{21} R_i} = \frac{-y_{21}}{G_L (1 + R_i y_{11}) + y_{22} + R_i \Delta Y}$$

where  $\Delta Y = \text{determinant of } Y$

another circuit with MOS

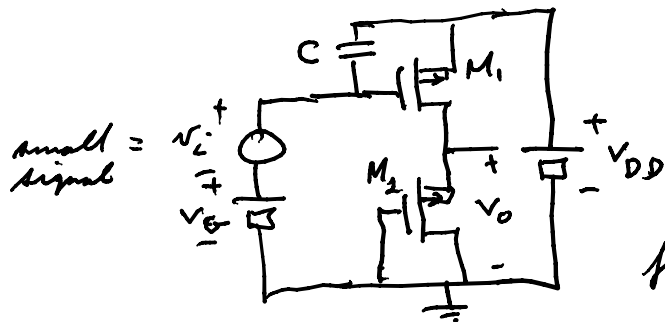assume bias so supply  $M_1$  is in saturation;  $M_2$  is in saturation



assume  $M_1 = M_2$   
& Early effect small

find  $v_o$  at bias,  $v_i = 0$

@ bias  $\frac{d}{dt} \equiv 0$  so ignore C for bias

$$I_{S_{D1}} = I_{D2} \Rightarrow \frac{K_P W}{2 L} (V_{SG} - |V_{TD}|)^2 = \frac{K_P W}{2 L} (V_o - |V_{TD}|)^2 (1 + \lambda(V_{DD} - V_o))$$

$$\Downarrow$$

$$V_{DD} - V_G - |V_{TD}| = V_o - |V_{TD}|$$



$$\Rightarrow V_o = V_{DD} - V_G$$

True in the case of Early effect if  $V_o = V_{DD} - V_o$   
 $\Rightarrow V_o = V_{DD}/2 \Rightarrow V_G = V_o = V_{DD}/2$

assume  $V_G = \frac{V_{DD}}{2}$  & find  $g_m$

$$g_m = \frac{\partial I_S}{\partial V_{SG}} = \frac{K_P W}{L} \cdot 2 (V_{SG} - |V_{TD}|) = 2 \frac{I_S}{(V_{SG} - |V_{TD}|)}$$

find small signal equivalent

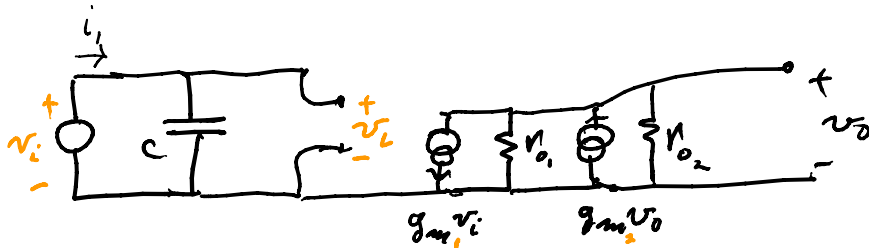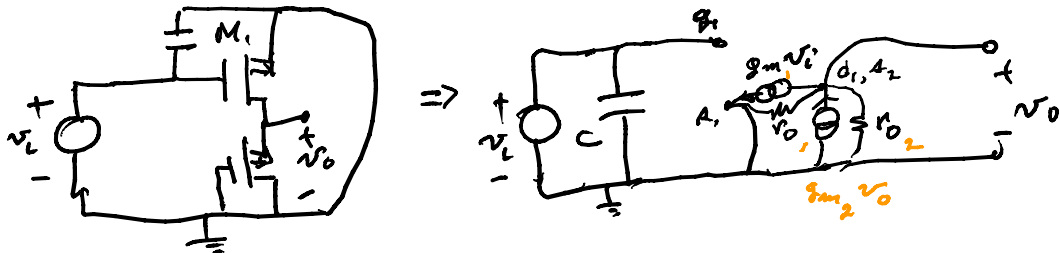

$$g_{m1} = g_{m2} = g_m$$

$$r_{o1} = r_{o2} = \frac{1}{g_o}$$

2-port  $Y$  as seen by  $v_i \in v_o$ :  $y_{11} = sC$ ,  $y_{12} = 0$ ,  $y_{21} = g_m$ ,  $y_{22} = 2g_o - g_{m2} = 2g_o - g_m$

By inspection

using  $y_{ik} = \frac{i_i}{v_k} \mid v_j = 0$

$i, k \in \{1, 2\}$

$$Y(s) = \begin{bmatrix} sC & 0 \\ g_m & 2g_o - g_m \end{bmatrix}$$