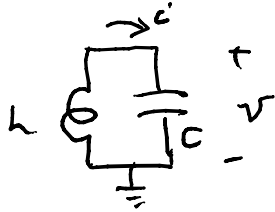


03/31/09  
EE303

oscillators




$$i = C \frac{dv}{dt}$$

$$-v = L \frac{di}{dt} \Rightarrow -v = L \frac{d(C \frac{dv}{dt})}{dt}$$

$$= LC \frac{d^2 v}{dt^2}$$
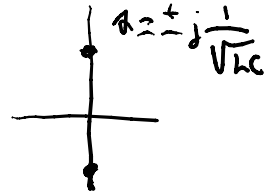
$$\frac{d^2 v}{dt^2} + \frac{1}{LC} v = 0 \Rightarrow \left( \frac{d^2}{dt^2} + \frac{1}{LC} \right) v = 0$$



$$\ddot{x} + \omega_0^2 x = 0$$

$\rightarrow \ddot{x} + \frac{dF(x)}{dx} + \omega_0^2 x = 0$  is a nonlinear system

$$\text{van der Pol} \Rightarrow \frac{dF(x)}{dt} = \epsilon(-1+x^2)\dot{x}$$

allows small signals to increase via a negative R  
 " large " " decrease " " positive R

$\therefore$  allows for a limit cycle  
 so convert to state variables for physical circuits

$$\rightarrow \frac{d(\dot{x} + F(x))}{dt} + \omega_0^2 x = 0$$

$$x_2 = \dot{x} + F(x) \Rightarrow \frac{dx_2}{dt} = -\omega_0^2 x$$

$$\text{set } x_1 = x \Rightarrow \begin{cases} \dot{x}_1 = x_2 - F(x_1) \\ \dot{x}_2 = -\omega_0^2 x_1 \end{cases}$$

} state variable eqs  
 for structurally  
 stable oscillator

replace  $t$  by  $\frac{1}{\omega_0} \hat{t}$  gives  $\omega_0^2 \rightarrow 1$

$$\begin{cases} \dot{x}_1 = x_2 - F(x_1) \\ \dot{x}_2 = -x_1 \end{cases} \text{ } \left. \vphantom{\begin{cases} \dot{x}_1 = x_2 - F(x_1) \\ \dot{x}_2 = -x_1 \end{cases}} \right\} \text{ look at } x_2 - x_1 \text{ plane}$$

$$\frac{dx_2/dt}{dx_1/dt} = \frac{dx_2}{dx_1}$$

$$= \frac{-x_1}{x_2 - F(x_1)}$$

