

Electronic circuits



BJT
exponentials






MOS
polynomial

nonlinear

for ODE $\frac{dx}{dt} \Rightarrow$ capacitor $\frac{1}{s} \equiv$


a handy device is the OTA

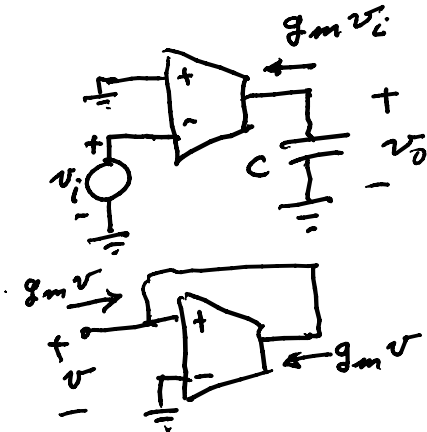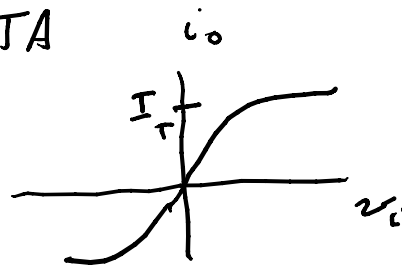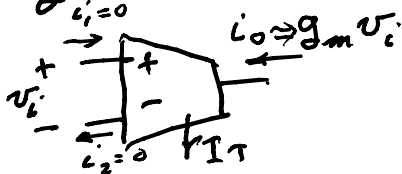

$$-g_m(-v_i) = C \frac{dv_o}{dt}$$

$$v_o = \frac{g_m}{C} \int_0^t v_i(\tau) d\tau + v_o(0)$$


$$i = g_m v$$

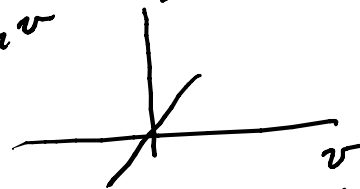


a good description is $Y(s)$; 2×2 for a 2-port
 $i = Y v$

$$Y \text{ for OTA} \Rightarrow \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix} \begin{bmatrix} v_i \\ v_o \end{bmatrix}; Y|_{\text{OTA}} = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix}$$

if add admittances use parallel ports

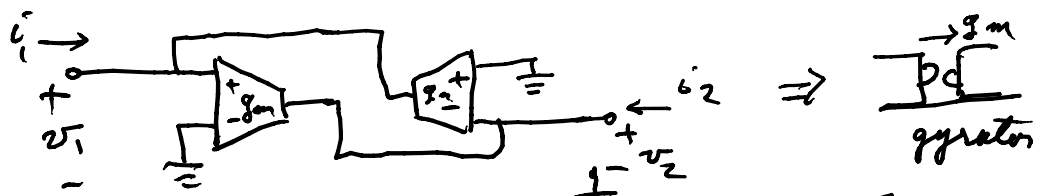

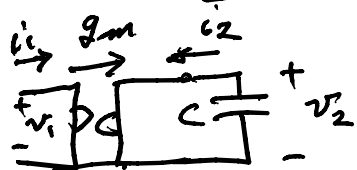
$$Y_1 + Y_2 = \begin{bmatrix} 0 & 0 \\ g_m & 0 \end{bmatrix} + \begin{bmatrix} 0 & -g_m \\ 0 & 0 \end{bmatrix} = \begin{bmatrix} 0 & -g_m \\ g_m & 0 \end{bmatrix}$$



$$C v_2 = -i_2 = -g_m v_1$$
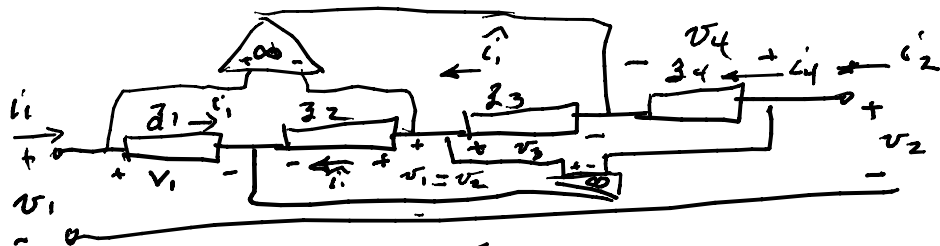
$$C v_2 = -i_2 \Rightarrow v_2 = \frac{C v_1}{g_m} = L v_1$$




$$v_1 = z_1 i_1 = z_2 \hat{i}_1 \Rightarrow \hat{i}_1 = \frac{z_1}{z_2} i_1 \quad v_2 = v_1$$

$$v_3 = -z_3 \hat{i}_1 = -z_3 \left(\frac{z_1}{z_2}\right) i_1 = v_4; \quad i_4 = \frac{1}{z_4} v_4 = \left(-z_3 \frac{z_1}{z_2}\right) \frac{i_1}{z_4}$$


$$i_2 = -\frac{z_3 z_1}{z_4 z_2} i_1; \quad v_2 = v_1 \quad \left. \vphantom{i_2} \right\} \text{no admittance}$$

can get high order polynomials in $A = \sigma + j\omega$


Biasing; small signal behavior

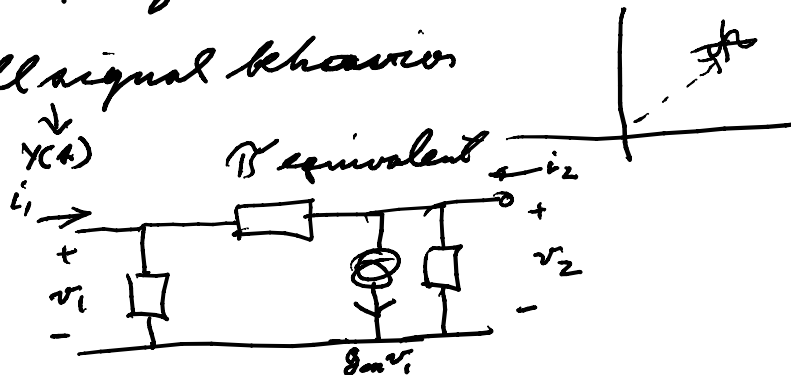

For the BJT is the forward active region

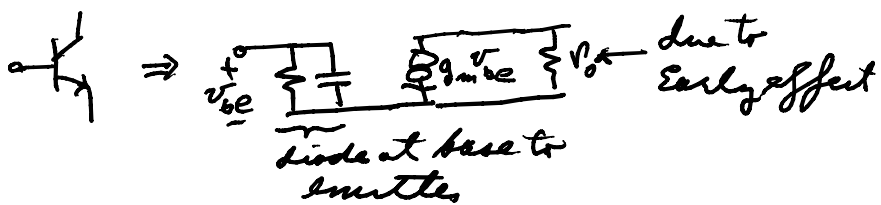

current mirror

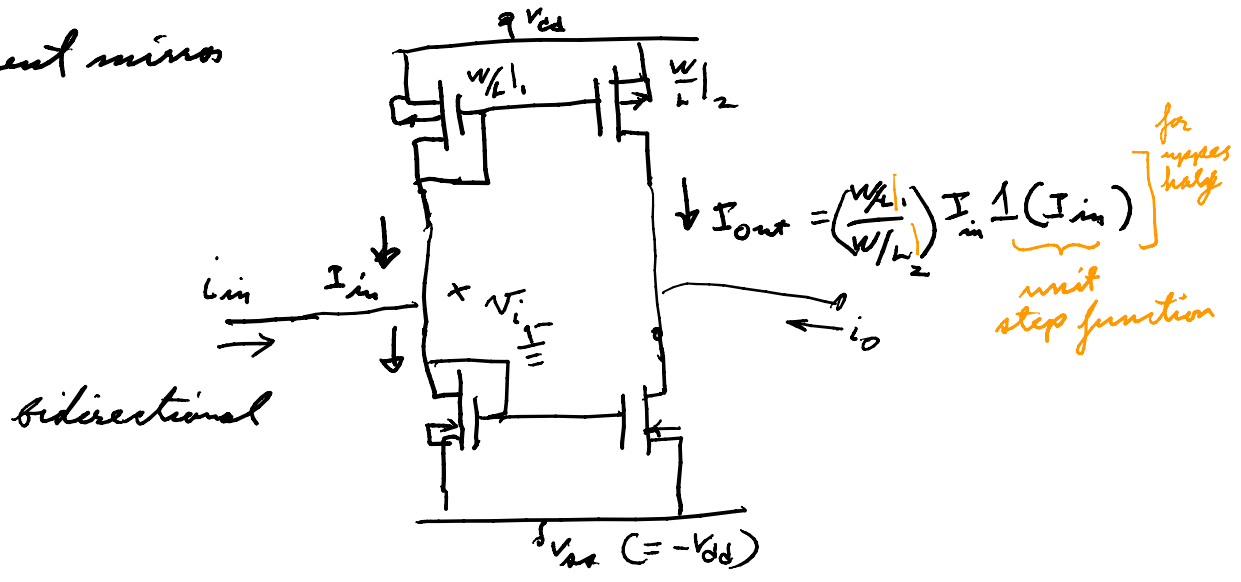



has current flowing (I_{in}) when $i_{in} = 0$

$$\begin{aligned}
 \text{if } i_{in} = 0 \Rightarrow I_{in} &= \frac{K_P W}{2 L_n} (v_i - V_{ds} - V_{TO_n})^2 (1 + \lambda_n [v_i - V_{ds}]) \\
 &= \frac{K_P W}{2 L_p} (V_{ds} - v_i - |V_{TO_p}|)^2 (1 + \lambda_p [V_{ds} - v_i]) \\
 &\quad \text{about equal } \approx 1 + \lambda V_{ds}
 \end{aligned}$$

$$\begin{aligned}
 \text{assume } \frac{K_P W_n}{2 L_n} = \frac{K_P W_p}{2 L_p} \Rightarrow v_i - V_{ds} - V_{TO_n} &= V_{ds} - v_i - |V_{TO_p}| \\
 2v_i &= V_{ds} + V_{ds} + V_{TO_n} - |V_{TO_p}|
 \end{aligned}$$

$$\text{if } V_{ds} = -V_{ds}, V_{TO_n} = +|V_{TO_p}| \Rightarrow 2v_i = 0 \Rightarrow v_i = 0$$

$$I_{in} = \left(\frac{K_P W}{2 L} \right) (V_{ds} - |V_{TO_p}|)^2 (1 + \lambda_p V_{ds})$$

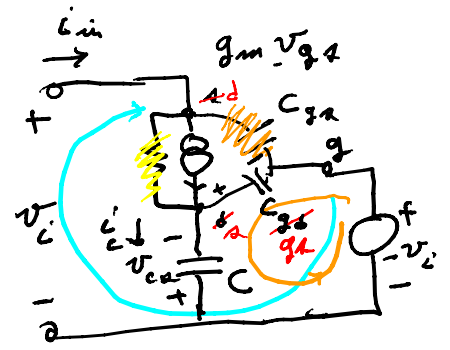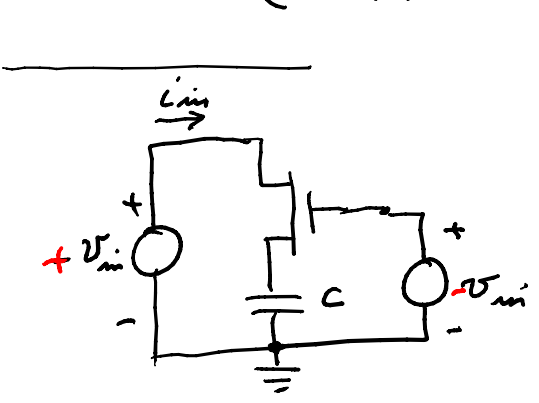

$$\begin{aligned}
 i_{in} &= g_m v_{ga} ; \quad v_{ga} = -v_i - v_sx = -2v_i \\
 &= -2g_m v_i \Rightarrow Y_{in} = -2g_m
 \end{aligned}$$

modified

$$\text{still } i_{in} = g_m v_{ga}$$

$$\text{here } v_i + v_{cs} + v_{cgs} = 0 ; \quad i_c = g_m v_{ga} + C_{gs} \cdot 2 \cdot v_{ga}$$

$$v_i + \frac{1}{ac} [g_m v_{gs} + C_{gs} a v_{gs}] + v_{cgs} = 0$$

$$v_i = \left(+1 + \frac{g_m}{ac} + \frac{C_{gs}}{c} \right) v_{gs} \Rightarrow v_{gs} = \frac{ac}{ac + (g_m) + ac C_{gs}} \cdot v_i$$

$$i_{in} = g_m v_{gs} = \frac{g_m C a}{a(C_{gs} + C) + g_m} \cdot v_i$$

$$\Rightarrow f_{in}(s) = \frac{g_m C a}{a(C_{gs} + C) + g_m} = \frac{g_m C}{C_{gs} + C} + \frac{-\left(\frac{g_m}{C_{gs} + C}\right)^2 C}{a + \frac{g_m}{C_{gs} + C}}$$



$$= \frac{g_m C}{C_{gs} + C} \cdot \frac{1}{a + \frac{g_m}{C_{gs} + C}}$$

by partial fraction expansion
pole at $s_p = -\frac{g_m}{C + C_{gs}}$, zero at $s_z = 0$

Note: actually $g_m \rightarrow -g_m$
if this is an NMOS device as it probably should be, then the pole is in the RHP \rightarrow unstable

CMOS

Capacitor

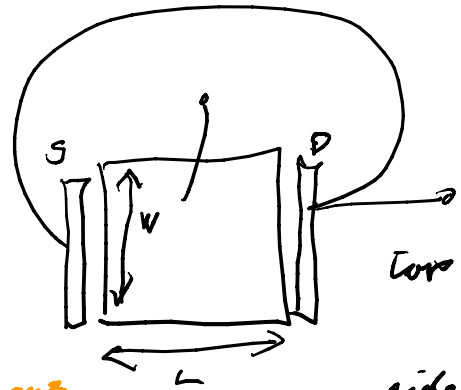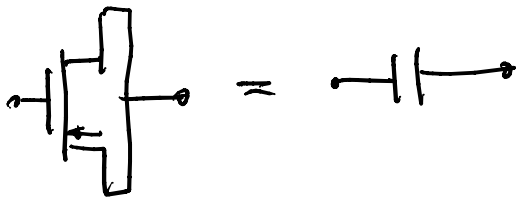

Thickness of oxide

$$t_{ox} \approx 100 \text{ \AA}; \quad A^0 = 10^{-10} \text{ m}$$

$$C = \frac{\epsilon A}{t_{ox}} = \frac{\epsilon_{SiO_2} \cdot W \cdot L}{t_{ox}} \quad \text{free space } \epsilon_0$$


$$\epsilon_{SiO_2} \approx \epsilon_0 \times 4 \approx 8 \times 10^{-12} \text{ F/m}$$

$$C \approx \frac{32 \times 10^{-12}}{100 \times 10^{-10}} \times W \cdot L = 32 \times 10^{-4} \times W \cdot L$$

$$= 32 \times 4 \times 10^{-4} \times 10^{-4} \times 10^{-12} \quad \text{if } W=L=2\mu$$

$$= 128 \times 10^{-16} = 1.28 \times 10^{-2} \times 10^{-12} = 0.0128 \text{ pF}$$
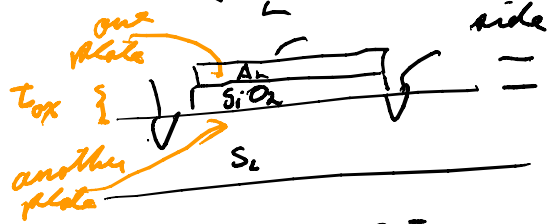
$$\text{if } L=L=100\mu \Rightarrow C \approx \frac{32 \times 10^{-12} \times 100 \times 10^{-2}}{100} = 32 \text{ pF}$$



$C \approx 1-10 \text{ fF}$
for a $1\mu \times 1\mu$