

Solutions EE303 Homework

#1. as  $V_0 = R_{out} I_{SD_{max}}$  we need  $I_{SD}$  (which is part b)



$I_{SD_{max}} = I_{SD_{min}}$  as  $V_{min} = V_0 = 3V \Rightarrow V_{SP_{min}} = V_{DD} - V_0 = 9 - 3 = 6V \Rightarrow M_{out}$  is in saturation  
 $= V_{SG}$

$\Rightarrow I_{SD_{min}} = \frac{K_P W}{2 L} (V_{SG} - |V_{TD}|)^2 (1 + \lambda_V V_{SG})$   
 $= \frac{10.32 \times 10^{-6}}{2} \times \frac{328 \times 10^{-6}}{8 \times 10^{-6}} (6 - 1.5)^2 (1 + 0.015 \times 6)$   
 $= 211.56 \times 10^{-6} (20.25) (1.09) = 4,669.658 \times 10^{-6} A$

b)  $I_{SD} = 4.670 \mu A$

a)  $R_{out} = \frac{V_0}{I_{SD}} = \frac{3}{4,669.658 \times 10^{-6}} = 0.6424 \times 10^3 = \frac{642 \Omega = R_{out}}$

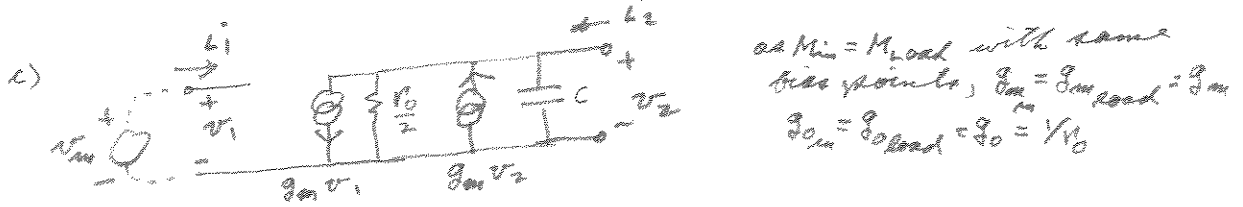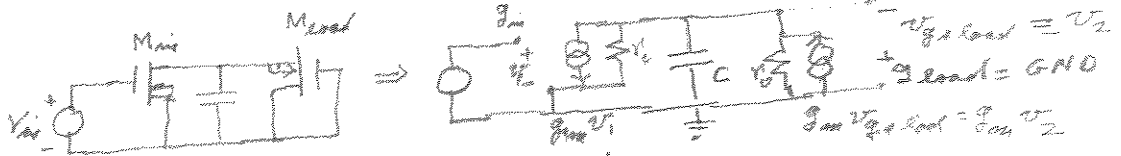- #2. a) By symmetry both transistors have  $V_{GS} = 5$  if  $V_0 = 5$  and then both are in saturation with the same current  $I_D$  giving the voltage  $V_0 = 5$   
 b) as  $V_{gs} \& V_{ds} \rightarrow 0$  for small signal




Numerically for the 400T:  $g_0 = \frac{2 I_D}{\partial V_{GS}} = \frac{\lambda_1 I_D}{1 + \lambda V_{DS}}, g_m = \frac{2 I_D}{(V_{GS} - V_{TD})}$   
 Hence  $I_D = \frac{K_P W}{2 L} (V_{GS} - V_{TD})^2 (1 + \lambda V_{DS}) = \frac{20.54 \times 10^{-6}}{2} \times \frac{144}{8} (5 - 1.3)^2 (1 + 0.015 \times 5) = 184.86 \times 10^{-6} (13.69) \times (1.075)$   
 $= 2.721 \text{ mA} \Rightarrow g_0 = 0.015 \times 184.86 \times 10^{-6} \times 13.69 = 37.96 \times 10^{-6}$   
 $g_m = 397.4 \times 10^{-6}$

$\Rightarrow Y = \begin{bmatrix} 0 & 0 \\ 397.4 & AC \times 10^6 - 321.5 \end{bmatrix} \times 10^{-6}$  (note: port 2 sees a negative R)

#3, you can use the results of the 03/24/09 lecture where its  $Y_{in}(s)$  or redo us here

Redrawing

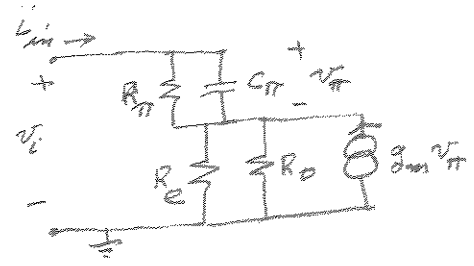

def  $Y_{\pi} = g_{\pi} + sC_{\pi} \Rightarrow$

$G_O = 1/R_O = 1/R_E$

Here  $i_{in} = Y_{\pi} v_{\pi} = (v_i - v_{\pi})(2G_O) - g_m v_{\pi}$   
 $= 2G_O v_i - [g_m + 2G_O] v_{\pi}$

$\Rightarrow \{Y_{\pi} + [g_m + 2G_O]\} v_{\pi} = 2G_O v_i \Rightarrow v_{\pi} = \frac{2G_O}{Y_{\pi} + [g_m + 2G_O]} \cdot v_i$

$\therefore i_{in} = Y_{\pi} v_{\pi} = Y_{\pi} \times \frac{2G_O}{Y_{\pi} + g_m + 2G_O} \cdot v_i \Rightarrow Y_{in}(s) = \frac{2G_O Y_{\pi}}{Y_{\pi} + g_m + 2G_O}$   
 $= \frac{2G_O (sC_{\pi} + g_{\pi})}{sC_{\pi} + g_{\pi} + [g_m + 2G_O]}$   
 $= 2G_O \left[ \frac{s + g_{\pi}/C_{\pi}}{s + \frac{g_{\pi}}{C_{\pi}} + \frac{g_m + 2G_O}{C_{\pi}}} \right]$

For a BJT

$g_m = \frac{I_c}{V_T}, g_{\pi} = \frac{g_m}{\beta}, g_O = \frac{I_c}{V_A} = G_O$   
 $\Rightarrow g_m = \frac{2.6 \times 10^{-3}}{26 \times 10^{-3}} = 0.1, g_{\pi} = \frac{0.1}{100} = 10^{-3}, G_O = \frac{2.6 \times 10^{-3}}{100} = 2.6 \times 10^{-6}$

a)  $\therefore Y_{in}(s) = 5.2 \times 10^{-6} \left[ \frac{s + 10^{-3}/C_{\pi}}{s + \frac{10^{-1} + 10^{-3} + 5.2 \times 10^{-6}}{C_{\pi}}} \right] \approx 5.2 \times 10^{-6} \frac{s + 10^{-3}/C_{\pi}}{s + \frac{1.01 \times 10^{-3}}{C_{\pi}}}$


a<sub>2</sub>) zeros @  $s_0 = -g_{\pi}/C_{\pi} = -10^{-3}/C_{\pi}$

a<sub>3</sub>) poles @  $s_p = -[g_m + g_{\pi} + 2G_O]/C_{\pi} \approx -1.01 \times 10^{-3}/C_{\pi}$

b) for  $C_{\pi} = 10 \text{ pF} = 10 \times 10^{-12} \Rightarrow s_0 = -10^{-3} \times 10^{-1} \times 10^{+12} = -10^8$   
 $s_p = 1.01 \times 10 = -1.01 \times 10^8$



c) at  $s = j\omega \rightarrow j\infty \Rightarrow Y_{in} \Rightarrow |Y_{in}(\infty)| e^{j\omega t} = 2G_O$   
 at  $s \rightarrow \infty, C_{\pi} \rightarrow \text{short} \& v_{\pi} \rightarrow 0 \Rightarrow$

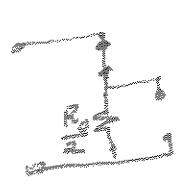

$\Rightarrow Y_{in} = \frac{1}{R_{O||2}} = 2G_O$