

Biasing problems:

1. Work Problem 5.130, p. 533, for the circuit of Figure P5.130.
2. Work Problem 4.58, p. 367, for the circuit of Figure 4.30 (c) of p. 282.

Inverter:

3. Work Problem 4.112, p. 375; also obtain  $t_{PLH}$ .