
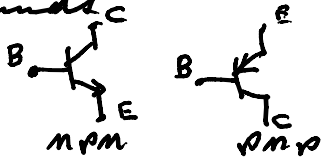


Transistor = transfer resistor

Two basic kinds
bipolar

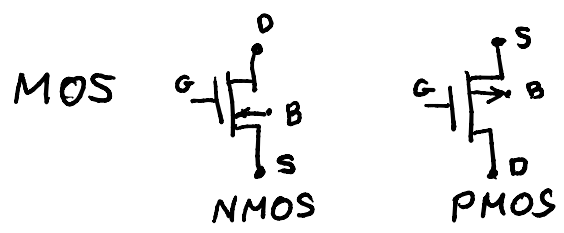

B = base
E = emitter
C = collector





G = gate
S = source
D = drain
B = bulk

β = beta = current gain of a bipolar transistor

KP = current for voltage gain of MOS \Rightarrow KP $\frac{W}{L}$



arrows come from current in diodes

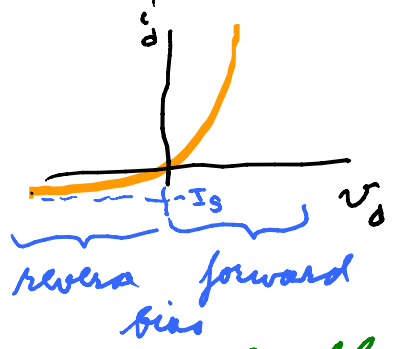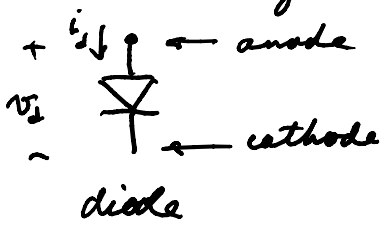


Law of diode

$$i_d = I_s (e^{v_d/V_T} - 1)$$

V_T = Thermal voltage
 $= \frac{kT}{|q|}$, T = temperature
 k = Boltzmann's constant
 |q| = electron charge
 $\approx 0.026 \text{ V @ room temp.}$

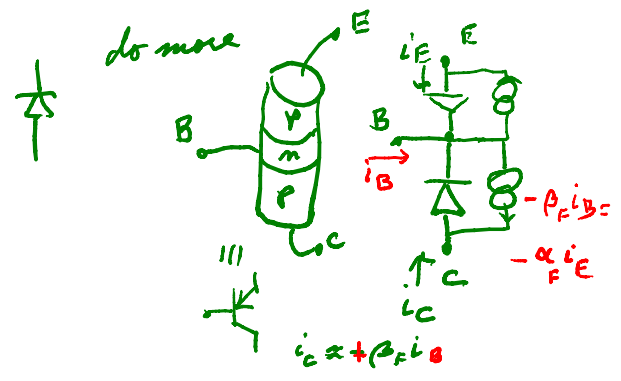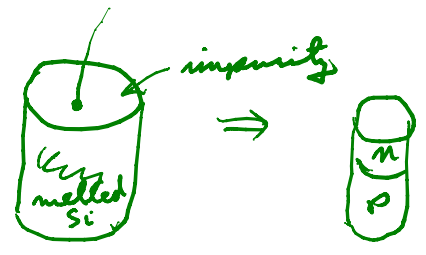

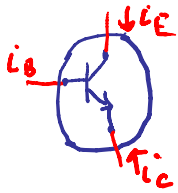

$$KCL \Rightarrow 0 = i_B + i_E + i_C$$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$i_E = -i_B - i_C$$

$$i_C = -\alpha i_E \Rightarrow i_E = -i_B + \alpha i_E$$



$$(1-\alpha)i_E = -i_B$$

$$= (1-\alpha)\left(-\frac{i_C}{\alpha}\right) = i_B$$

$$i_C = \frac{\alpha}{1-\alpha} i_B = \beta i_B$$

Bipolar transistor is a current controlled current source

MOS

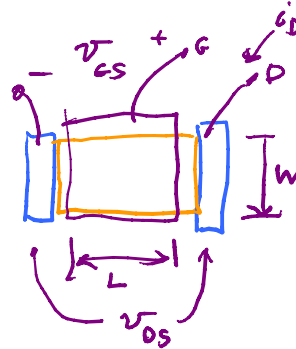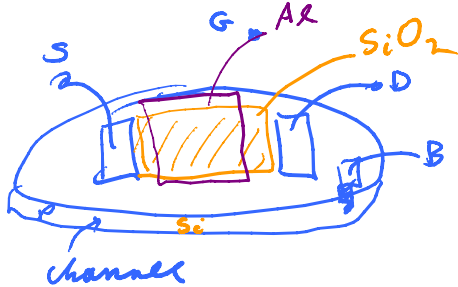

$$i_D = \frac{K_P W}{2 L} (v_{GS} - V_{th})^2 \quad \text{if } v_{GS} > V_{th}$$

$$\& v_{GS} - V_{th} \leq v_{DS}$$

$V_{th} \approx V_{TO}$ = turn on voltage

= threshold voltage

$$V_{TO} = V_{th} \text{ if } v_{BS} = 0$$

$$= \frac{K_P W}{2 L} \left\{ 2(v_{GS} - V_{th})v_{DS} - v_{DS}^2 \right\} \quad \text{if } v_{GS} > V_{th}$$

$$\& v_{GS} - V_{th} \geq v_{DS}$$

looks like a resistor



which with v_{GS}

an MOS transistor is like a voltage controlled current source.

all of the above is for DC; note these transistors are quite nonlinear.