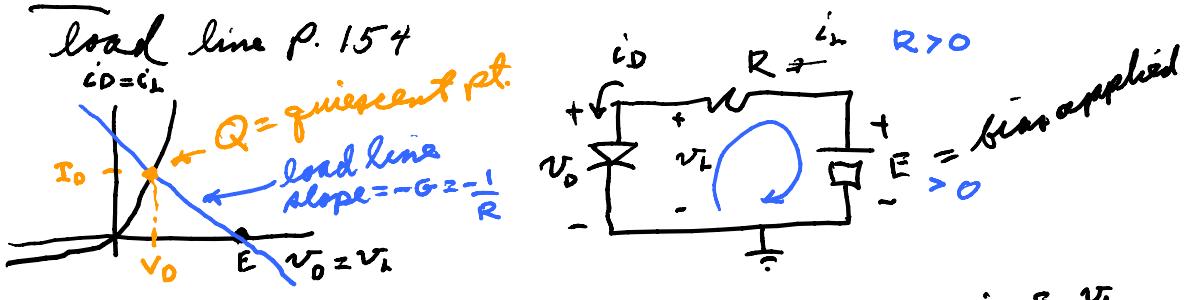


To next time: appendix B, pp. B-1 through B-7
 BJT biasing, p. 432-436
 BJT hybrid Π , p. 488

EE 303
 02/02/10





$$KVL: -v_L - R i_L + E = 0 \Rightarrow i_L = \frac{E - v_L}{R}$$

$$KVL: v_L = v_0$$

$$KCL: i_D = i_L$$

Put in signal

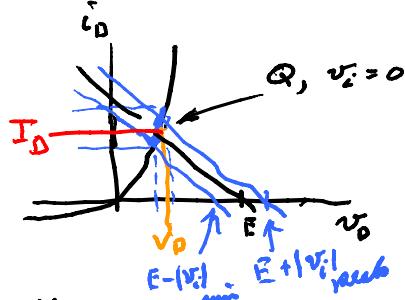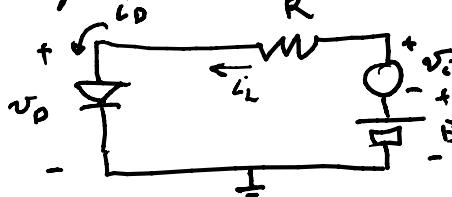

desire to know changes in i_D , call
 this signal current, i_s , when v_i changes
 i.e. desire current due to signal.

$$i_D = I_D + i_s \quad ; \quad i_D = \text{total current}$$

$$I_D = \text{bias current}$$

$$i_s = \text{signal current}$$

$$v_D = V_D + v_d$$

$i_D = f(v_D)$ make a Taylor series expansion
 about $v_Q = V_D$

$$= f(V_D) + \left. \frac{df(v_D)}{dv_D} \right|_{V_D} (V_D - V_D) + \frac{1}{2!} \left. \frac{d^2 f(v_D)}{dv_D^2} \right|_{V_D} (V_D - V_D)^2 + \dots$$

$$v_D = V_D$$

ignore if
 small signal



$$i_D - f(v_D) = i_D - I_D = i_s$$

$$v_D - V_D = v_d$$

$$\left. i_s = \frac{df(v_D)}{dv_D} \right|_{V_D} \cdot v_d = g_s \cdot v_d$$

for small signal
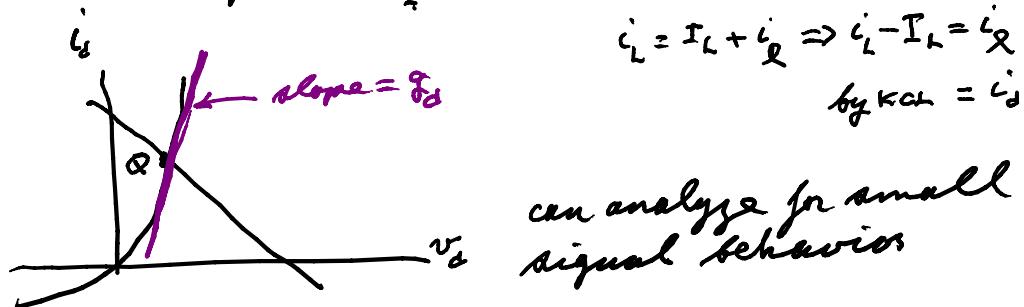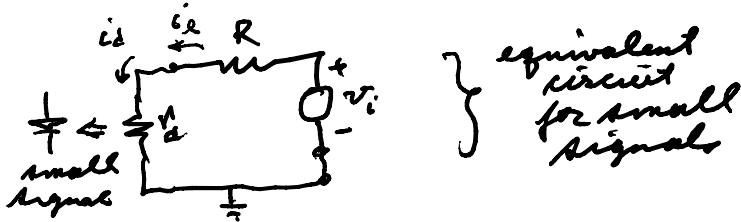
$$\frac{1}{R} \Rightarrow \frac{1}{R} = \frac{1}{\frac{1}{g_d}} = g_d$$



$$(R + r_d) i_d = v_i$$




$$i_d = \frac{v_i}{R + r_d}$$

$$v_d = \frac{r_d}{R + r_d} \cdot v_i$$


power into v_i :

$$v_i (-i_d) = - \frac{v_i^2}{R + r_d}$$

To find the Q point in SPICE

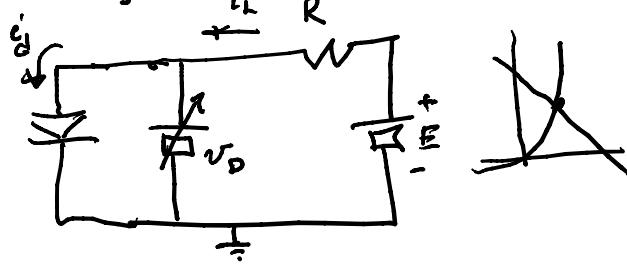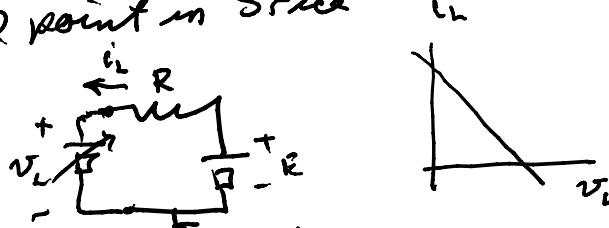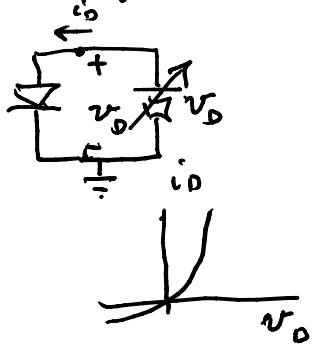


Equivalent circuit for a transistor NMOS

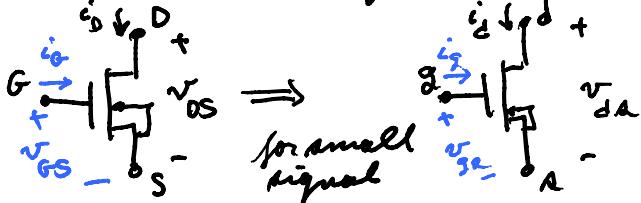

for small signal

choose v_{GS} for Q

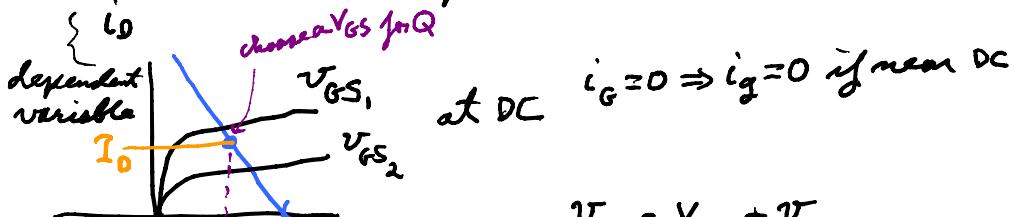

$i_G = 0 \Rightarrow i_g = 0$ if near DC

$$V_{DS} = V_{DS} + V_{dA}$$

$$i_D = I_D + i_d \quad ; \quad Q = (v_{GS}, v_{DS})$$

$$v_{GS} = v_{GS} + v_{gA} \quad ; \quad Q = \text{bias point of transistor}$$

δ_m

$$i_d = f(v_{GS}, v_{DS}) = f(v_{GS}, v_{DS}) + \frac{\partial i_d}{\partial v_{GS}} | (v_{GS} - v_{GS}) \quad m = \text{mutual}$$


$$+ \frac{\partial i_d}{\partial v_{DS}} | (v_{DS} - v_{DS}) + \frac{1}{2!} \frac{\partial^2 i_d}{\partial v_{GS}^2} | (v_{GS} - v_{GS})^2$$

$$+ \frac{1}{2!} \frac{\partial^2 i_d}{\partial v_{DS}^2} | (v_{DS} - v_{DS})^2$$

$$+ \frac{\partial^2 i_d}{\partial v_{GS} \partial v_{DS}} | (v_{GS} - v_{GS})(v_{DS} - v_{DS}) + \dots$$

Throw away for small signals

$$i_d = g_m v_{gA} + g_d v_{dA}$$

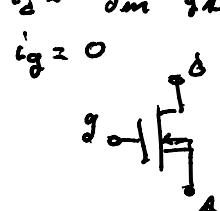

$$i_g = 0$$



$$r_d = \frac{1}{g_d} = \text{drain resistance}$$

To find these parameters, g_m & g_d , when in saturation

$$i_D = \frac{k_P}{2} \cdot \frac{W}{L} (v_{GS} - V_{TO})^2 (1 + \lambda v_{DS})$$

$$\frac{i_D}{v_{GS}} = \frac{1}{r_d} = \frac{1}{g_d}$$

$$\text{for } g_m = \left. \frac{\partial i_o}{\partial v_{gs}} \right|_Q = 2 \left(\frac{k_p w}{2} \right) (v_{gs} - V_{TO}) (1 + \lambda v_{ds}) \Big|_Q$$

$v_{ds} = v_{os}, v_{gs} = V_{GS}$

$$= 2 \cdot \frac{c_o}{(v_{gs} - V_{TO})} \Big|_Q = 2 \cdot \frac{I_o}{(V_{GS} - V_{TO})}$$

$$\text{for } g_d = \left. \frac{\partial i_o}{\partial v_{ps}} \right|_Q = \frac{k_p w}{2} (v_{gs} - V_{TO}) \cdot \lambda \Big|_Q \approx I_o \cdot \lambda$$

