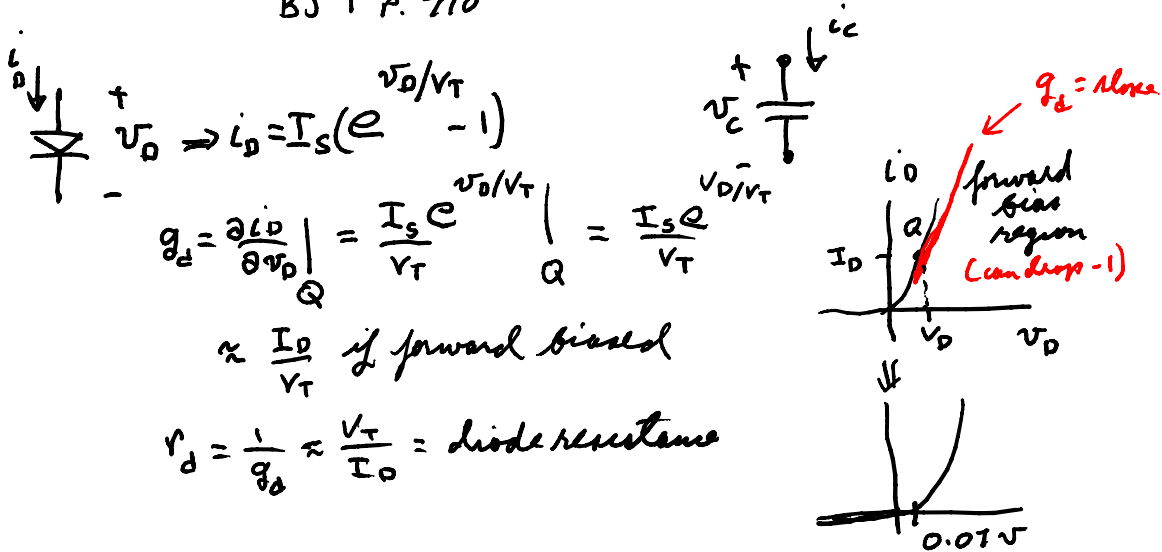



for next time
 current sources/mirrors
 MOS p. 563 & 649
 BJT p. 442 & 650

EE303
 02/04/10

differential pair
 MOS p. 721
 BJT p. 710



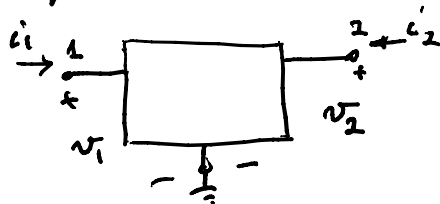small signals \Rightarrow linear behavior




use admittance description; $Y(s)$ a 2×2 matrix


$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = Y(s) \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

if $v_2 = 0 \Rightarrow i_1 = y_{11} v_1$ $y_{11} = \frac{i_1}{v_1} \bigg|_{v_2=0} \Rightarrow \text{short port 2}$

$i_2 = y_{21} v_1$ $y_{21} = \frac{i_2}{v_1} \bigg|_{v_2=0}$

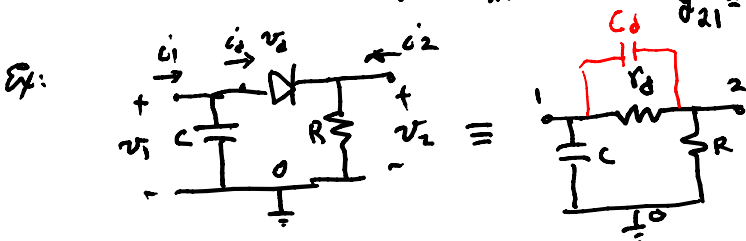

for y_{11} & y_{21} short port 2

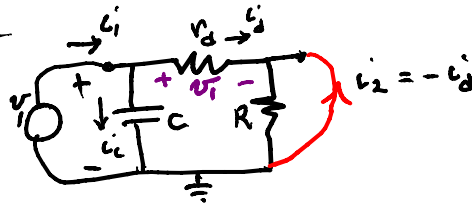


$$y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0} = -\frac{i_1}{v_1} = -g_d$$

$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0} = \frac{i_d + i_c}{v_1} = +\frac{g_d \cdot v_1 + \omega C v_1}{v_1} = \omega C + g_d$$

$$y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0} = -g_d$$

$$y_{22} = \frac{g_d \cdot v_2 + G v_2}{v_2} = g_d + G$$

$$G = 1/R$$

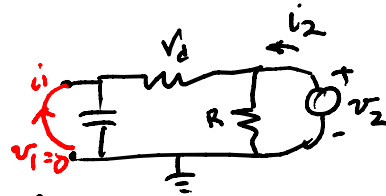


$$Y(s) = \begin{bmatrix} g_d + \omega C & -g_d \\ -g_d & g_d + G \end{bmatrix}; \quad Z = Y^{-1} = \frac{1}{g_d(\omega C + G)} \begin{bmatrix} g_d + G & g_d \\ +g_d & g_d + \omega C \end{bmatrix}$$

$$= \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$$

note $z_{11} = \frac{g_d + G}{g_d(\omega C + G)}$

$$\neq \frac{1}{y_{11}} = \frac{1}{g_d + \omega C}$$

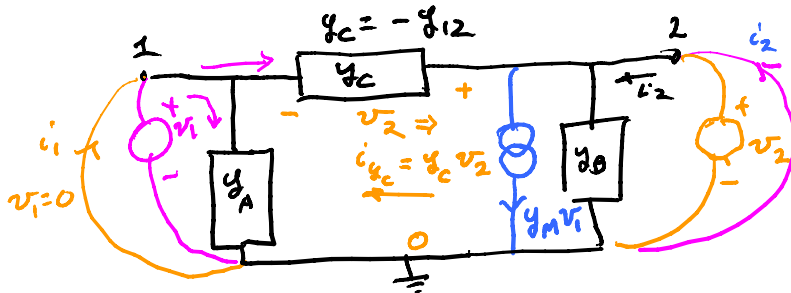a universal equivalent circuit for $Y(s)$



$$y_{12} = \left. \frac{i_1}{v_2} \right|_{v_1=0} = -y_C$$

$$y_{11} = \left. \frac{i_1}{v_1} \right|_{v_2=0} = y_A + y_C$$

$$= \frac{y_C v_1}{v_1} + \frac{y_A v_1}{v_1}$$

— for $v_1=0$

— for $v_2=0$ node 2=0

$$y_{22} = \left. \frac{i_2}{v_2} \right|_{v_1=0} = y_B + y_C$$

$$y_B = y_{22} - y_C$$

$$\dots = y_{22} + y_{12}$$

$$y_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0} = \frac{-y_C v_1}{v_1} + \frac{y_M v_1}{v_1} = y_{12} + \text{correction}$$


$$= -y_C + y_M$$

$$y_M = y_{21} + y_C = y_{21} - y_{12}$$

$$y_A = y_{11} - y_C = y_{11} + y_{12}$$

given $Y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$

Equivalent circuit

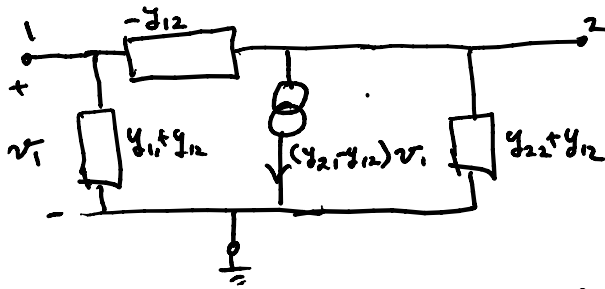


For

the NMOS transistor small signal equivalent



at DC $i_c = i_q = 0$
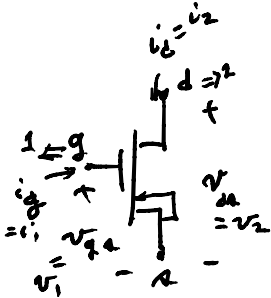
$$i_d = g_m v_{gs} + g_d v_{ds} \Rightarrow \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} 0 & 0 \\ g_m & g_d \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$




$$g_d = \frac{I_D}{V_A} = \lambda I_D$$

$$g_m = \frac{I_D}{(V_{GS} - V_{TO})}$$

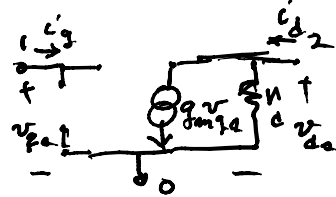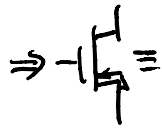



in saturation region

add in gate capacitors C_{gs} & C_{gd}

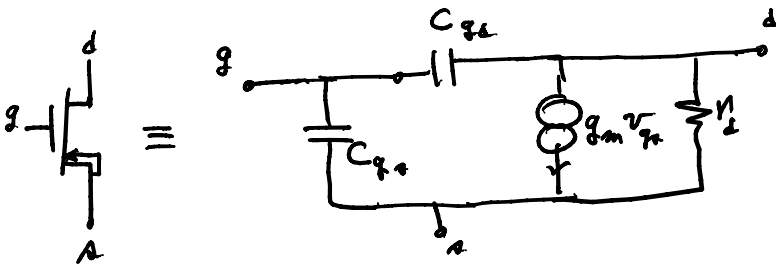


for "all"


for the BJT

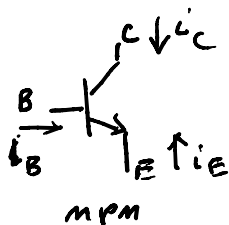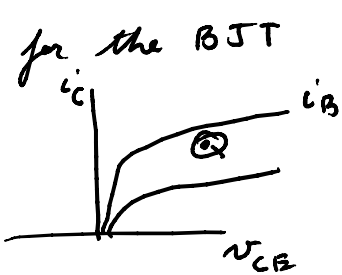

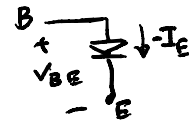for forward active region
diode CB we reverse bias
diode BE we forward bias



forward active

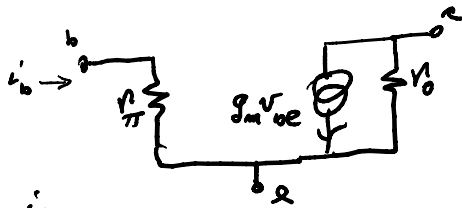

$$i_b + i_c + i_e = 0$$

by KCL

$$i_c = -\alpha i_e$$

$$\left. \frac{\partial i_b}{\partial v_{BE}} \right|_Q = g_{\pi} = \frac{i_b}{v_{be}}$$