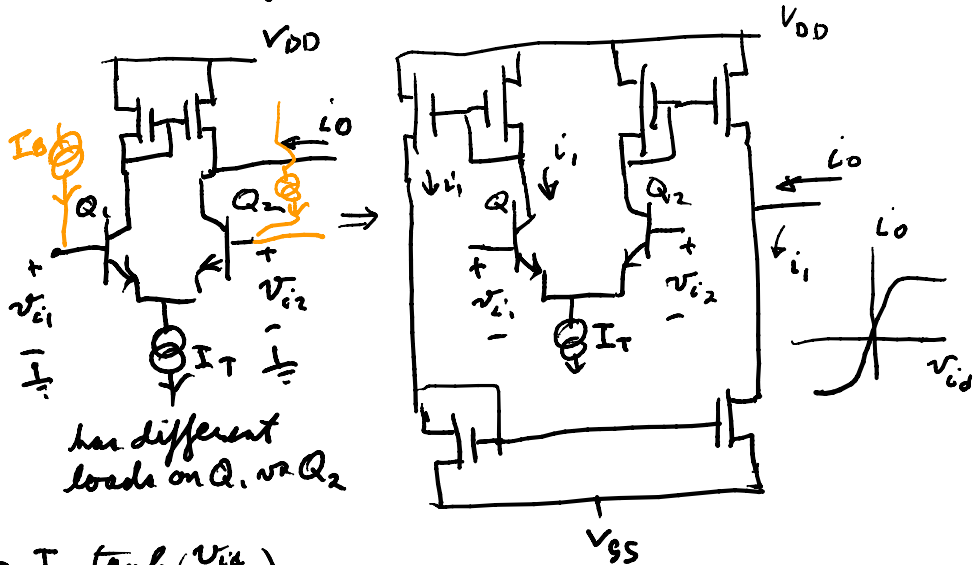


For next time: inverters p. 338
 Biscati eq. for, p. 343

EE303
 02/18/10


Today, more on diff. pair, CMOS eqn, p. 693



$$i_o = I_T \tanh\left(\frac{v_{id}}{2V_T}\right)$$

$\frac{d \tanh x}{dx} = 1 - \tanh^2 x$ is nice for optimizations

CMOS diff. pair

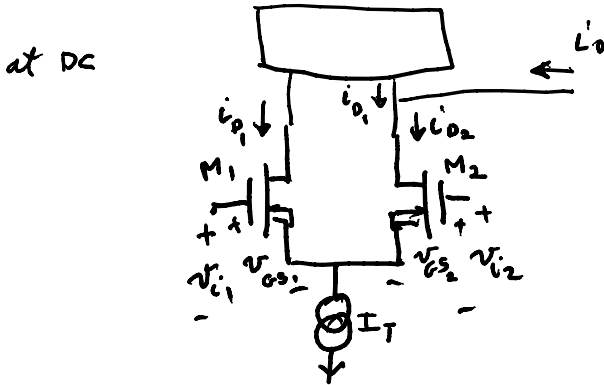

if M_1, M_2 are in saturation

$$i_{o1} = \frac{K_P W}{2 L} (v_{GS1} - V_{T0})^2$$

$$i_{o2} = \frac{K_P W}{2 L} (v_{GS2} - V_{T0})^2$$

$$\beta = \frac{K_P W}{2 L}$$

$$i_o = i_{o2} - i_{o1}$$

$$v_{i0} = v_{i1} - v_{i2} = v_{GS1} - v_{GS2}$$

$$I_T = i_{o1} + i_{o2}$$

$$\text{but } v_{GS1} = V_{T0} \pm \sqrt{i_{o1}/\beta} = V_{T0} + \sqrt{i_{o1}/\beta}$$

if M_1 is on

$$v_{GS2} = V_{T0} + \sqrt{i_{o2}/\beta}$$

$$v_{i0} = v_{GS1} - v_{GS2} = \sqrt{\frac{i_{o1}}{\beta}} - \sqrt{\frac{i_{o2}}{\beta}}$$

square $\beta v_{i0}^2 = i_{o1} + i_{o2} - 2\sqrt{i_{o1}i_{o2}} = I_T - 2\sqrt{i_{o1}(I_T - i_{o1})}$

$$2\sqrt{i_{D1}(I_T - i_{D1})} = I_T - \beta v_{i0}^2$$

$$4(I_T i_{D1} - i_{D1}^2) = (I_T - \beta v_{i0}^2)^2$$

$$i_{D1}^2 - I_T i_{D1} + \frac{1}{4}(I_T - \beta v_{i0}^2)^2 = 0 \quad \text{an eq. for } i_{D1} \text{ vs } v_{i0}$$

$$i_{D1} = \frac{I_T}{2} \pm \frac{1}{2} \sqrt{\cancel{I_T^2} - \frac{1}{4}(I_T - \beta v_{i0}^2)^2}$$

$$= \frac{I_T}{2} \pm \frac{1}{2} \sqrt{\cancel{I_T^2} - 2I_T\beta v_{i0}^2 + \beta^2 v_{i0}^4}$$

$$= \frac{I_T}{2} \pm \frac{1}{2} \sqrt{2I_T\beta v_{i0}^2 - \beta^2 v_{i0}^4} = \frac{I_T}{2} \pm \frac{1}{2} \sqrt{2I_T\beta} \cdot v_{i0} \sqrt{1 - \frac{\beta}{2I_T} v_{i0}^2}$$

need + sign for i_{D1} as $i_{D1} \uparrow$ when $v_{i0} \uparrow$

$$i_{D2} = I_T - i_{D1} = \frac{I_T}{2} - \frac{1}{2} \sqrt{2I_T\beta} v_{i0} \sqrt{1 - \frac{\beta}{2I_T} v_{i0}^2}$$

$$i_{D1} - i_{D2} = i_{D1} - (I_T - i_{D1}) = 2i_{D1} - I_T$$

$$= \frac{I_T}{2} - \frac{1}{2} \sqrt{2I_T\beta} v_{i0} \sqrt{1 - \frac{\beta}{2I_T} v_{i0}^2} - \frac{I_T}{2} + \frac{1}{2} \sqrt{2I_T\beta} v_{i0} \sqrt{1 - \frac{\beta}{2I_T} v_{i0}^2}$$

$$= -\sqrt{2I_T\beta} v_{i0} \sqrt{1 - \frac{\beta}{2I_T} v_{i0}^2}$$

can't hold for large v_{i0}
 $\therefore M_1$ or M_2 must go out of saturation

when $v_{i0} = 0$

$$i_{D1} = I_{D1} = \beta(V_{GS1} - V_{T0})^2 = I_T/2$$

$$i_{D2} = I_{D2} = \beta(V_{GS2} - V_{T0})^2 = I_T/2$$

$$\text{let } V_{ov} = V_{GS} - V_{T0}, \quad V_{GS1} = V_{GS2} = V_{GS}$$

$$V_{ov}^2 = \frac{I_T}{2\beta} \Rightarrow \beta = \frac{I_T}{2V_{ov}^2}$$

$$\therefore i_{D1} - i_{D2} = -\sqrt{2I_T \cdot \frac{I_T}{2V_{ov}^2}} \cdot v_{i0} \sqrt{1 - \frac{I_T}{2V_{ov}^2} \cdot \frac{1}{2I_T} v_{i0}^2}$$

$$= -I_T \cdot \frac{v_{i0}}{V_{ov}} \sqrt{1 - \frac{v_{i0}^2}{4V_{ov}^2}} = -I_T \left(\frac{v_{i0}}{V_{ov}}\right) \sqrt{1 - \left(\frac{v_{i0}}{2V_{ov}}\right)^2}$$

$$\therefore \frac{i_{D1} - i_{D2}}{I_T} = -2 \left(\frac{v_{i0}}{2V_{ov}}\right) \sqrt{1 - \left(\frac{v_{i0}}{2V_{ov}}\right)^2} \Rightarrow y = \frac{i_{D1} - i_{D2}}{I_T} = -2x \sqrt{1 - x^2}$$

$$x = v_{i0}/2V_{ov}$$

to get the maximum (or min)

$$\frac{dy}{dx} = 0; \quad \frac{dy}{dx} = -2\sqrt{1-x^2} - 2x \cdot \frac{1}{2} \frac{1}{\sqrt{1-x^2}} \cdot (-2x)$$

$$0 = -2(1-x^2) + 2x^2 \quad (\text{as } x^2 \neq 1)$$

$$= -2 + 4x^2 \Rightarrow x^2 = 1/2$$




$$y = \frac{i_o}{I_T} = -2 \frac{1}{\sqrt{2}} \sqrt{1 - \frac{1}{2}} = -\sqrt{2} \cdot \frac{1}{\sqrt{2}} = -1$$

at min

∴ at the minimum of i_o or v_{iD} , $i_o = -I_T$




$$\frac{v_{iD}}{2V_{ov}} = x = \frac{1}{\sqrt{2}} \Rightarrow |v_{iD}| = \sqrt{2} \cdot V_{ov}$$

at min

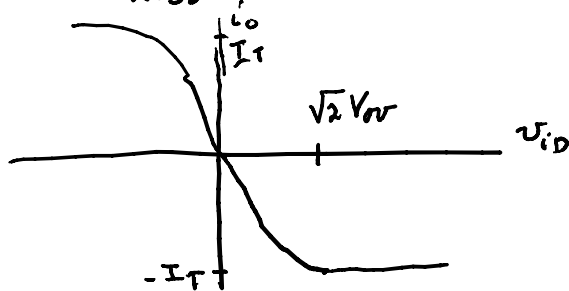

$$i_o = \begin{cases} -I_T & v_{iD} \geq \sqrt{2} V_{ov} \\ -2I_T \left(\frac{v_{iD}}{2V_{ov}} \right) \sqrt{1 - \left(\frac{v_{iD}}{2V_{ov}} \right)^2} & -\sqrt{2} V_{ov} \leq v_{iD} \leq \sqrt{2} V_{ov} \\ +I_T & v_{iD} \leq -\sqrt{2} V_{ov} \end{cases}$$

Biasing for "small signal" behavior

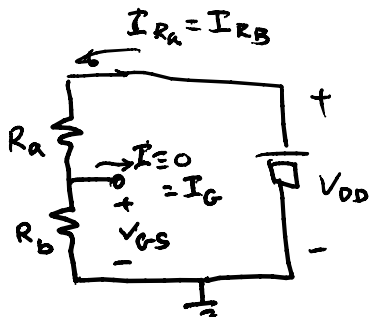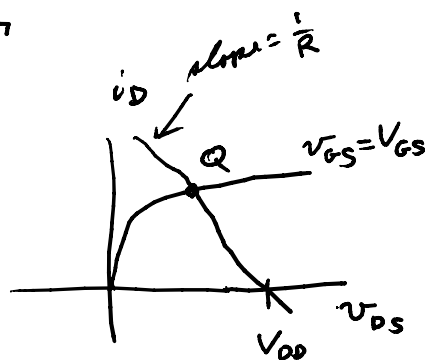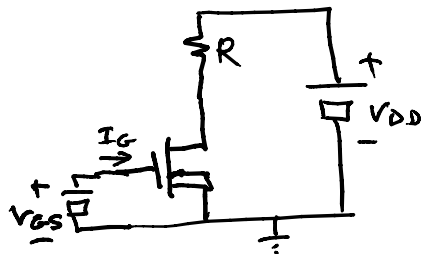

$$V_{GS} = I_{R_B} \cdot R_b$$

$$I_{R_B} = \frac{V_{DD}}{R_a + R_b}$$

$$V_{GS} = \frac{R_b}{R_a + R_b} V_{DD} \quad \left. \vphantom{V_{GS}} \right\} \text{voltage divider}$$

