
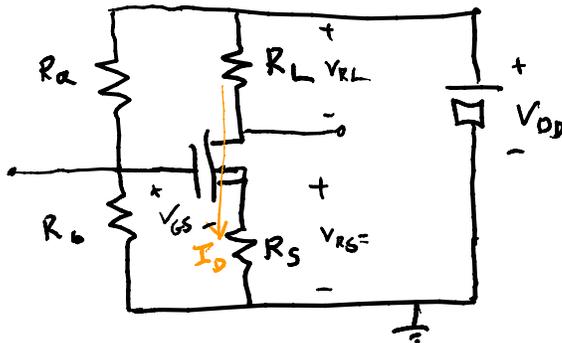


Homework due today now
due next period

EE303
02/23/10

Biasing: (@DC)
MOS - n-channel

small signal gain $\approx g_m R_L$

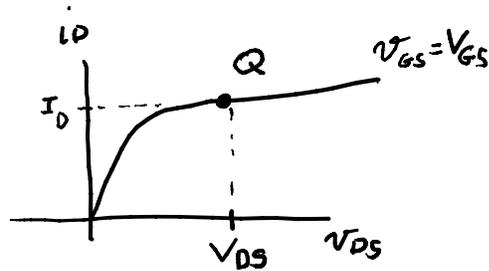

bias in saturation

$$I_D = \frac{K_P W}{2 L} (V_{GS} - V_{TO})^2 (1 + \lambda V_{DS})$$
ignore @ start

assume $K_P = 2 \times 10^{-5} \text{ A/V}^2$, $W/L = 20$, $V_{TO} = 1.2 \text{ V}$, $\lambda = 10 \times 10^{-3} \frac{1}{\text{V}}$

$k = \frac{K_P W}{2 L} = \frac{2 \times 10^{-5}}{2} \times 20 = 2 \times 10^{-4}$

choose $V_{GS} = 3.2 \text{ V}$, $V_{GS} - V_{TO} = 2$, $(V_{GS} - V_{TO})^2 = 4$

$I_D = k (V_{GS} - V_{TO})^2 = 2 \times 10^{-4} \times 4 = 0.8 \times 10^{-3} = 0.8 \text{ mA}$

$R_S = 1 \text{ k}\Omega = 10^3 \Omega$, $V_{RS} = R_S \times I_D = 10^3 \times 0.8 \times 10^{-3} = 0.8 \text{ V}$

$V_{RL} = R_L \cdot I_D$; fix R_L from the gain:

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_Q = \frac{2 I_D}{V_{GS} - V_{TO}} = \frac{2 \times 0.8 \times 10^{-3}}{2} = 0.8 \text{ mS}$$

$A_v \approx g_m R_L$; choose $A_v = \frac{v_o}{v_i}$ for small signal

$\Rightarrow g_m R_L = 4$; $R_L = \frac{4}{0.8 \times 10^{-3}} = \frac{4 \times 10^3}{0.8}$


$= 5 \text{ k}\Omega$

$V_{RL} = R_L I_D = 5 \times 10^3 \times 0.8 \times 10^{-3} = 4 \text{ V}$


for M in saturation
need $V_{DS} > V_{GS} - V_{TO} = 2$

$V_{DS} = V_{DD} - 4 - 0.8 = V_{DD} - 4.8 > 2$

$V_{DD} > 6.8$

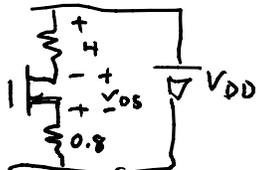

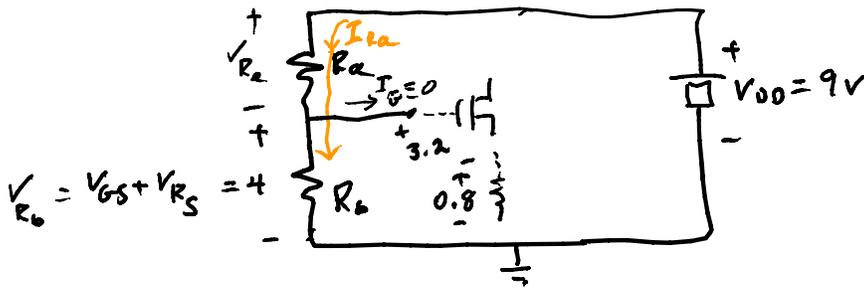Choose $V_{DD} = 9V$; need $V_{GS} = 3.2$ so now design R_a, R_b



$$V_{R_b} = V_{GS} + V_{RS} = 4$$

$$\left. \begin{aligned} V_{R_b} &= R_b \cdot I_{R_a} = 4 \\ V_{R_a} &= R_a \cdot I_{R_a} = V_{DD} - V_{R_b} = 9 - 4 = 5 \end{aligned} \right\} \frac{4}{5} = \frac{R_b I_{R_a}}{R_a I_{R_a}} = \frac{R_b}{R_a}$$


$\therefore R_b = \frac{4}{5} R_a$ choose R_a , say $R_a = 1 \text{ Meg } \Omega = 10^6$
 $R_b = \frac{4}{5} \text{ Meg } \Omega = 800 \text{ k } \Omega$

Effect of the Early voltage $\frac{1}{\lambda}$

$$\begin{aligned} \lambda V_{DS} &= 10 \times 10^{-3} \times 4.2, & V_{DS} &= V_{DD} - 4.8 = 9 - 4.8 \\ &= 4.2 \times 10^{-2} & &= 4.2 \text{ V} \\ &= 0.042 \end{aligned}$$


gives an increase of I_D by 0.042

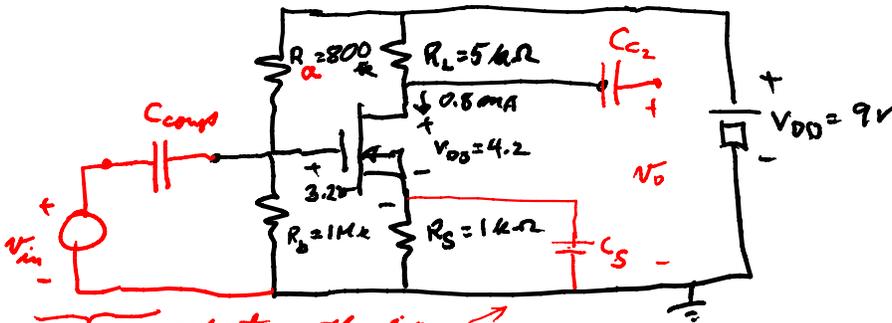Best to go into SPICE & do parametric runs to adjust to desired.



does not destroy the bias \rightarrow

R_s stabilizes w.r.t changes in I_D

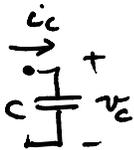


$$i_c = C \frac{dv_c}{dt} \quad \text{for bias } \frac{dv_c}{dt} = 0 \text{ as @ DC}$$

for bias $i_c = 0 \Rightarrow$ an open circuit for bias

for sine waves $I_c = j\omega C V_c$ acts as a short for high enough frequencies

Biasing for BJT: n-p-n

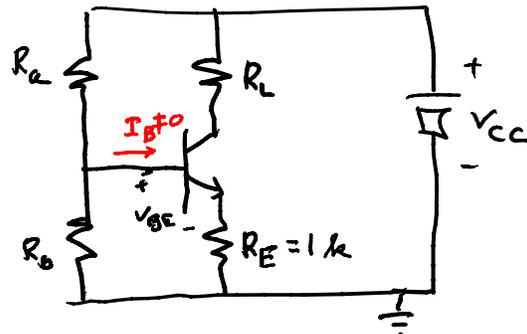

bias in forward active region
 $\Rightarrow V_{BE} \approx 0.7V$

$$A_v \approx g_m R_L \quad ; \quad g_m = \frac{I_c}{V_T} \quad \text{assume } I_c = 0.8 \times 10^{-3} A$$

$$V_T = 0.026 = 26 \times 10^{-3}$$

$$= \frac{8 \times 10^{-4}}{26 \times 10^{-3}} = 3.07 \times 10^{-2} = 30.7 \times 10^{-3} \Omega^{-1}$$

assume $A_v = 4 \Rightarrow R_L = \frac{4}{3.07 \times 10^{-2}} = 1.3 \times 10^2 = 130 \Omega$


need I_B , $I_c = \beta I_B$ assume $\beta = 400$ close 2

$$I_B = \frac{0.8 \times 10^{-3}}{400} = \frac{8 \times 10^{-4}}{4 \times 10^2} = 2 \times 10^{-6} = 2 \mu A$$

Q2N3904
 ↑
 npn

to choose R_a & R_b

choose $V_{DD} = 9V$

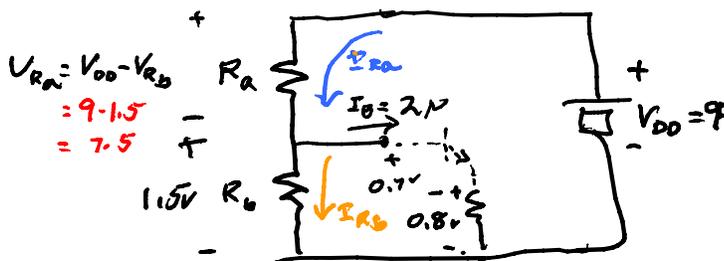

$$V_{R_a} = V_{DD} - V_{R_b}$$

$$= 9 - 1.5$$

$$= 7.5$$

$$I_{R_a} = I_B + I_{R_b}$$

$$= 2 \times 10^{-6} + \frac{1.5}{R_b}$$

$$= \frac{7.5}{R_a}$$

Choose $R_b = 1M\Omega \Rightarrow \frac{7.5}{R_a} = (2 + 1.5) \times 10^{-6} = 3.5 \times 10^{-6}$

$$\Rightarrow R_a = \frac{7.5}{3.5} \times 10^6 = 2.14M\Omega$$