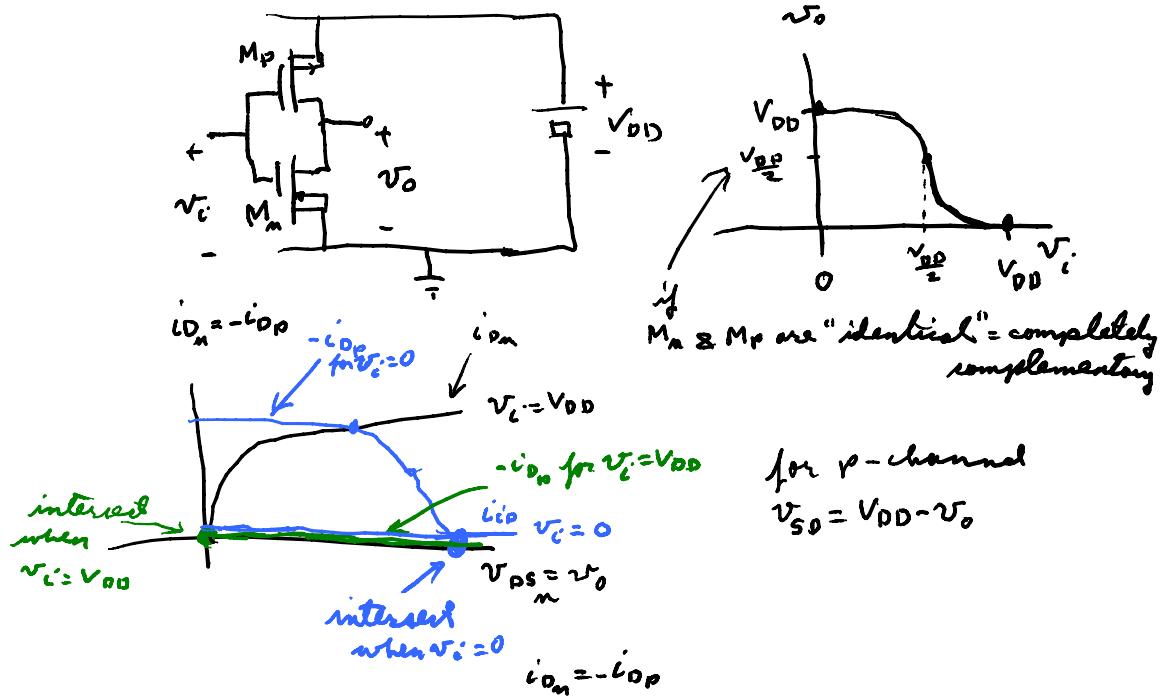



P. 338 inverters (CMOS)

EE303
02/25/10




When $v_i \neq 0$ or V_{DD}


v_i

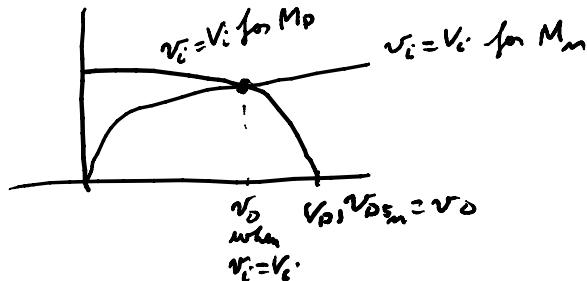

for no Early effect

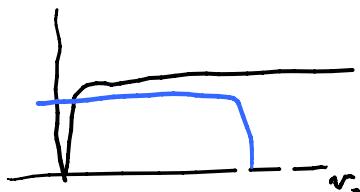


Look at switching time:

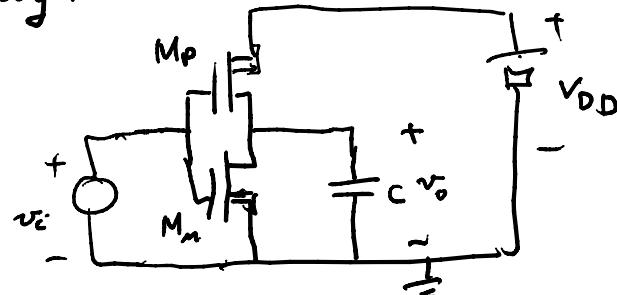

assume $v_i(t)$ is a pulse

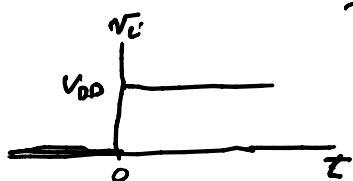assume at $t = 0$ $v_i(0-) = 0$ (for a long time for $t < 0$)
 $v_i(0+) = V_{DD} \Rightarrow C$ was charged to V_{DD}



$$v_o(0-) = V_{DD}$$

$$v_o(0+) = V_{DD} \text{ as assume no impulse}$$

$$i(t) = C \frac{dv_o}{dt}$$

$$-i_o(0+) = 0 \text{ as } M_p \text{ is turned off}$$

$$(V_{SG} - V_{TO}) < 0$$

\Rightarrow discharge of capacitor C through M_m

$$i_{Dm} \\ \text{initially } t > 0_+$$

$$\text{check } v_{GS} - V_{TO} \text{ vs } v_{DS} = v_o$$

$$@ t=0_+ \quad " \quad " \quad V_{DD} - V_{TO} \quad V_{DD}$$

\Rightarrow in saturation as $v_{GS} - V_{TO} < v_{DS}$

remains in saturation until
 v_{DS} decreases to $V_{DD} - V_{TO}$

i.e. the differential equation for the time interval
 for when M_m is in saturation is

$$I_D = i_{Dm} = \frac{K_P w}{2} \frac{1}{L} (V_{DD} - V_{TO})^2 = -C \frac{dv_o}{dt}$$

$$dv_o = -\frac{1}{C} I_D \cdot dt \Rightarrow dt = -\frac{C}{I_D} dv_o$$

$$\text{integrate } \int_0^{t_1} dt = -\frac{C}{I_D} \int_{v_o(0)}^{v_o(t_1)} dv_o$$

$$t_1 = -\frac{C}{I_D} [(V_{DD} - V_{TO}) - V_{DD}] = \frac{C V_{TO}}{I_D}$$

at t_1 , M_m changes to the Ohmic state,
 $v_{GS} - V_{TO} = V_{DD} - V_{TO} \geq v_{DS}$

then $i_{Dm} = \frac{K_P w}{2} \frac{1}{L} (2(V_{DD} - V_{TO}) v_{DS} - v_{DS}^2) = \text{Ohmic region law}$

$$= -C \frac{dv_o}{dt}$$

$$dv_o = -\frac{K_P w}{2C} \frac{1}{L} (2(V_{DD} - V_{TO}) v_o - v_o^2) dt ; b, a = \frac{K_P w}{2} \frac{1}{L} \frac{1}{C}$$

$$ab = 2(V_{DD} - V_{TO})$$

$$v_o = x$$

$$dt = -\frac{dx}{b(ax - x^2)}$$

$$\int_{t_1}^{t_2} dt = \frac{1}{b} \int_{x(t_1)}^{x(t_2)} \frac{dx}{x^2 - ax} = \frac{1}{b} \int_{x(t_1)}^{x(t_2)} \frac{dx}{x(x-a)}$$

$$t_2 - t_1 = \frac{1}{b} \int_{v_o(t_1)}^{v_o(t_2)} dx \left[\frac{-1/a}{x} + \frac{1/a}{x-a} \right] = \frac{1}{b} \int_{v_o(t_1)}^{v_o(t_2)} -\frac{1}{a} \frac{dx}{x} + \frac{1}{b} \int_{v_o(t_1)}^{v_o(t_2)-a} \frac{dx}{a} \frac{1}{x-a}$$

$$\frac{1}{x(x-a)} = \frac{kx_1}{x} + \frac{kx_2}{x-a}$$

$$k_1, 2 \left(\frac{x}{x(x-a)} - \frac{k_2 x}{x-a} \right) \Big|_{x=0} = \frac{1}{-a}$$

$$k_2 = \left(\frac{(x-a)}{x(x-a)} - \frac{k_1(x-a)}{x} \right) \Big|_{x=a} = \frac{1}{a}$$

$$\int \frac{dx}{x};$$

$$x = \ln e^x; \frac{dx}{dx} = \frac{d \ln y}{dy} \cdot \frac{dy}{dx}; y = e^x$$

$$1 = \frac{d \ln y}{dy} \cdot e^x = \frac{d \ln y}{dy} \cdot y \Rightarrow \frac{1}{y} = \frac{d \ln y}{dy}$$

$$\Rightarrow \frac{dy}{y} = d \ln y$$

$$t_2 - t_1 = \frac{-1}{ab} \ln x \Big|_{x=v_o(t_1)}^{v_o(t_2)} + \frac{1}{ab} \ln(x-a) \Big|_{x=v_o(t_1)}^{v_o(t_2)-a}$$

$$= \frac{1}{ab} \ln \left(\frac{x-a}{x} \right) \Big|_{x=v_o(t_1)}^{v_o(t_2)}, \quad t_2 > t_1$$

$$= \frac{1}{\frac{K_p w}{2} \frac{2(V_{DD}-V_{TO})}{C}}, \left[\ln \left(1 - \frac{2(V_{DD}-V_{TO})}{V_o(t_2)} \right) - \ln \left(1 - \frac{2(V_{DD}-V_{TO})}{V_o(t_1)} \right) \right]$$

as $\ln(-1)$ is complex number terms

united

$$= \frac{1}{\frac{K_p w}{2} \frac{2(V_{DD}-V_{TO})}{C}} \ln \left[\frac{2(V_{DD}-V_{TO})}{V_o(t_2)} - 1 \right]$$

We are interested in $v_o(t_2) = 0$ but never reach (get $\ln(\infty)$) so evaluate to get delay to $v_o(t_2) = V_{DD}/2$, as per the book.
also can get fall time, usually 0.90 to 0.1 of V_{DD}