
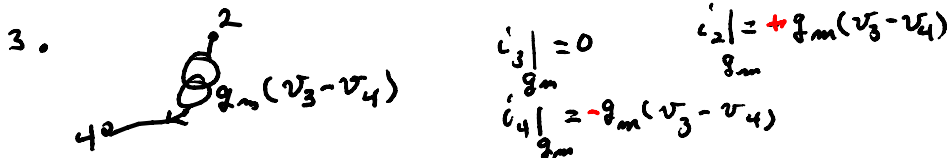


$$i = Y_{ind} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix}$$

for $y_{13} = \frac{i_1}{v_3} \Big|_{v_1=v_2=v_4=v_5=0} = y_{31}$ by reciprocity

$$y_{11} = y_{33} = \frac{i_3}{v_3} \Big|_{v_1=v_2=v_4=v_5=0} = AC$$

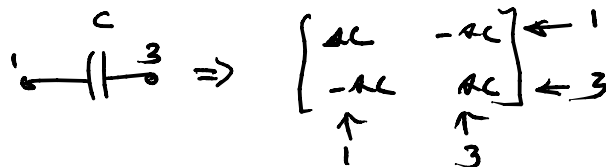

$$\begin{matrix} 2 \rightarrow \\ 3 \rightarrow \\ 4 \rightarrow \end{matrix} \begin{bmatrix} 0 & g_m & -g_m \\ 0 & 0 & 0 \\ 0 & -g_m & g_m \end{bmatrix}$$

ind = indefinite
 $Y_{ind} \downarrow$
 Y_{dep} (4x4)
 ground \rightarrow node 5

1	2	3	4	5
\downarrow	\downarrow	\uparrow	\uparrow	\downarrow
\uparrow	\uparrow	\uparrow	\downarrow	\downarrow
1	2	3	4	5
\leftarrow	\leftarrow	\leftarrow	\leftarrow	\leftarrow
\leftarrow	\leftarrow	\leftarrow	\leftarrow	\leftarrow
\leftarrow	\leftarrow	\leftarrow	\leftarrow	\leftarrow
\leftarrow	\leftarrow	\leftarrow	\leftarrow	\leftarrow
\leftarrow	\leftarrow	\leftarrow	\leftarrow	\leftarrow

for Y_{ind} , sum of entries in a row & in a column = 0
 set $v_5 = 0 \Rightarrow$ can delete column 5 as entries multiply v_5

Now have $\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = Y_{def} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix}$ $Y_{def} = Y_{ind}$ after quad nodes 5
 \Rightarrow removed row 5 & col. 5

want these = 0 $\begin{bmatrix} i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$; $\begin{bmatrix} v_3 \\ v_4 \end{bmatrix} \neq 0$

$$\begin{bmatrix} i_1 \\ i_2 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \end{bmatrix} \quad Y_{ij} \text{ all } 2 \times 2$$

solve for $\begin{bmatrix} v_3 \\ v_4 \end{bmatrix} \Rightarrow \begin{bmatrix} 0 \\ 0 \end{bmatrix} = Y_{21} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + Y_{22} \begin{bmatrix} v_3 \\ v_4 \end{bmatrix}$

$$\begin{bmatrix} v_3 \\ v_4 \end{bmatrix} = Y_{22}^{-1} \left\{ \begin{bmatrix} 0 \\ 0 \end{bmatrix} - Y_{21} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \right\} = -Y_{22}^{-1} Y_{21} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

into 1st 2 rows

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = Y_{11} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + Y_{12} \begin{bmatrix} v_3 \\ v_4 \end{bmatrix} = Y_{11} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} + Y_{12} \left\{ -Y_{22}^{-1} Y_{21} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} \right\}$$

$$= \left\{ Y_{11} - Y_{12} Y_{22}^{-1} Y_{21} \right\} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = Y_{2-port} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$Y_{2-port} = Y_{11} - Y_{12} Y_{22}^{-1} Y_{21}$$

$$Y_{11} = \begin{bmatrix} sC_c & 0 \\ 0 & sC_{g1} + g_0 + G_c \end{bmatrix} \quad Y_{12} = \begin{bmatrix} -sC_c & 0 \\ -sC_{g1} + g_m & -g_0 - g_m \end{bmatrix}$$

$$Y_{21} = \begin{bmatrix} sC_c & -sC_{g1} \\ 0 & g_0 \end{bmatrix} \quad Y_{22} = \begin{bmatrix} sC_c + sC_{g1} + sC_{g2} & -sC_{g2} \\ -sC_{g2} & g_0 + sC_{g2} + g_m + sC_s + G_s \end{bmatrix}$$

need $Y_{22}^{-1} = \frac{1}{\Delta} \begin{bmatrix} g_0 + sC_{g2} & +sC_{g2} \\ +g_m + sC_s + G_s & sC_c + sC_{g1} + sC_{g2} \end{bmatrix}$

$$\Delta = \text{determinant of } Y_{22} = s(C_c + C_{g1} + C_{g2})(g_0 + G_s + g_m + sC_s) - (-sC_{g2})(-sC_{g2} - g_m)$$

$\Delta = \text{degree 2 polynomial in } s$

$$Y_{2-port} = \begin{bmatrix} sC_c & 0 \\ 0 & g_0 + G_L + sC_{gd} \end{bmatrix} - \frac{1}{\Delta} \begin{bmatrix} -sC_c & -sC_{gd} \\ 0 & g_d \end{bmatrix} \begin{bmatrix} g_0 + sC_{gs} & sC_{gs} \\ sC_{gs} + G_S + G_3 & 2C_{gs} + g_m \\ 2C_{gs} + g_m & 2(C_c + C_{gs} + C_{gd}) \end{bmatrix}$$

$$X = \begin{bmatrix} -sC_c & 0 \\ -sC_{gs} + g_m & -g_0 - g_m \end{bmatrix}$$

to get voltage gain $v_0/v_{in} = \frac{v_2}{v_1}$

$$Y_{2-port} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \quad \begin{matrix} i_2 = 0 \text{ if no} \\ \text{load} \\ \Rightarrow = \text{open circuit} \\ \text{voltage gain} \end{matrix}$$

$$i_2 = 0 \Rightarrow y_{21} v_1 + y_{22} v_2 = 0$$

$$v_2 = -\frac{y_{21}}{y_{22}} v_1 \Rightarrow A_v = \frac{v_2}{v_1} \Big|_{\text{no load}} = -\frac{y_{21}}{y_{22}}$$

$$0 = \begin{bmatrix} g_0 + G_L + sC_{gd} \\ 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} - \frac{1}{\Delta} \begin{bmatrix} 0 & 0 \\ 0 & g_d \end{bmatrix} \begin{bmatrix} 0 & 0 \\ sC_{gs} & 2(C_c + C_{gs} + C_{gd}) \end{bmatrix} \begin{bmatrix} -sC_c & 0 \\ -sC_{gs} + g_m & -g_0 - g_m \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$y_{21} = 0 - g_d \frac{(-sC_c + s(C_c + C_{gs} + C_{gd}))(-sC_{gs} + g_m)}{\Delta}$$

$$y_{22} = \left\{ (g_0 + G_L + sC_{gd}) \Delta + (-g_d)(-g_0 - g_m)(s(C_c + C_{gs} + C_{gd})) \right\} / \Delta$$

$$A_v = \frac{\text{degree three in numerator (in } s)}{\text{degree three in denominator (in } s)}$$

in summary: can carry out these steps

- 1) draw small signal equivalent circuit [which is "linear"]
- 2) move ground off of circuit
- 3) bring out leads from all nodes
- 4) use variables, i, v , from ground to nodes & write indefinite admittance, $Y_{ind}^{(n)}$, by inspection [it also has sums of row & of column entries to 0]
- 5) move the ground to a circuit node

(This removes a column [as its $v=0$] and a row [as its current is a combination of others by KCL])

This gives a "definite" admittance, Y_{def}

- 6) If some nodes do not have access externally, eliminate their rows & columns by setting their currents to zero. By numbering them

$$\text{last } Y_{ports} = Y_{11} - Y_{12} Y_{22}^{-1} Y_{21} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}$$

- 7) If there are two ports the y_{ij} are 1×1 matrices and

$$A_v = -\frac{y_{21}}{y_{22}} = \frac{V_{out}}{V_{in}} = \text{open circuit voltage gain when no load}$$

$$A_i = -\frac{y_{21}}{y_{11}} = -\frac{i_2}{i_1} = \text{short circuit current gain}$$