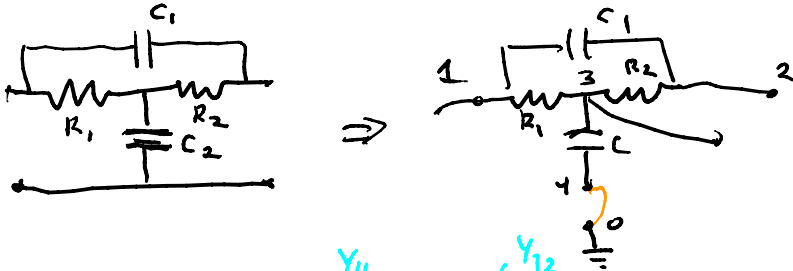


EE303
03/09/10




$$Y_{ind} = \begin{bmatrix} AC_1 + G_1 & -AC_1 & 0 & 0 \\ -AC_1 & G_2 + AC_1 & -G_2 & 0 \\ -G_1 & -G_2 & G_1 + G_2 & -AC_2 \\ 0 & 0 & -AC_2 & AC_2 + G_2 \end{bmatrix}$$


$$Y_{2-port} = Y_{11} - Y_{12} Y_{22}^{-1} Y_{21}$$

$$= \begin{bmatrix} AC_1 + G_1 & -AC_1 \\ -AC_1 & G_2 + AC_1 \end{bmatrix} - \begin{bmatrix} -G_1 \\ -G_2 \end{bmatrix} \frac{1}{G_1 + G_2 + AC_2} \begin{bmatrix} -G_1 & -G_2 \end{bmatrix}$$

p. 967 = NOR gate made with inverters

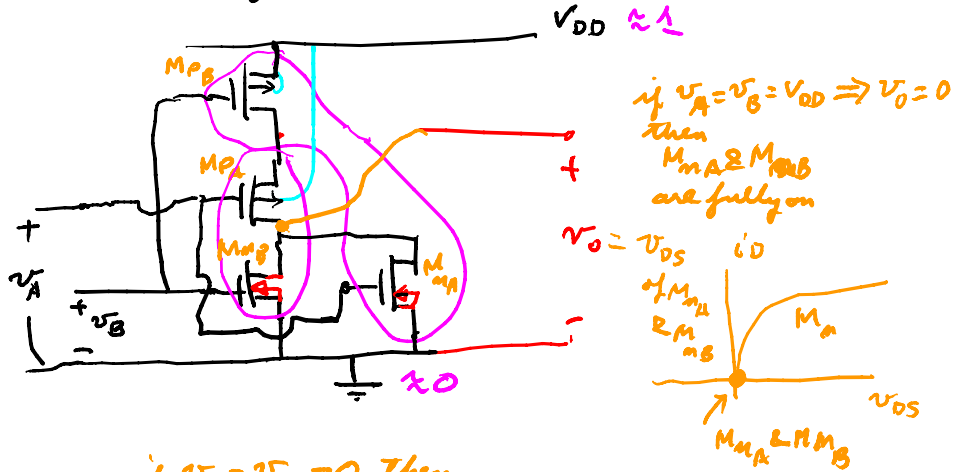

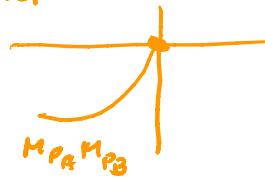if $V_A = V_B = 0$ then
 $M_{NA} \& M_{NB}$ have no current
but $M_{PA} \& M_{PB}$ are on
 $\Rightarrow V_O = V_{DD}$



if $V_A = 1, V_B = 0$ then

M_{NA} is off

M_{PB} is on




$M_{NA} = \text{off}$

but with no current as M_{PA} is off

then $V_O = 0$


P. 982 = pass transistor

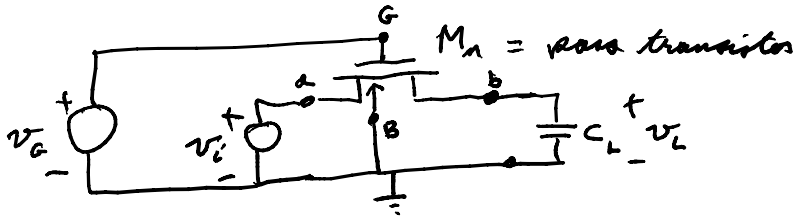


If $v_L = 0$ at $t = 0$ then M_n will switch
 & $v_i = V_{DD}$ at $t = 0$ on if $v_G = V_{DD}$

as $v_{G_b} > V_{TO}$

& then v_i attaches to v_L

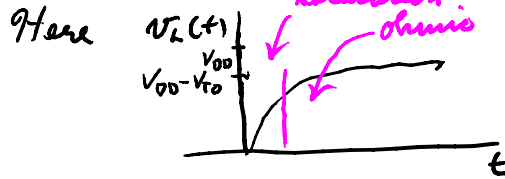

P. 1054 = latch

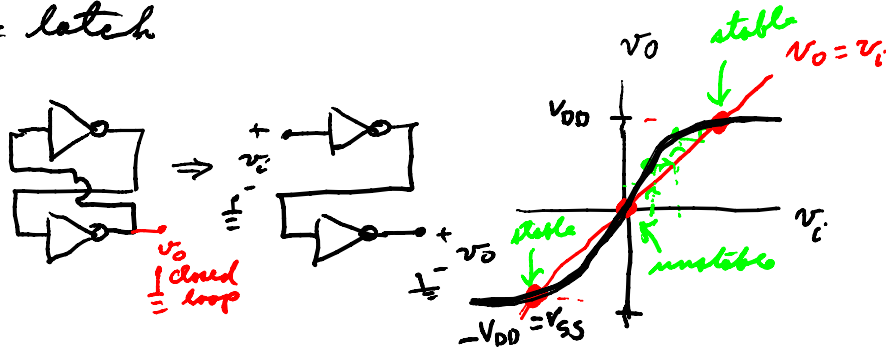

When close the loop $v_o = v_i$

To turn into a flip-flop, make the inverters with nor gates

