
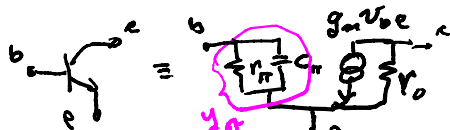
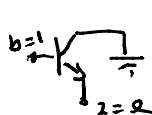


pp. 484-485 Common b, c, e  $\Rightarrow$  CB, CC, CE

EE303  
03/11/10  $g_m(v_b - v_e)$

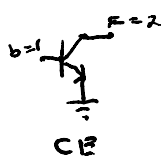

$y_{in} = y_{\pi} = \frac{1}{r_{\pi}} + g_m$

$g_m = \frac{I_C}{V_T}$   
 $g_{\pi} = g_m / \beta = 1/r_{\pi}$   
 $g_o = \frac{V_T}{V_A} \cdot g_m = 1/r_o$

Y<sub>ind</sub> =

	b	c	e
b	0	0	-g <sub>m</sub>
c	g <sub>m</sub>	g <sub>o</sub>	-g <sub>m</sub>
e	-g <sub>m</sub>	0	g <sub>o</sub> + g <sub>m</sub>




$i_b + i_c + i_e = 0$  by KCL  
 $\Rightarrow$  entries in a column = 0


$$i = \begin{bmatrix} i_b \\ i_c \\ i_e \end{bmatrix} = Y_{ind} \begin{bmatrix} v_b + E \\ v_c + E \\ v_e + E \end{bmatrix}$$

$$= Y_{ind} \begin{bmatrix} v_b \\ v_c \\ v_e \end{bmatrix} + Y_{ind} \begin{bmatrix} E \\ E \\ E \end{bmatrix}$$

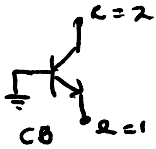
$$= 0$$
 $\Rightarrow$  sum of entries in row = 0



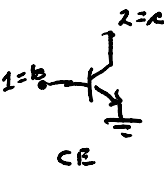
$Y_{CB} = \begin{bmatrix} g_o & -g_m - g_o \\ -g_o & g_o + g_{\pi} + g_m \end{bmatrix}$



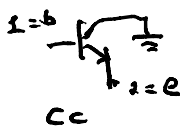$Y_{CE} = \begin{bmatrix} g_{\pi} & 0 \\ g_m & g_o \end{bmatrix}$



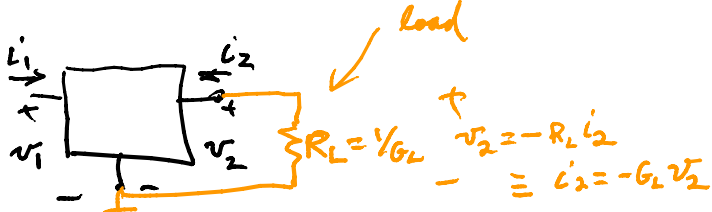$Y_{CC} = \begin{bmatrix} g_{\pi} & -g_{\pi} \\ -g_m & g_m + g_o + g_{\pi} \end{bmatrix}$






$Y = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \Rightarrow \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$

to get voltage gain when load in  $G_L$


last row  $i_2 = -G_L v_2 = y_{21} v_1 + y_{22} v_2$


and  $i_1 = y_{11} v_1 + y_{12} \left( -\frac{y_{21}}{G_L + y_{22}} \right) v_1 \Rightarrow y_{in} = y_{11} - \frac{y_{12} y_{21}}{G_L + y_{22}}$

$$\frac{v_2}{v_1} = A_v \Big|_{\text{loaded}} = \frac{-y_{21}}{y_{22} + G_L} ; \text{ for } \frac{i_2}{v_2} = \frac{y_{21}}{y_{11}} = A_i$$

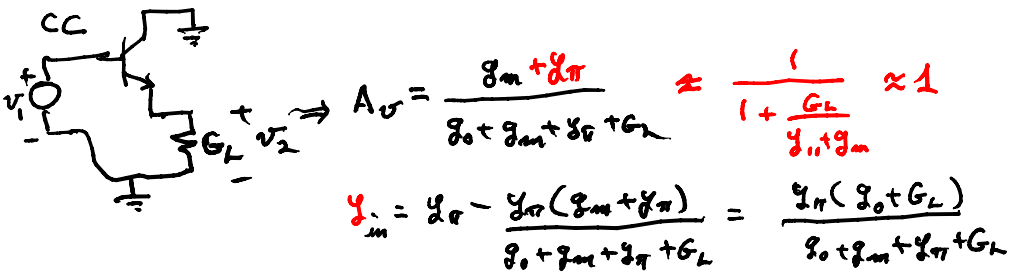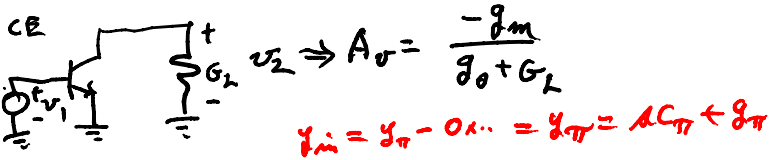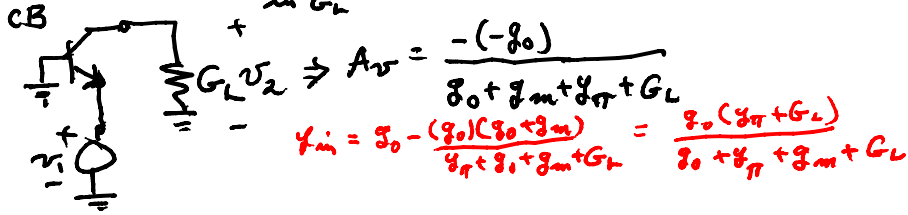

P.1187 = hysteresis

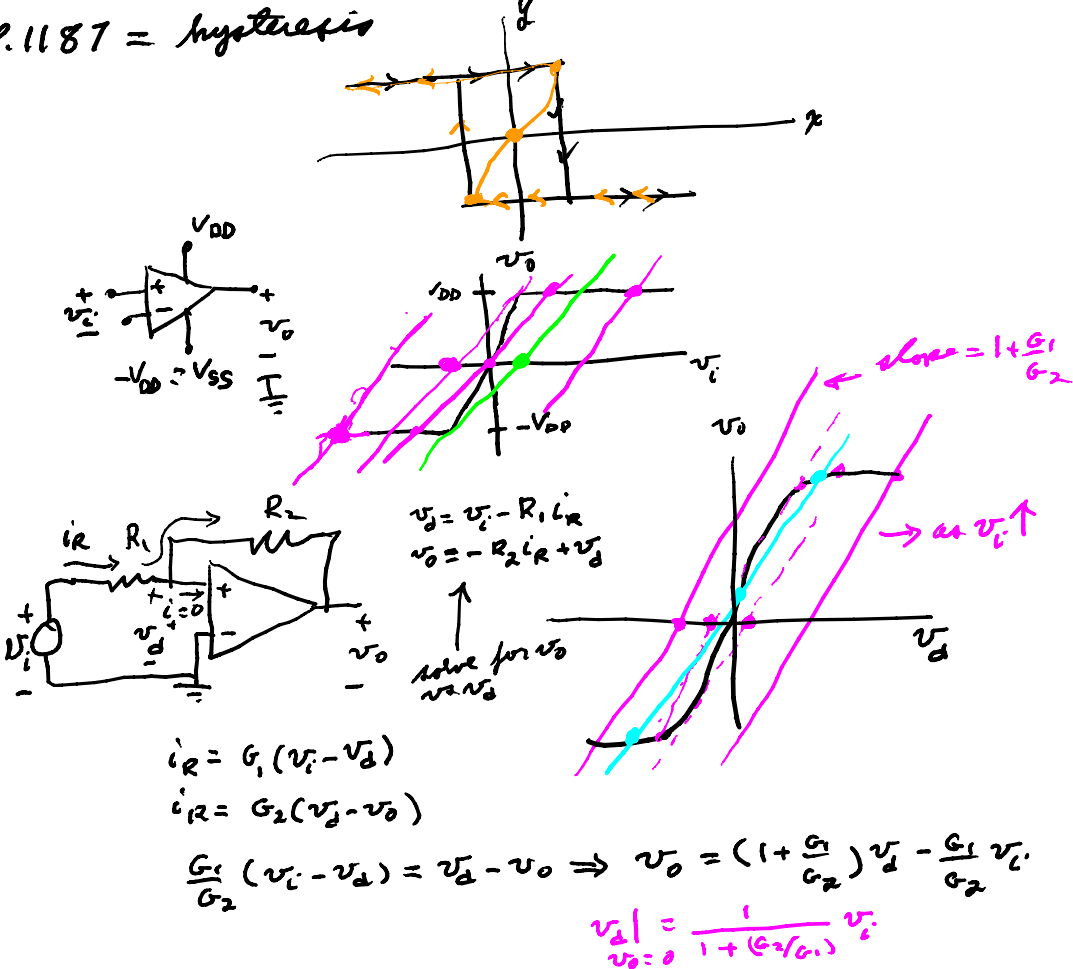

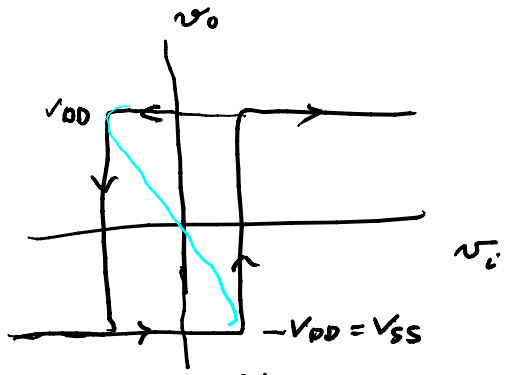

Schmitt trigger