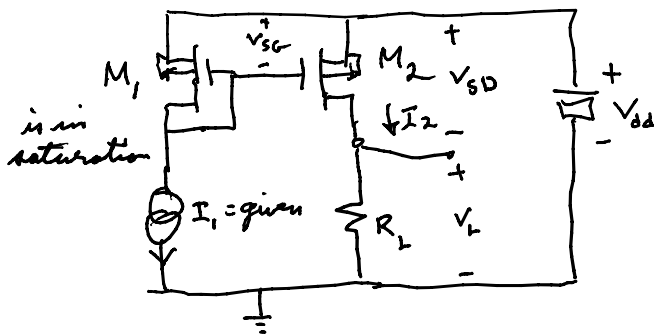


Exam next period
open book open notes calculator

EE303
03/23/10
Corrected

current mirrors = CMOS
biasing of BJT's
small signal equivalents
Y matrix
CMOS equations
bulk use for VTO adjust
poles & zeros
inverters

current mirror



assume $M_1 = M_2$

Here $I_2 = I_1$ if $V_{dd} - V_L \geq V_{sg} - |V_{T0}|$

$$V_{sg} \Rightarrow I_1 = I_{SD} = \frac{K_P W}{2 L} (V_{sg} - |V_{T0}|)^2$$

$$V_{sg} = |V_{T0}| + \sqrt{\frac{I_1}{\frac{K_P W}{2 L}}}$$

choice of \pm as M_1 on if $I_1 > 0$

$$V_{dd} - V_L \stackrel{P}{\geq} V_{sg} - |V_{T0}| = \sqrt{\frac{I_1}{\frac{K_P W}{2 L}}}$$

if M_2 is in saturation $V_L = R_L I_2$


$$\begin{aligned} &= R_L \frac{K_P W}{2 L} (V_{sg} - |V_{T0}|)^2 \\ &= R_L I_1 \end{aligned}$$

$V_{dd} - R_L I_1$


\therefore have a good current mirror ($I_2 = I_1$)

$$V_{dd} - R_L I_1 \geq \sqrt{\frac{I_1}{\frac{K_P W}{2 L}}}$$

\therefore require R_L small enough

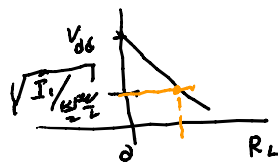


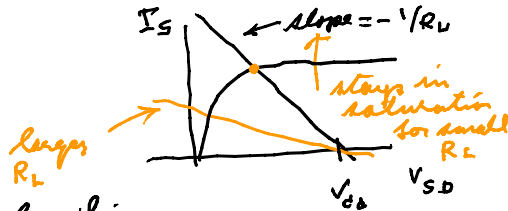
$$\frac{V_{dd} - \sqrt{\frac{I_1}{\frac{K_P W}{2L}}}}{I_1} \gg R_L$$




Boundary ohmic vs saturation

$$V_{SG} - |V_{T0}| = V_{SD} ; I_S = \frac{K_P W}{2L} (V_{SG} - |V_{T0}|)^2$$

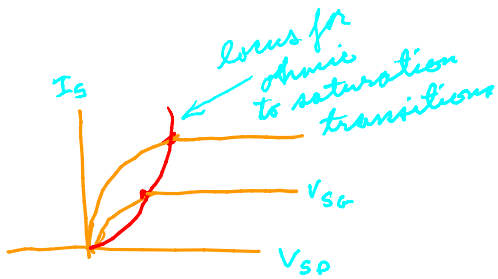
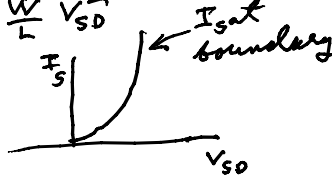
at boundary = $\frac{K_P W}{2L} V_{SD}^2$




Inserting signal

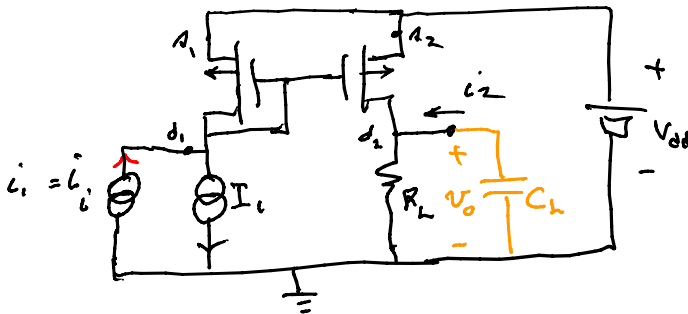

for signal

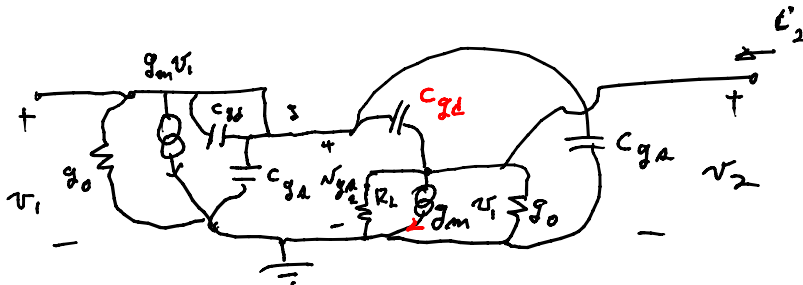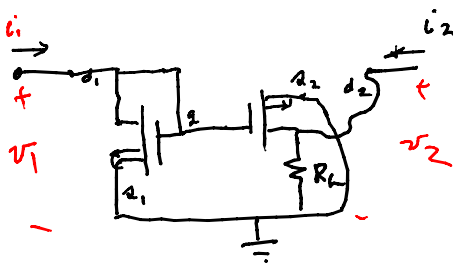

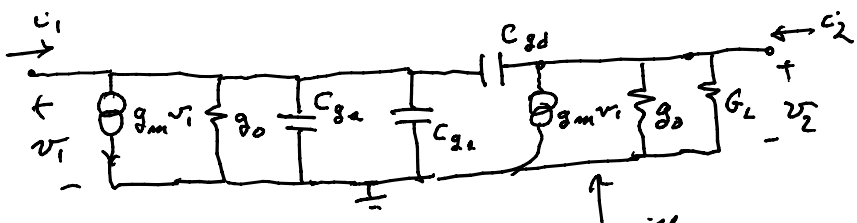

$$y_{11} = g_0 + g_m + s(2C_{gs} + C_{gd})$$

$$y_{12} = -sC_{gd}; \quad y_{21} = g_m - sC_{gd}$$

$$y_{22} = g_0 + G_L + sC_{gd} = \frac{i_2}{v_2} \Big|_{v_1=0}$$

$$Y(s) = \begin{bmatrix} (g_0 + g_m) + s(2C_{gs} + C_{gd}) & -sC_{gd} \\ g_m - sC_{gd} & (g_0 + G_L) + sC_{gd} \end{bmatrix}$$


$$= s \begin{bmatrix} 2C_{gs} + C_{gd} & -C_{gd} \\ -C_{gd} & C_{gd} \end{bmatrix} + \begin{bmatrix} g_0 + g_m & 0 \\ g_m & g_0 + G_L \end{bmatrix}$$

If load in C_L , derive v_2/v_1


$$-i_2 = C_L s v_2$$

$$-C_L s v_2 = i_2 = (g_m - sC_{gd})v_1 + [(g_0 + G_L) + sC_{gd}]v_2$$
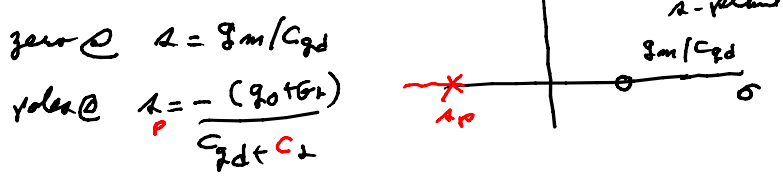
$$\frac{v_2}{v_1} = -\frac{(g_m - sC_{gd})}{(g_0 + G_L) + s(C_{gd} + C_L)}; \quad DC \text{ gain} = \frac{v_2}{v_1}(s=0) = -\frac{g_m}{g_0 + G_L}$$



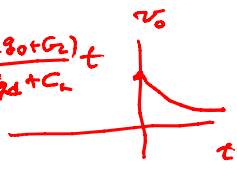if $v_i = e^{-s_0 t} \Rightarrow$ "infinite" output "gain" \equiv 0 input $\Rightarrow \neq 0$ output
 if $v_i = e^{(g_m/C_{gs})t} \Rightarrow v_o = 0$
 natural response is $e^{s_0 t} = e^{-\frac{(g_0 + G_L)t}{C_{gd} + C_L}}$




matching of NMOS & PMOS

$$I_{Dn} = \frac{K_P}{2} \left(\frac{W}{L}\right)_n (V_{GS} - V_{Thn})^2$$


$$I_{Sp} = \frac{K_P}{2} \left(\frac{W}{L}\right)_p (V_{GS} - |V_{Thp}|)^2 \quad V_{Thn} \leq |V_{Thp}|$$

$$V_{TOP} = V_{th_m} = V_{TO_m} + \underbrace{\gamma [\sqrt{\phi_s + V_{SB}} - \sqrt{\phi_s}]}_{\text{can be } > 0}$$

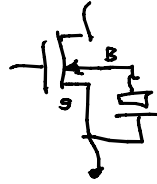by choice of V_{SB} can usually get $V_{th_m} = V_{TOP}$



Biasing:

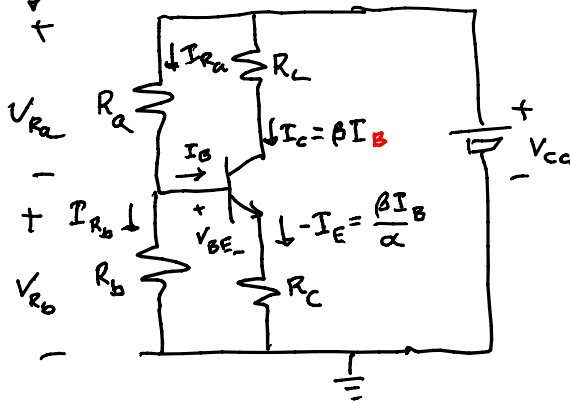

$$V_{BE} = 0.7$$

$$I_{R_a} = I_B + I_{R_b}$$

$$V_{R_b} = R_b I_{R_b} = V_{BE} + R_c \frac{\beta I_B}{\alpha}$$

$$V_{cc} = V_{R_a} + V_{R_b}$$

$$= R_a I_{R_a} + V_{R_b}$$


$$= R_a I_B + R_a I_{R_b} + V_{R_b}$$

correction \rightarrow

$$= R_a I_B + \underbrace{\frac{R_a V_{R_b}}{R_b}}_{(1 + \frac{R_a}{R_b}) V_{BE} + R_c (1 + \beta) I_B} \quad \text{let } r_{ab} = \frac{R_a}{R_b}$$

$$\Rightarrow I_B = \frac{V_{cc} - (1 + r_{ab}) V_{BE}}{R_a + R_c (1 + \beta) [1 + r_{ab}]}, \quad I_C = \beta I_B$$

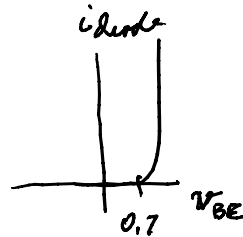From this if given R 's can determine the Q point or if given Q point can solve for R 's



$$\beta = \frac{\alpha}{1 - \alpha}$$

$$\alpha = \frac{\beta}{1 + \beta}$$

$$\frac{\beta}{\alpha} = 1 + \beta$$