

Final exam: open books, notes
part take home

- Topics
- current mirrors
 - small signal
 - biasing
 - inverters
 - poles-zeros
 - oscillator
 - BJT & CMOS
 - op-amp, OTA

Review:


electronics can mimic if scale almost anything

Main devices, R, L, C, BJT, CMOS, diodes
all describe by models & use Spice
need the mathematical models

put into systems

2-port descriptions
if "linear" use Taylor series
need Q point, need to bias

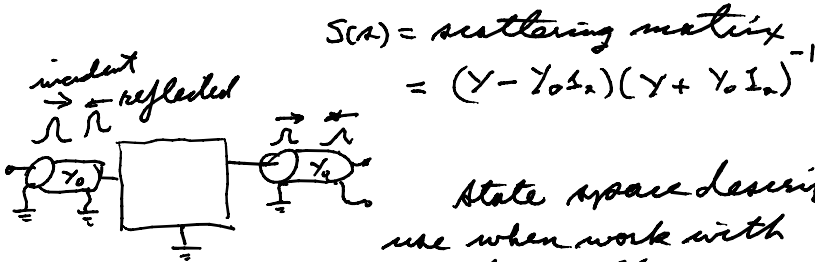
small signal
 $i = Y(s)v$, $Y(s) = \text{admittance matrix}$
 $Z(s) = Y^{-1}(s)$




State space descriptions
use when work with nonlinearities

from cap $\rightarrow \dot{x} = A(x) + Bu$ $x = \text{state-vector}$
 $y = Cx + Du$

Ex: Colpitts oscillator p. 1179

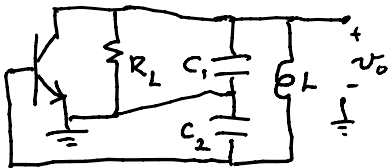


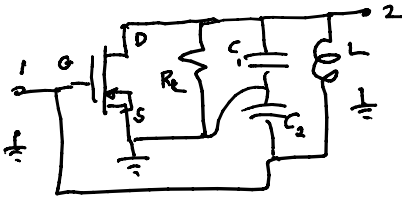


for bias to allow signal to pass

C large $\left\{ \begin{array}{l} \text{bias open} \\ \text{signal short} \end{array} \right.$

L large $\left\{ \begin{array}{l} \text{bias short} \\ \text{signal open} \end{array} \right.$
 an RFC = radio frequency choke

for small signal

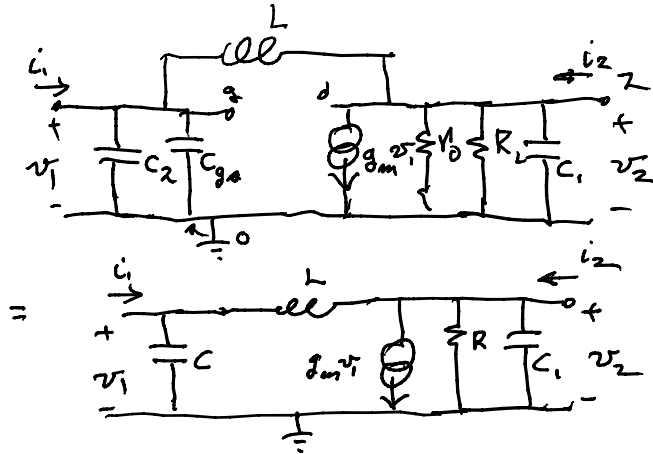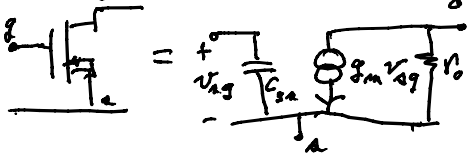

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} \alpha C + \frac{1}{sL} & -\frac{1}{sL} \\ g_m - \frac{1}{sL} & \alpha C_1 + \frac{1}{sL} + G \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}; \quad i = Yv \quad \begin{array}{l} G = 1/R \\ G = g_m + G_L \\ G_L = 1/R_L \end{array}$$

$$\begin{aligned} \det Y(s) &= (\alpha C + \frac{1}{sL})(\alpha C_1 + \frac{1}{sL} + G) - (g_m - \frac{1}{sL})(-\frac{1}{sL}) \\ &= \alpha^2 C C_1 + \frac{C}{L} + \alpha C G + \frac{C_1}{L} + \frac{1}{s^2 L^2} + \frac{G}{\alpha L} + \frac{g_m}{\alpha L} - \frac{1}{s^2 L^2} \\ &= \frac{1}{s^2 L^2} \{ \alpha^3 C C_1 L + \alpha^2 C G L + \alpha(C + C_1) + (G + g_m) \} \end{aligned}$$

For an oscillator desire a pole of $Z(s)$ on $j\omega$ axis

$$s = j\omega_0$$

$$\det Y(j\omega_0) = \frac{1}{j\omega_0^2 L^2} \{ -j\omega_0^3 C C_1 L - \omega_0^2 C G L + j\omega_0(C + C_1) + (G + g_m) \}$$

$$\Rightarrow -\omega_0^3 C C_1 L + \omega_0(C + C_1) = 0; \quad \omega_0 \neq 0 \quad \omega_0^2 = \frac{C + C_1}{C C_1 L}$$

$$\omega_0 = \frac{1}{\sqrt{L \cdot \frac{C C_1}{C + C_1}}}$$

$$\Rightarrow -\omega_0^2 G C L + (G + g_m) = 0$$


$$g_m = -G + G(C L \omega_0^2) = G \left[-1 + C L \times \frac{C + C_1}{C C_1 L} \right] = G \left[\frac{-G + C + C_1}{C_1} \right]$$

$$\Rightarrow g_m = \frac{G C}{C_1} > 0 \text{ if pos. element values}$$

$$\det \gamma(s) = \frac{k_2}{s} (s^2 + \omega_0^2)(s + \sigma_0) =$$

$$= \frac{C C_1 L}{s L} \left\{ s^3 + s^2 \frac{C G L}{C C_1 L} + s \frac{(C+C_1)}{C C_1 L} + \frac{(G+g_m)}{C C_1 L} \right\}$$
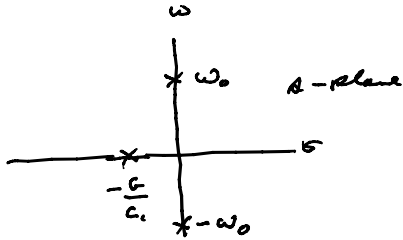
$$\text{show } \omega_0^2 \sigma_0 = \frac{G+g_m}{C C_1 L} \Rightarrow \sigma_0 = \frac{G+g_m}{C C_1 L} \cdot \frac{1}{\omega_0^2} > 0$$



$$\begin{aligned} &= \frac{G+g_m}{C C_1 L} \cdot \frac{1 \cdot C C_1}{C+C_1} \\ &= \frac{G+g_m}{C+C_1} = \frac{G+G \frac{C}{C_1}}{\left(\frac{C}{C_1} + 1\right) C_1} \\ &= \frac{G}{C_1} \cdot \frac{(1 + \frac{C}{C_1})}{(1 + \frac{C}{C_1})} = \frac{G}{C_1} \end{aligned}$$

$$\text{Deter } \frac{v_2(s)}{v_1(s)} \Big|_{i_2=0}$$

$$\text{2nd row of } \gamma \quad i_2 = y_{21} v_1 + y_{22} v_2$$

$$0 \Rightarrow \frac{v_2}{v_1} = -\frac{y_{21}}{y_{22}}$$


$$= -\frac{y_{21}}{y_{22}} = \frac{-(g_m - \frac{1}{sL})}{CA + \frac{1}{sL} + G} = \frac{-(g_m L s - 1)}{CLs^2 + GLs + 1} = \frac{-g_m L (s - \frac{1}{g_m L})}{CLs^2 + \frac{G}{C} s + \frac{1}{LC}}$$

denominator polynomial

$$s^2 + \frac{G}{C} s + \frac{1}{LC} = s^2 + \frac{\omega_n}{Q} s + \omega_n^2 \Rightarrow \frac{\omega_n}{Q} = \frac{G}{C} \Rightarrow Q = \frac{\omega_n C}{G}$$

$\frac{v_2}{v_1}$ has a zero in RH s-plane @ $s = \frac{1}{g_m L}$

Desire to bias otherwise it won't work

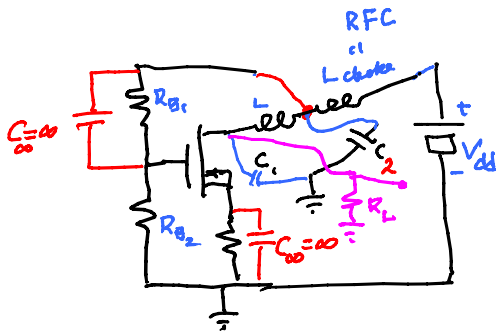

choose R_{G1} & R_{D2} very large

if properly bias can put the NMOS in saturation

$$i_D = \frac{k_p}{2} \frac{W}{L} (v_{GS} - v_{Tn})^2 (1 + \lambda_n v_{DS})$$

$$g_m = \frac{2i_D}{2v_{GS}} \Big|_Q = \frac{2i_D}{v_{GS} - v_{Tn}} \Big|_Q = \frac{2I_D}{v_{GS} - v_{Tn}}$$