

Solutions 303 Midterm

#1. $I_C = \beta I_B$ & $V_{CE} = V_{CC} - (R_L + \frac{R_E}{\alpha}) I_C = V_{CC} - (R_L + \frac{1+\beta}{\beta} R_E) \beta I_B$ so find I_B

$$I_{R_2} = I_B + I_{R_b}$$

$$V_{R_b} = V_{BE} + R_E \cdot \frac{I_C}{\alpha} = V_{BE} + R_E \frac{\beta}{\alpha} I_B = V_{BE} + R_E (1+\beta) I_B$$

$$\Rightarrow I_{R_b} = \frac{1}{R_b} \{ V_{BE} + R_E (1+\beta) I_B \} \Rightarrow I_{R_2} = \left\{ 1 + \frac{R_E (1+\beta)}{R_b} \right\} I_B + \frac{V_{BE}}{R_b}$$

$$V_{CC} = R_a I_{R_2} + R_b I_{R_b} = R_a \left\{ 1 + \frac{R_E (1+\beta)}{R_b} \right\} I_B + \frac{R_a}{R_b} V_{BE} + \{ V_{BE} + R_E (1+\beta) I_B \}$$

$$= \left[R_a \left\{ 1 + \frac{R_E (1+\beta)}{R_b} \right\} + R_E (1+\beta) \right] I_B + (1 + R_a/R_b) V_{BE} = \left[R_a + \left\{ 1 + \frac{R_a}{R_b} \right\} R_E (1+\beta) \right] I_B + \left\{ 1 + \frac{R_a}{R_b} \right\} V_{BE}$$

$$\Rightarrow I_B = \frac{V_{CC} - \left\{ 1 + \frac{R_a}{R_b} \right\} V_{BE}}{R_a + \left\{ 1 + \frac{R_a}{R_b} \right\} R_E (1+\beta)} = \frac{9 - 2 \times 0.7}{10^6 + 2 \times 10^3 (1+\beta)} = \frac{7.6}{10^6 + 2 \times 10^3 (\beta+1)}$$

$$I_B \Big|_{\beta=200} = 5.42 \times 10^{-6} \text{ A} = 5.42 \text{ nA}$$

$$\Rightarrow I_C \Big|_{\beta=200} = 1.084 \times 10^{-3} \text{ A} = 1.08 \text{ mA}$$

a)

$$V_{CE} = 9 - 10^3 \left(1 + \frac{201}{200} \right) \times 1.084 \times 10^{-3} = 9 - 2.17 = 6.83 \text{ V}$$

$$b) I_B = \frac{7.6}{10^6 + 10^3 \times 22} = \frac{7.6 \times 10^{-6}}{1.022} = 7.44 \text{ } \mu\text{A}$$

$$I_C = 10 \times 7.44 \times 10^{-6} = 0.0744 \text{ mA}$$

$$V_{CE} = 9 - 10^3 \left(1 + \frac{11}{10} \right) \times 10 \times 7.44 \times 10^{-6} = 9 - 156 \times 10^{-3} = 9 - 0.156 = 8.844 \text{ V}$$

$$c) g_m = \frac{I_C}{V_T}, V_T = 0.026 \Rightarrow g_{m_s} = \frac{1.09 \times 10^{-3}}{26 \times 10^{-3}} = 0.0419$$

$$g_{m_f} = \frac{74.4 \times 10^{-6}}{26 \times 10^{-3}} = 2.863 \times 10^{-3} = 0.00286$$

$$\text{or } A_v = -g_m R_L \Rightarrow A_{v_s} = -41.9$$

$$\Rightarrow A_{v_f} = -2.86$$

#2. a) By symmetry the drains sit at ground potential when no external signals are applied. Then all NMOS currents are equal & PMOS their negatives as all transistors are in saturation (#'s 1 are by connection & #'s 2 by having all voltages of #'s 1).

Thus

$$I_{D_{m_1}} = I_{D_{m_2}} = -I_{D_{p_1}} = -I_{D_{p_2}} = I_D$$

$$= \frac{K_P W}{2} \frac{1}{L} (V_{GS} - V_{TO})^2 (1 + \lambda V_{GS})$$


$$= \frac{20.54 \times 10^{-6}}{2} \cdot \frac{144 \mu}{8 \mu} (5 - 1.3)^2 (1 + 15 \times 10^{-3} \times 5)$$

a) $= 184.86 \times 10^{-6} (13.69) (1.075) = 2.721 \times 10^{-6} = 2.72 \text{ mA}$

b) The bias power is that supplied by the batteries for the currents of part a), Thus

$$Power_{bias} = 4 \times I_D \times V_{GS} = 54.4 \times 10^{-3} \text{ Watts} = 54.4 \text{ mW}$$

c)

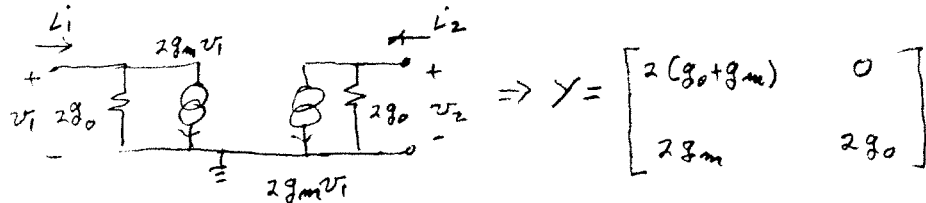

$$g_m = \frac{2 I_D}{(V_{GS} - V_{TO})} = \frac{2 \cdot 2.72 \times 10^{-3}}{(5 - 1.3)} = \frac{5.44}{3.7} \text{ mS} = 1.47 \text{ mS}$$

$$g_o = \frac{\lambda I_D}{1 + \lambda V_{GS}} = \frac{15 \times 10^{-3} \times 2.72 \times 10^{-3}}{1.075} = 37.95 \times 10^{-6} \text{ S}$$

d) $A_{v}(s) = \frac{-y_{21}}{y_{22} \pm y_L} = \frac{-2g_m}{2g_o + AC_L} = \frac{-2.94 \times 10^{-3}}{75.9 \times 10^{-6} + 20 \times 10^{-9} s} = -\frac{2.94 \times 10^{-3}}{20 \times 10^{-9} s + \frac{25.9 \times 10^{-6}}{20 \times 10^{-9}}}$

$$= -147 \times 10^3 \times \frac{1}{s + 3.80 \times 10^3}$$

pole @ $s_p = -3.80 \times 10^3$

zero @ $s_z = \text{infinity}$