

1. For the following two complementary BJT grounded emitter amplifier circuits:



a) Make a table with the following data from the Spice models (except find f_T from the data sheets)

| | Beta = Bf | Early V=Vaf | f_T |
|--------------|-----------|-------------|-------|
| 2N3904 = npn | | | |
| 2N3906 = pnp | | | |

b) Run the Spice curves and choose a Q point which has $|I_C| = 4\text{mA}$ and $V_{CE}=4\text{V}$. Give the resulting I_B from the curves and compare the beta with that of part a). Using I_B from the Spice curves give hand calculations to fill in the following table; use $|V_{BE}|=0.7$. Assume that a voltage gain, $A_V = -100$, is desired (when the Early effect is ignored). Choose $R_{b2}=R_{b3}=10\text{k}\Omega$. Again make a table with the following Q point values.

| amplifier | R_{Cn} | R_{Cp} | R_{En} | R_{Ep} | I_B | R_{b1} | R_{b4} | g_m | g_{π} | g_o |
|-----------|----------|----------|----------|----------|-------|----------|----------|-------|-----------|-------|
| npn | | | | | | | | | | |
| pnp | | | | | | | | | | |

c) In Spice do a frequency response (of $|v_o/v_{in}(j\omega)|$) and compare (for both amplifiers) the low-frequency gain with that calculated. Finally run a frequency response to frequencies above f_T of the transistors (starting at 100Hz) and note the

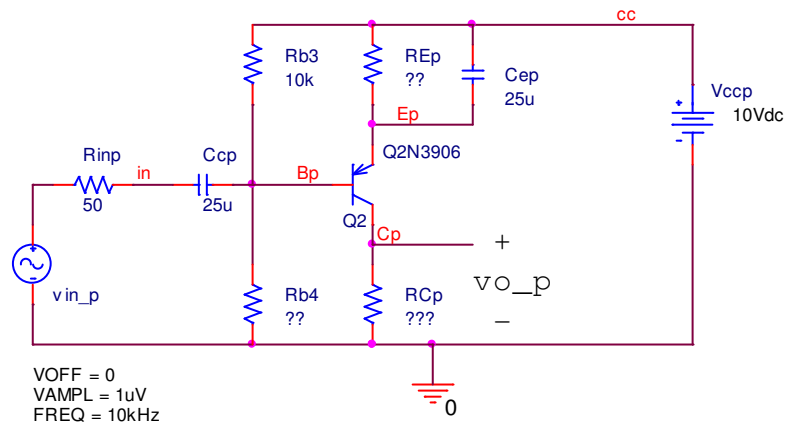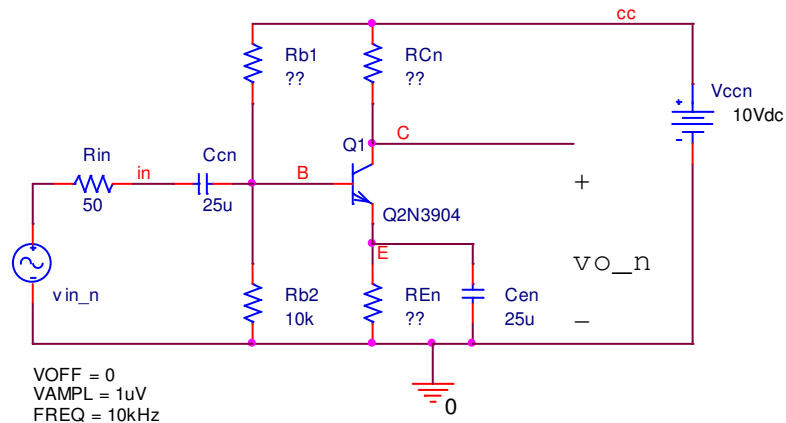

behavior.

Homework 3, S2011, continued

- Using the following circuit with 4007 transistors design a current source and a sink to create output currents of 2 milliAmps. You can use F components to measure the output currents.

