

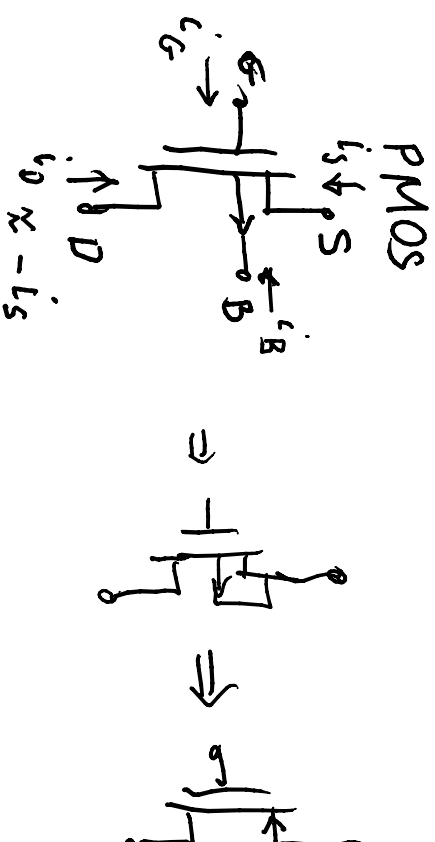
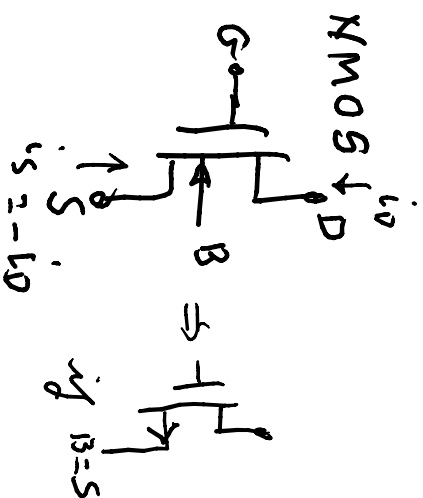
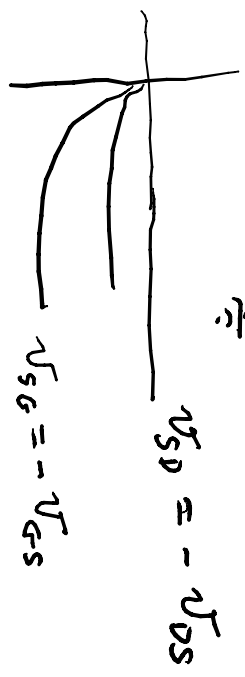
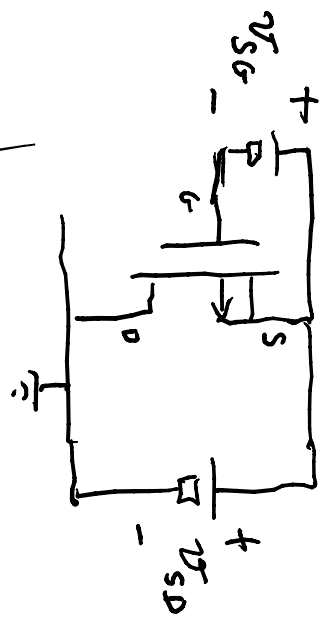
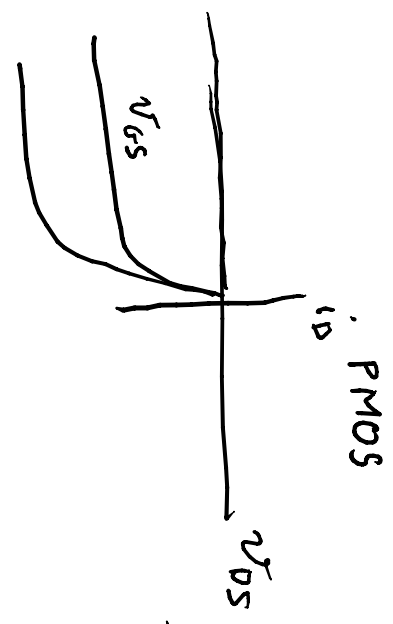


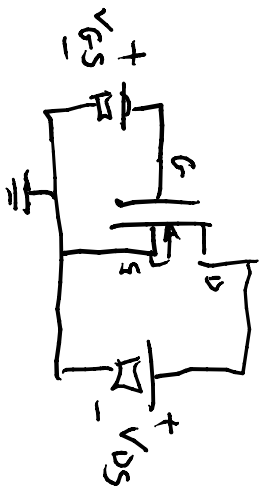1. Meet review & after, meet in CSI 1115
2. Homework new due date next M
3. on M bring a copy of preliminary choice of paper



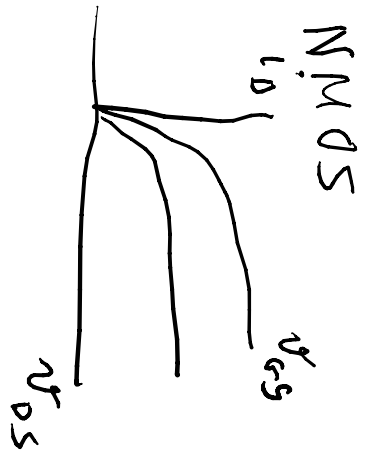

⇒ complementary
CMOS
of NMOS & PMOS

in solution


$$I_{Dn} = \frac{K_n}{2} \cdot \frac{W}{L} (V_{GSn} - V_{T0n})^2 (1 + \lambda_n V_{DSn}) \quad I_{Dp} = -\frac{K_p}{2} \cdot \frac{W}{L} (-V_{GSp} - V_{T0p})^2 (1 - \lambda_p V_{DSp})$$

$V_{T0} =$ threshold voltage when $B = S$


> 0 for NMOS enhancement mode

< 0 for PMOS " " mode

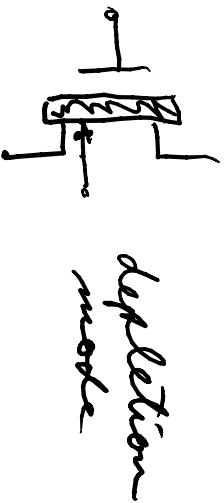for depletion mode get opposite signs to these



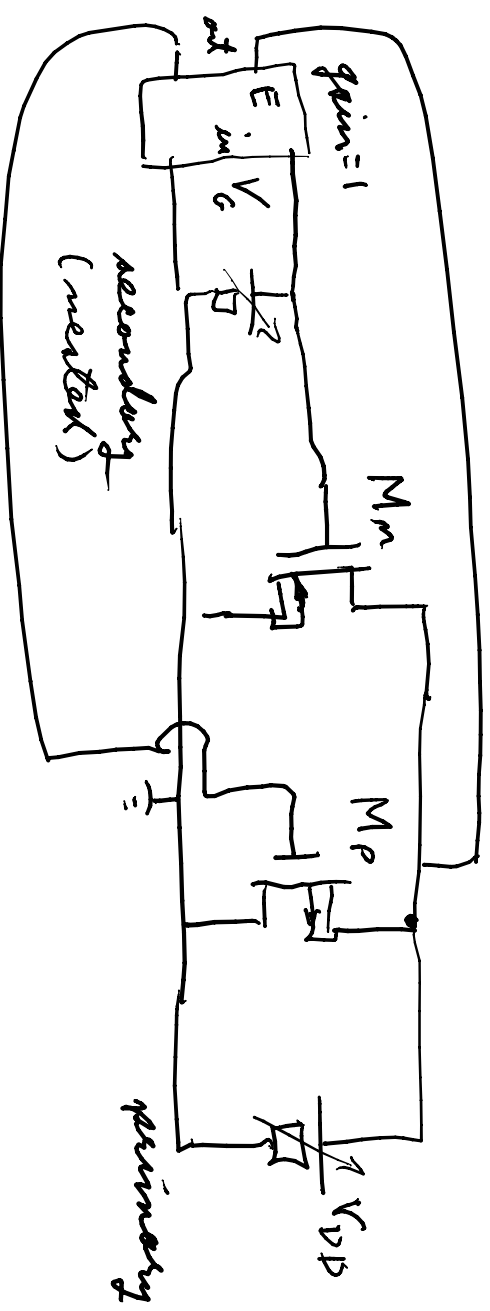OT or get both NB PMOS together with 2 sources




Voltage controlled voltage source } E_{in} in series
 VCVS } analog library

(E_{-} & G_{-} nodes components are in ABM library)


 diode small signal behavior, p. 184 shows idea

$$i_D = I_D + i_d$$

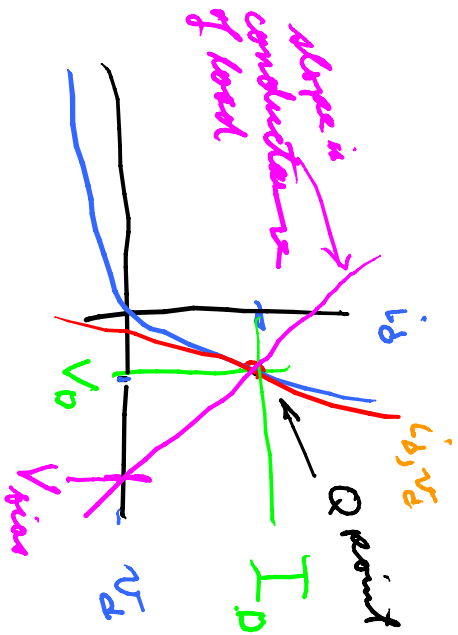


$$i_D = I_D + i_d$$

$$v_D = V_D + v_d$$

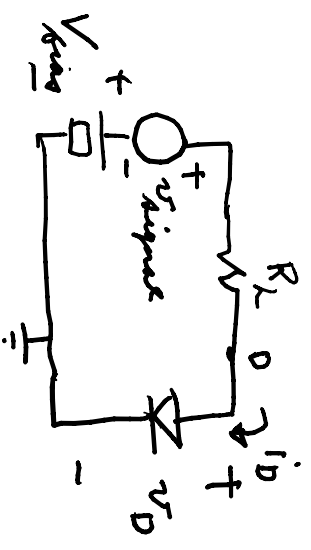

at $v_{signal} = 0$ only the bias current

$$\frac{V_{Bias} - v_D}{R_L} = i_{RL}$$

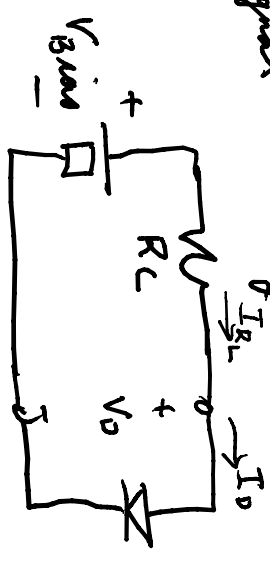


$$I_D = I_S (e^{v_D/V_T} - 1) = G_L \cdot V_{BIAS} - G_L \cdot v_D$$

to get Q point

need to solve for $v_D = V_D$

at Q point operation

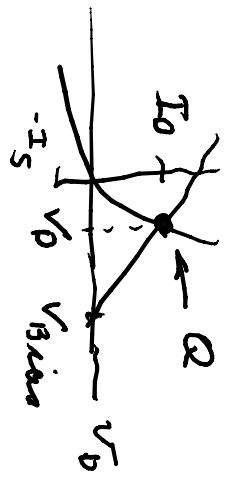

for small signals, $|v_{signal}|$ small


$$i_D = I_D + \frac{\partial i_D}{\partial v_D} (V_D - v_D) + \frac{1}{2!} \frac{\partial^2 i_D}{\partial v_D^2} (V_D - v_D)^2 + \dots$$

$$i_D - I_D = i_D'$$

$$= \frac{\partial i_D}{\partial v_D} \cdot v_D = g_D \cdot v_D$$

↑ diode conductance

drop there if $|v_{signal}|$ small

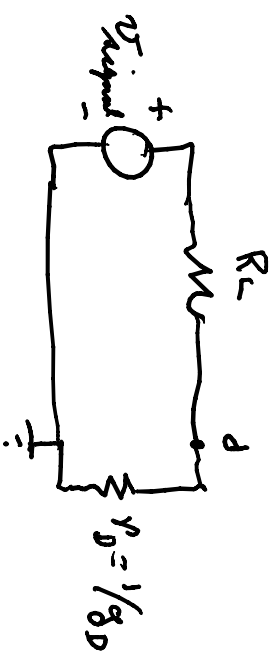


This is a (linear) small signal equivalent circuit

$$g_D = \frac{\partial}{\partial v_D} (I_S [e^{v_D/V_T} - 1]) = \frac{I_S}{V_T} \cdot e^{v_D/V_T}$$

$$v_D = V_D$$

Simplest circuit

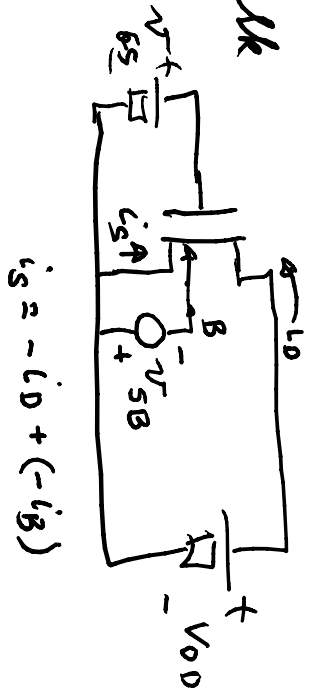

Rank to diode

