

02/07/11





EE 303

BJT's  $\Rightarrow$  need next in 307 cat  
 TA in ANW 1371 on M 10-12  
 dem in the 417 cat 2-5 & after to help with Spice


G\_value f\_G in the ABM library

Spice command for voltage V (node.name)


for 307 case 2N3904 = MPN 2N3906 = PARP

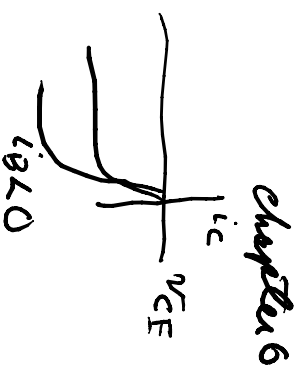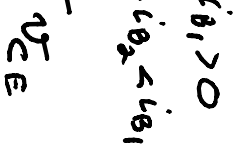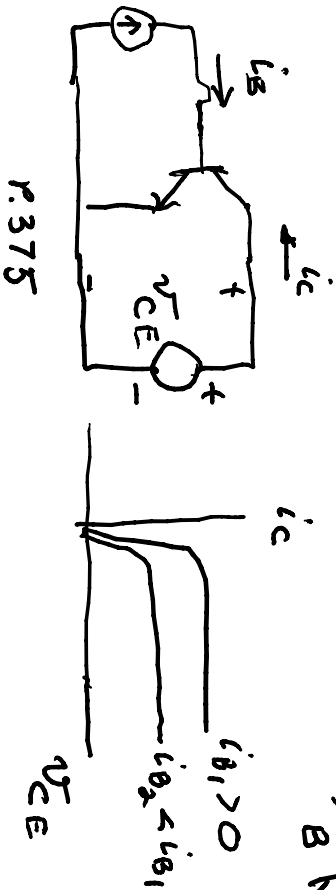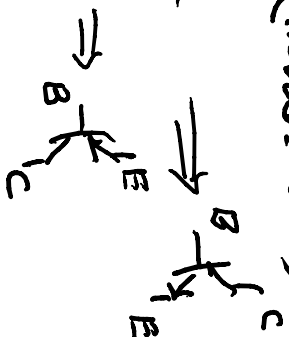


Chapter 6

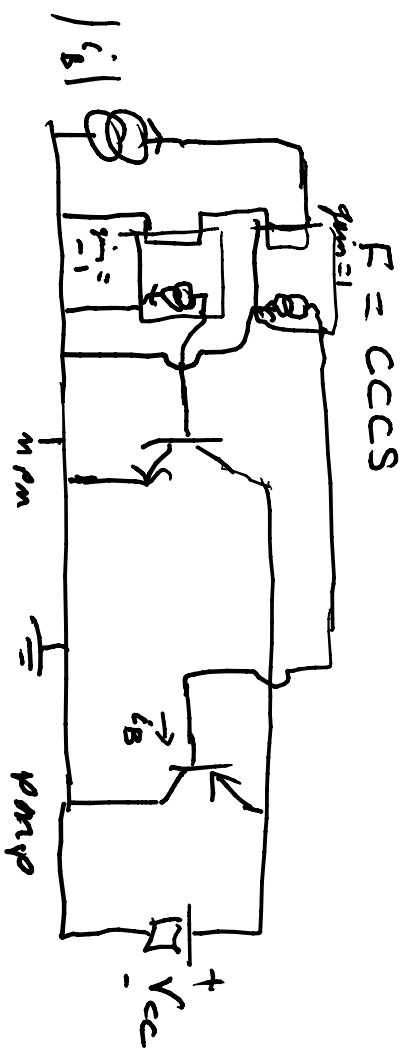


for Spice to give  
transfer curve

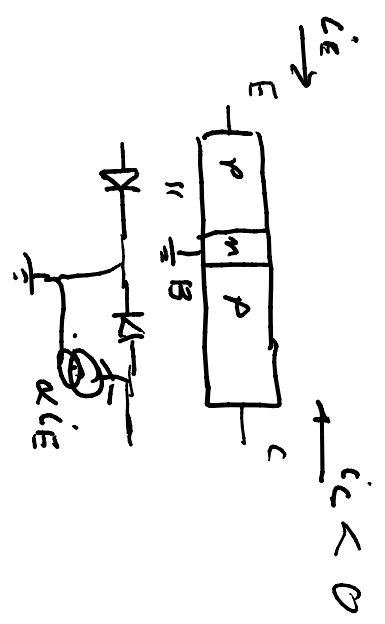

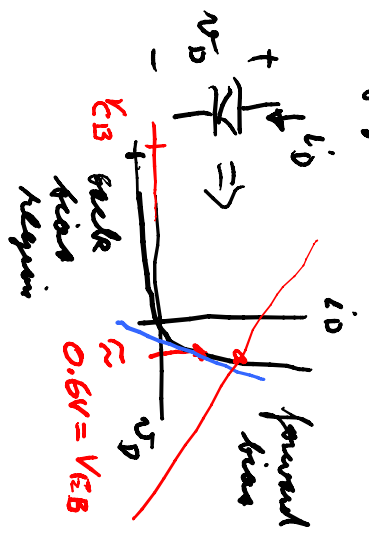$\alpha \approx 1 =$  current gain  
of grounded base




see P. 364  
for bias

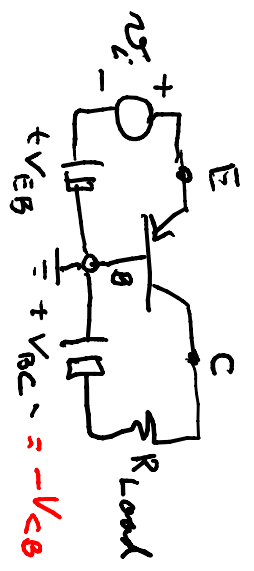

For small signal (N.T. model)

current gain  $\approx -1$

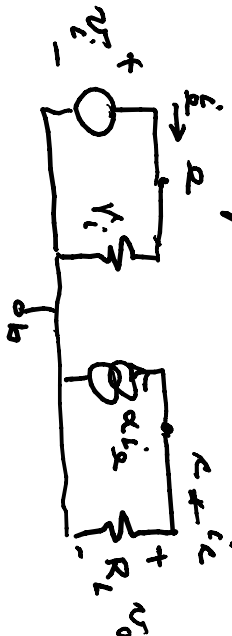

$$i_e = v_i / R_i$$

$$v_o = -R_L i_e = -R_L (-\alpha i_e) = + \frac{R_L}{R_i} \alpha \cdot v_i$$


$$\frac{v_o}{v_i} = \alpha \frac{R_L}{R_i}$$

$$\text{if } R_L = 5 \text{ k}\Omega$$

$$R_i = 50 \Omega$$

$$\alpha = 0.998$$
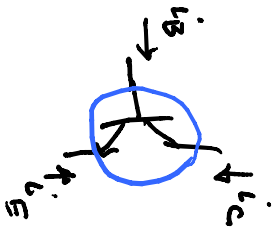
$$\frac{v_o}{v_i} = \text{voltage gain} \approx 100$$



$$\text{KCL: } 0 = i_c + i_b + i_e;$$

$$= i_c + i_b - \frac{1}{\alpha} i_c \Rightarrow -i_b = \frac{(\alpha - 1)}{\alpha} i_c$$

$$i_c = -\alpha i_e \Rightarrow i_e = -\frac{1}{\alpha} i_c$$


$$i_c = \frac{\alpha}{1 - \alpha} i_b = \beta i_b,$$

$$\beta = h_{FE} = \beta_{\text{forward of the transistor}}$$

gives a current gain  $\approx 10^2 - 10^3$


large

∴ use the grounded emitter transistor for amplifying  
 output  $\left| \frac{v_o}{v_i} \right| \sim \beta \frac{R_L}{r_i'} , \left| \frac{v_o}{v_i} \right| \approx \beta$  both large

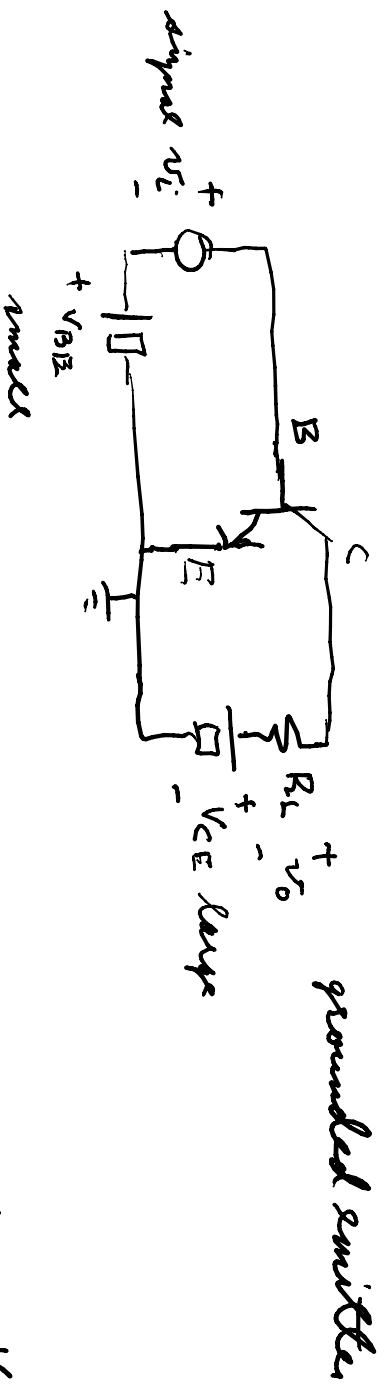

To eliminate  $V_{BE}$  battery we divide down  $V_{CC} \Rightarrow V_{CC}$

p.390

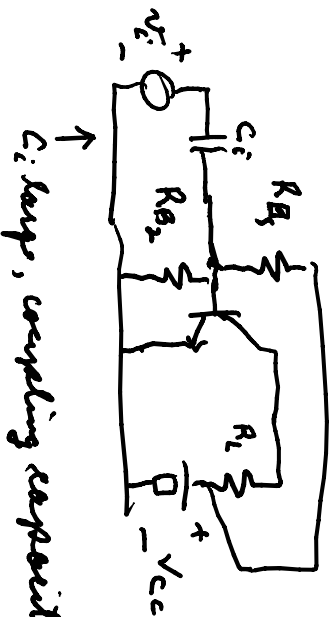

$C_i$  large, coupling capacitor  $\beta = \frac{i}{\Delta C} , C$  large  $\beta \rightarrow 0$  for signals  $> 500$  or more

