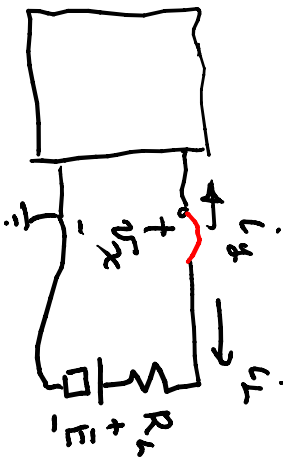


Biasing: P. 390

↑ equivalent circuit, P. 410


Load line




KCL: $0 = -i_y - i_L$

$i_L = -i_y$

when correct

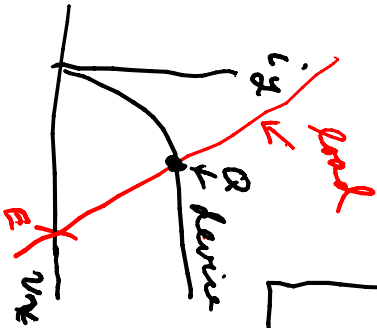


2-port's appendix C

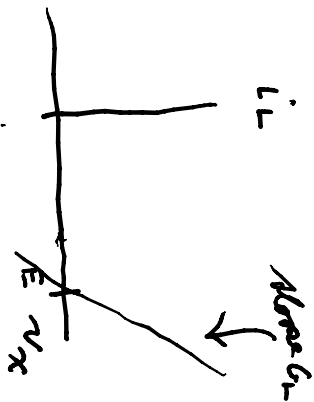


KVL: $0 = R_L i_L + E - v_L$

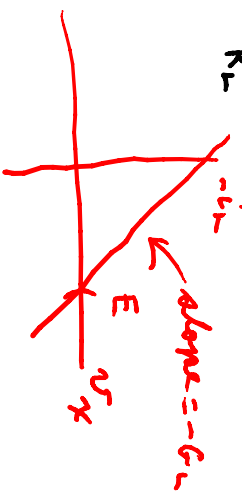$i_L = \frac{1}{R_L} (v_L - E) = G_L v_L - G_L E$





Biasing an NPN P. 390


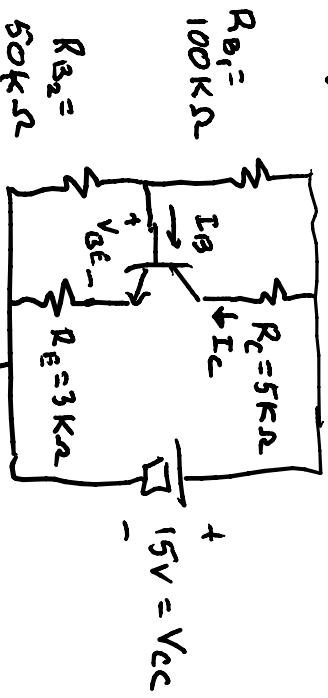


$$\beta = \frac{I_C}{I_B} = 100$$


i_C

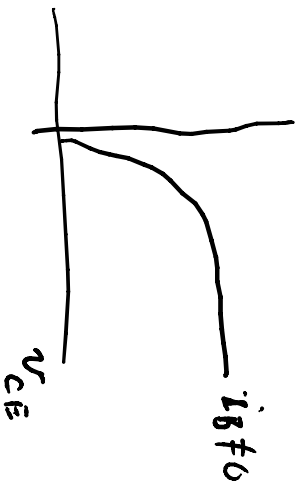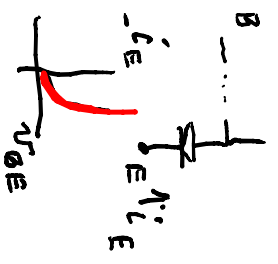

for Base

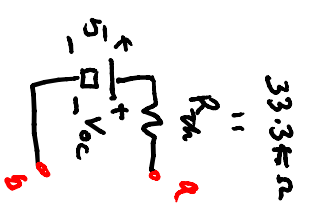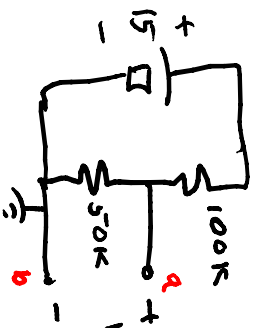
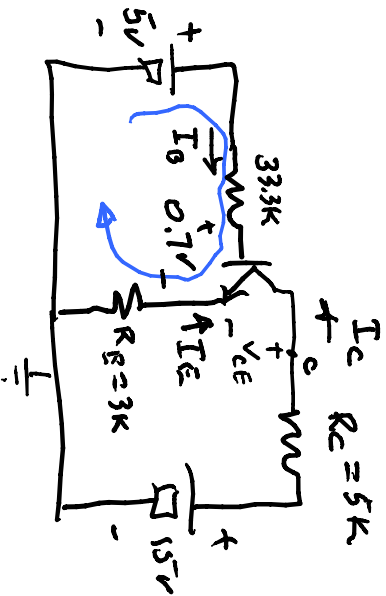
$$R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{5}{15/100k} = 33.3k\Omega$$



$$I_C = -\alpha I_E$$

$$= \beta I_B$$

$$I_E = -\frac{\beta}{\alpha} I_B$$

$$\beta = \frac{\alpha}{1-\alpha}$$

$$\Rightarrow (1-\alpha)\beta = \alpha$$

$$\beta = \alpha + \beta\alpha \Rightarrow \alpha = \frac{\beta}{1+\beta}$$

"

KVL: $0 = -5 + 33.3 \times 10^3 I_B + 0.7 + R_E (-I_E)$

$$4.3 = (33.3 \times 10^3 + \frac{\beta}{\alpha} 3 \times 10^3) I_B, \quad \frac{\beta}{\alpha} = \frac{\beta}{\beta} = (1+\beta)$$

$$4.3 = (33.3 \times 10^3 + 3 \times 101 \times 10^3) I_B$$

$$I_B = \frac{10^{-3}}{336.3} = 0.013 \text{ mA} = 13 \mu\text{A}$$


$$I_C = \beta I_B = 1.3 \text{ mA}, \quad I_E = \frac{-100}{101} \times 1.3 \text{ mA} = -1.29 \text{ mA}$$

$$V_E = \text{voltage at emitter} = R_E (-I_E) = 3.87 \text{ V}$$


$$V_{R_C} = 1.3 \times 10^{-3} \times 5 \times 10^3 = 6.5 \text{ V}$$

$$V_C = \text{voltage at collector} = V_{CC} - V_{R_C} = 15 - 6.5 = 8.5 \text{ V}$$
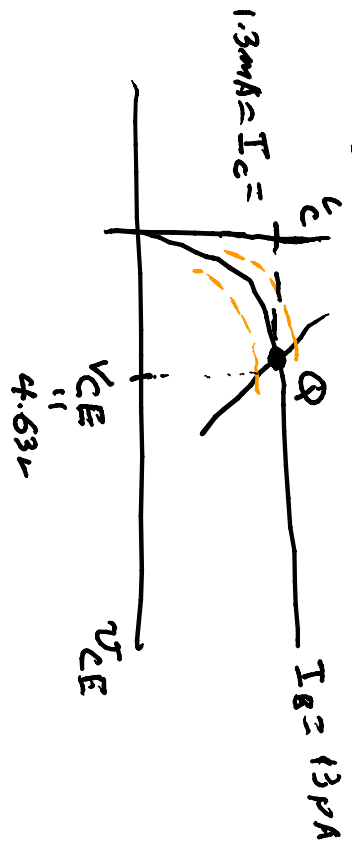
$$V_{CE} = V_C - V_E = 8.5 - 3.87 = 4.63V$$



π Equivalent circuits, p. 410

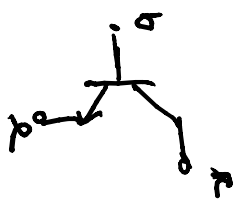

$$i_c = f(v_{CE}, i_B) \quad -i_e = I_{SE} e^{v_{BE}/V_T}, \quad V_T = \frac{kT}{q}$$

$$\approx 0.026V$$

$$= I_C + \frac{\partial f}{\partial v_{CE}} \Big|_Q (v_{CE} - V_{CE}) + \frac{\partial f}{\partial i_B} \Big|_Q (i_B - I_B) + \dots$$

$$A_{ij} = i_c = \frac{\partial i_c}{\partial v_{be}} \Big|_{v_{ce}} + \frac{\partial i_c}{\partial i_b} \Big|_{v_{ce}} = g_o \cdot v_{ce} + \beta i_b$$

$$-i_E = I_{SE} e^{v_{be}/V_T} + \frac{\partial(-i_E)}{\partial v_{be}} \cdot (v_{BE} - V_{BE})$$

$$= -I_E + \frac{I_{SE}}{V_T} \cdot e^{v_{be}/V_T} \cdot v_{be}$$

$$= -I_E - \frac{I_E}{V_T} \cdot v_{be} \quad \text{mit } i_E = -\frac{\beta}{\alpha} i_b$$


$$i_b = I_B + \frac{\partial i_b}{\partial v_{be}} \cdot v_{be} = -\frac{\alpha}{\beta} i_E$$

$$= \frac{\alpha}{\beta} I_E + \frac{I_E}{V_T} \left(\frac{\alpha}{\beta} \right) \cdot v_{be}, \quad I_C = \alpha I_E$$

$$i_b = \frac{1}{\beta} \left(\frac{I_C}{V_T} \right) \cdot v_{be}$$

$$= g_{\pi} \cdot v_{be}$$
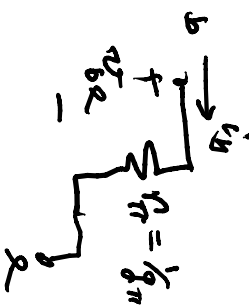
$$r_{\pi} = \frac{1}{g_{\pi}} = \beta \frac{V_T}{I_C}$$




$$i_c = g_o v_{ce} + \beta i_b = g_o v_{ce} + \beta \left[\frac{1}{\beta} \cdot \frac{I_c}{V_T} \right] v_{be}$$

$\underbrace{\hspace{10em}}_{g_m}$


$$\Rightarrow g_m = \frac{I_c}{V_T}, \quad g_{\pi} = \frac{g_m}{\beta}$$

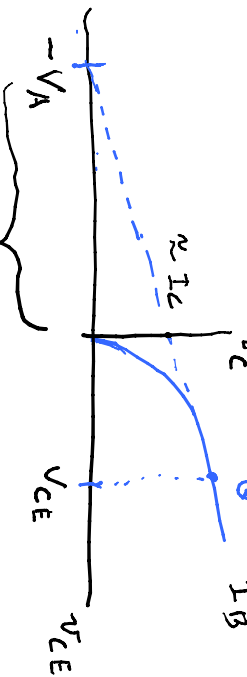Or we need the slope of i_c vs v_{ce} at I_B



$$\text{Slope} \approx \frac{(I_c - 0)}{(0 - (-V_A))} = \frac{I_c}{V_A} = \frac{I_c}{V_T} \cdot \frac{V_T}{V_A} = \frac{V_T}{V_A} \cdot g_m$$

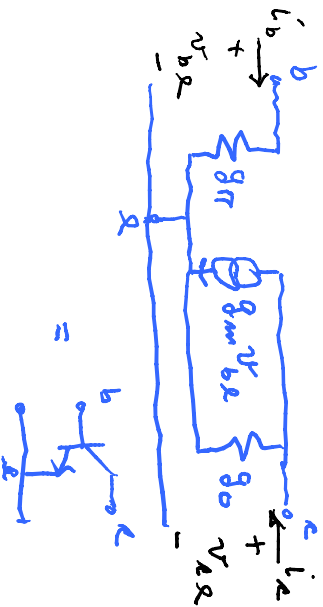2-port equivalent & Y matrix, grounded emitter



$$\begin{bmatrix} i_b \\ i_c \end{bmatrix} = \begin{bmatrix} g_{\pi} \\ g_m \\ g_o \end{bmatrix} \begin{bmatrix} v_{be} \\ v_{ce} \end{bmatrix}$$