

diode connected MOS


$$V_{DS} \approx V_{GS} - V_{T0}$$

$$V_{GS} \approx V_{T0} + V_{DS}$$

for diode connection

if enhancement mode NMOS


activation

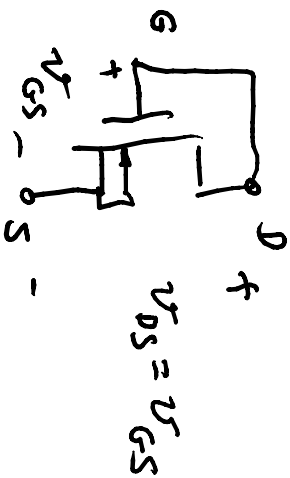


\Rightarrow in saturation
in square law region

$$i_D \approx \frac{K_P \cdot W}{L} (V_{GS} - V_{T0})^2 (1 + \lambda V_{GS})$$

($V_{GS} \approx V_{T0}$)

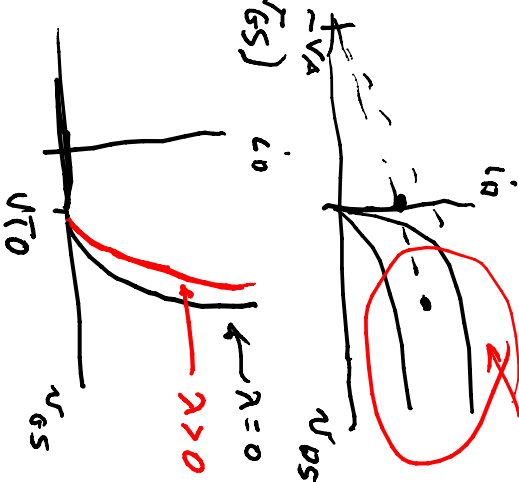

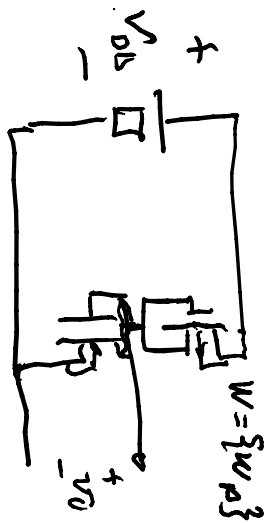

$i_{Dn} = -i_{Dp}$
 have this eq. &
 if W_D is unknown
 then can solve for it

in Spice can adjust W_D as a parameter from the
 special library

for BJT's

$$g_m = \frac{I_C}{V_T}$$


$$r_o = 405 \text{ (6.45)}$$

$g_m = \text{mutual conductance}$

$$g_m = \frac{g_m}{\beta}$$

$$r_o = 407 \text{ (6.51)}$$


$g_m = \text{input conductance}$

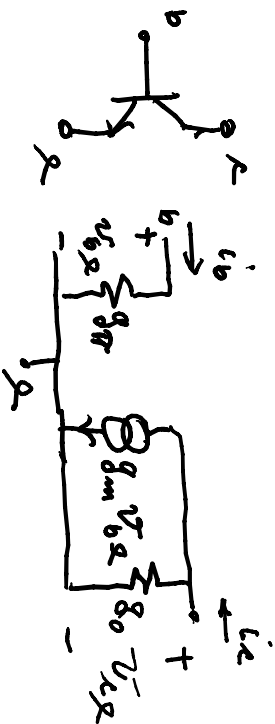


$$\beta = \frac{I_C}{I_B} = \left. \frac{\partial i_c}{\partial i_b} \right|_{Q} = \text{current gain}$$

$$= h_{FE}$$

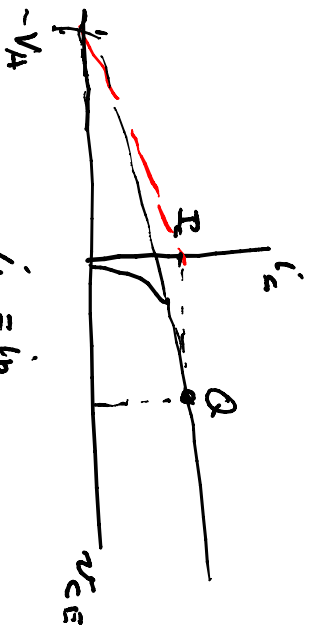$\beta = \text{forward, } R = \text{grounded emitter}$



$$\text{slope} = \frac{\partial i_c}{\partial v_{CE}} \Big|_{I_C=0} = \frac{I_C}{V_A} = g_0$$

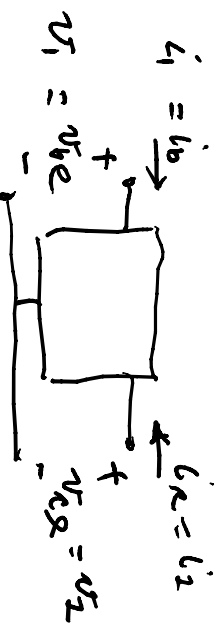

$$\begin{bmatrix} i_1 \\ i_2 \end{bmatrix} = \mathbf{Y} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$i_1 = i_b = g_{11} v_1 \quad v_2 = 0 \text{ (short)} = g_{11} v_1 \quad g_{11} = g_{\pi} \quad g_{12} = 0$$

$$i_2 = i_c = g_{21} v_1 \quad v_2 = 0$$



$$\Rightarrow g_{21} = g_m$$

$$i_2 = i_c = g_{22} v_2 \quad v_1 = v_{be} = 0 \Rightarrow i_{in} g_m = 0 = g_o$$




$$Y = \begin{bmatrix} g_{\pi} & 0 \\ g_m & g_o \end{bmatrix} \Rightarrow \text{small signal description}$$

$$i_c = \begin{bmatrix} i_b \\ i_c \end{bmatrix} = \begin{bmatrix} i_b \\ i_c \end{bmatrix}$$

$$KCL: i_c = -i_b - i_r$$

$\left. \begin{matrix} \text{Kocher} \\ \text{Kinner} \end{matrix} \right\} \Rightarrow r_p \ll r_n$
 forward \Rightarrow looks like a capacitor
 the diode
 r_n

P. 707
at bottom

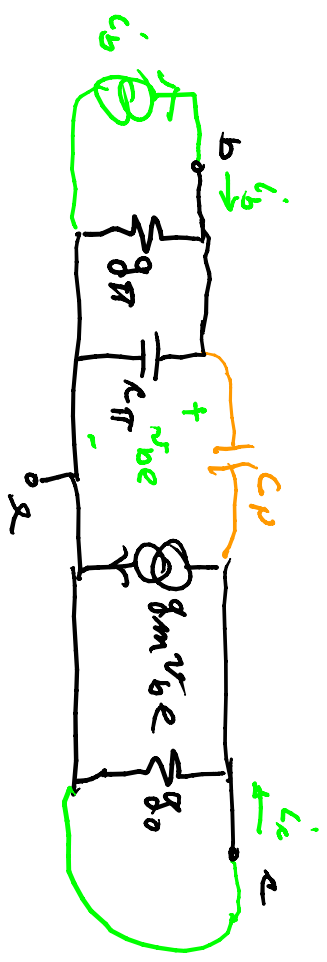

$$\frac{i_c}{i_b} \Big|_{v_{CE}=0} = \text{short the port } r$$

$$i_b = (g_m + A[C_{\pi} + C_{\mu}]) v_{be} \Rightarrow v_{be} = \frac{i_b}{g_m + A[C_{\pi} + C_{\mu}]}$$

$$g_m v_{be} = \frac{g_m}{g_m + A[C_{\pi} + C_{\mu}]} \cdot i_b$$


if ignore $C_{in} C_{\mu} \Rightarrow i_c = g_m v_{be} \Rightarrow \frac{i_c}{i_b} \approx \frac{g_m / g_m}{1 + A[C_{\pi} + C_{\mu}]} \approx \frac{\beta_{oc}}{1 + A C_{\pi} / g_m}$

if $A = j\omega \Rightarrow j\omega$ is very large


$$\left| \frac{i_c}{i_b} \right| \approx \frac{\beta_{oc}}{C_{\pi} \cdot \omega} \Rightarrow \text{if } \omega = 1 \text{ then transition occurs near } \omega = \frac{\beta_{oc}}{C_{\pi}}$$

that frequency is $\omega_T = 2\pi f_T$, transition frequency
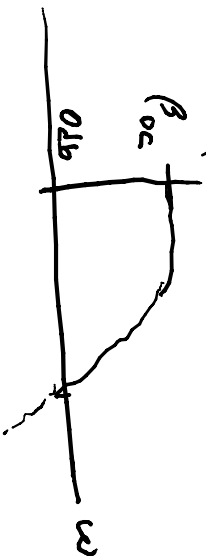
$$1 = \frac{\beta_{oc}}{C_{\pi} \cdot \omega_T} \Rightarrow \omega_T = \frac{g_m \beta_{oc}}{C_{\pi}} = \frac{g_m}{C_{\pi}}$$



for an amplifier

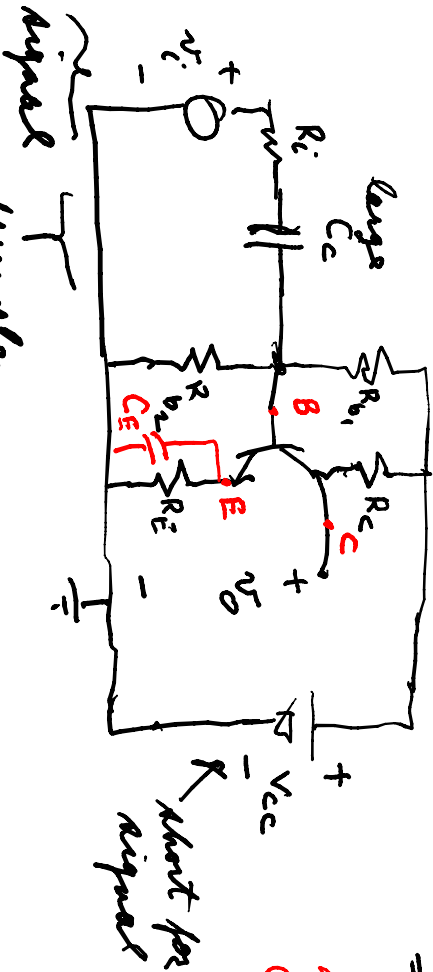


decouples
bias from
input signals

short for
signals

$$Z_c = \frac{1}{A_c} \Rightarrow \frac{1}{j\omega C_c}$$


$\Rightarrow 0$ for C_c large

do also for C_E
(opposite of R_E)

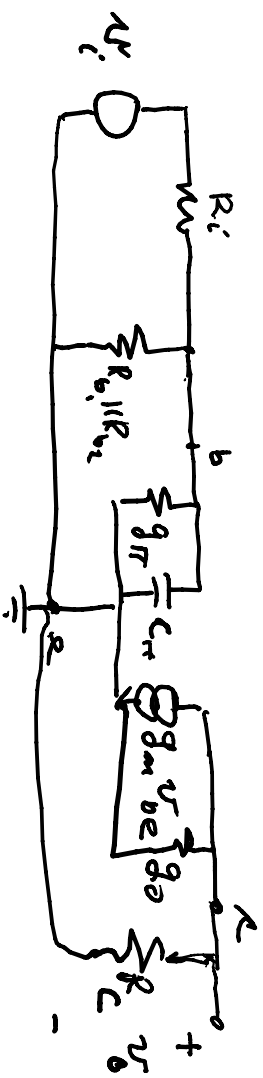

We are interested in v_o vs v_i

1st approximation

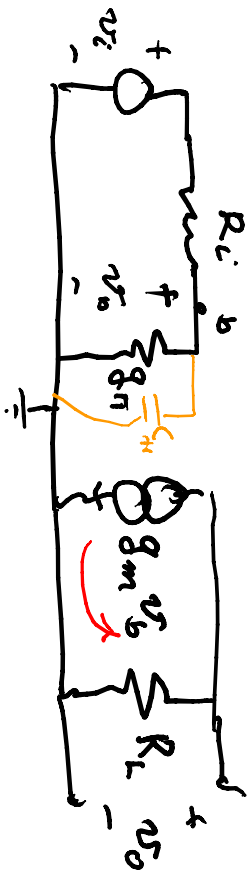

$$\frac{v_o}{v_b} = -g_m R_L \quad \text{Ass. } R_L = \frac{R_C \parallel R_o}{R_C + R_o}$$

So get $\frac{v_o}{v_i}$

use $g_m \Rightarrow g_m + A C_E = y_H$

$$y_H v_b \approx i_b \Rightarrow v_b = \frac{i_b}{g_m + A C_E}$$



$$-v_i + R_i i_b + v_b = 0 \Rightarrow -v_i + R_i g_m v_b + v_b = 0$$

$$v_b = \frac{v_i}{1 + R_i y_H} \Rightarrow \frac{v_o}{v_i} = \frac{-g_m R_L}{1 + R_i (g_m + A C_E)}$$

