

02/16/11
 ££303

P. 705 = MOS equiv. circ.

P. 703 = C¹_A for

P. 528 = current mirror

P. 595 = MOS differential pairs

P. 613 = BST " " "



$\beta \Rightarrow$ BF, BR

beta forward ≈ 100
 beta reverse ≈ 1

$V_A \Rightarrow$ VAF, VAR




Early voltage forward
 " " reverse

v



← forward Active BE


small signal

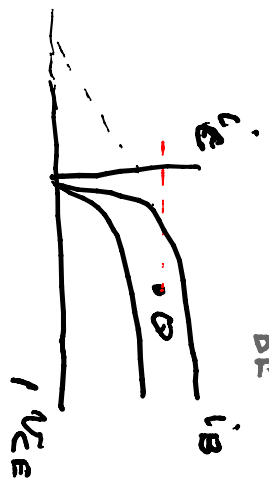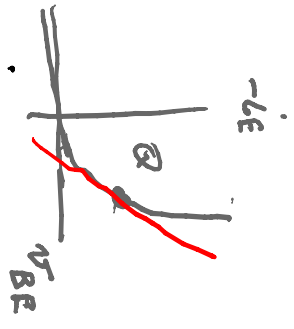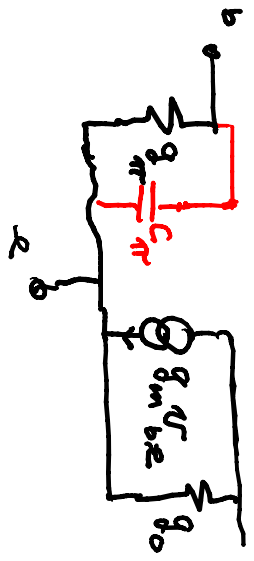

$\beta = \frac{\partial i_C}{\partial i_B}$ | also $i_C = \beta i_B$

$g_m = \frac{I_{CQ}}{V_T}$

for finding of V.370,

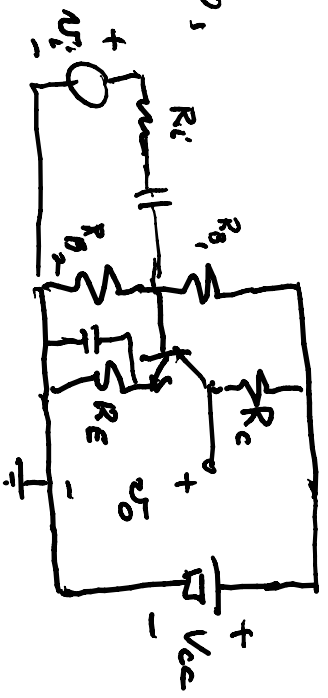


$$I_C = 1.28 \text{ mA} \Rightarrow g_m = \frac{1.28 \times 10^{-3}}{26 \times 10^{-3}} \quad V_T = \frac{kT}{q} \approx 26 \text{ mV} @ 300 \text{ mK}$$


$$= 0.0492 \quad = 49.2 \text{ mS}$$

for $\beta = 100 = h_{FE}$ (BF414) $g_m = \frac{g_m}{\beta} = 49.2 \times 10^{-5} \text{ S}$

$$r_\pi = \frac{1}{g_m} \approx \frac{10^5}{49.2} = \frac{10 \times 10^4}{4.92 \times 10} = 2.03 \times 10^3 \Omega = 2 \text{ k}\Omega$$

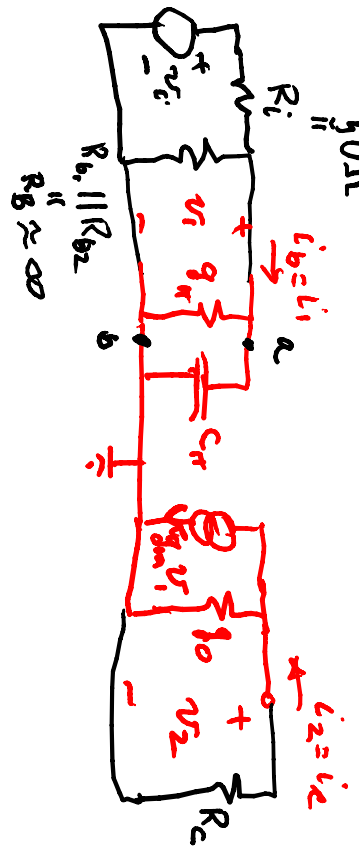If $V_{AF} = 100 = g_o = \frac{I_C}{V_{AF}} = \frac{1.28 \text{ mA}}{100 \text{ V}} = 1.28 \times 10^{-5} \text{ S}$, $r_o = \frac{1}{g_o} = 0.78 \times 10^5 = 78 \text{ k}\Omega$




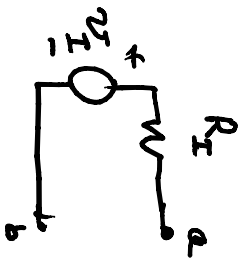

$$R_I = \frac{50 \times 2 \times 10^3}{50 + 2000} = \frac{10^5}{2050} = \frac{100}{2.05} \approx 50 \Omega$$

$$v_I = v_i \cdot \frac{R_I}{R_i + R_I} = v_i \cdot \frac{2 \times 10^3}{2,050} = v_i \cdot \frac{2}{2.05} \approx v_i$$

$R_I =$ parallel combination of R_i, R_0, R_n
 \Rightarrow Thevenin's equivalent
 $v_I = v_i \cdot \left(\frac{R_0 \parallel R_n}{R_i + R_0 \parallel R_n} \right)$
 \approx Thevenin's eq.

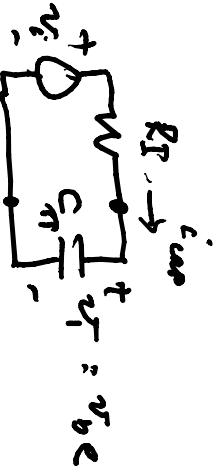

node 2) for $i_{cap} \Rightarrow$ 1)

$$i_{cap} = C_{\pi} \frac{dv_o}{dt} \quad 1)$$

$$v_i - v_o = \frac{v_o}{R_I} = R_I \cdot i_{cap} \quad 2)$$

$$i_{cap} = G_{\pi} (v_i - v_o) = C_{\pi} \frac{dv_o}{dt}$$

$$C_{\pi} \frac{dv_o}{dt} + G_{\pi} v_o = G_{\pi} v_i$$

$$C_T a V(s) + G_I V(s) = G_I V_i(s)$$

$$V(s) = \frac{G_I}{C_T a + G_I} V_i(s) \quad (\text{transfer function}) V_i$$

here $G_I = \frac{1}{50}$, choose $C_T = 10 \text{ pF} = 10 \times 10^{-12} \text{ F}$

$$T_V(s) = \frac{G_I / C_T}{a + G_I / C_T} = \frac{1}{50 \times 10 \times 10^{-12}} = \frac{G_I}{C_T} = \frac{10^3 \times 10^9}{500} = 2 \times 10^9$$

pole at $a = -\frac{G_I}{C_T} = -2 \times 10^9$

zero at $a = \infty$; impulse response = $\mathcal{L}^{-1}(T_V(s))$


$$v(t) |_{v_i = \delta(t)}$$

$$= \frac{G_I}{C_T} e^{-t \cdot G_I / C_T} 1(t)$$

time constant = $\frac{1}{G_I / C_T}$

$$\frac{G_I}{C_T}$$

time constant = $\frac{1}{G_I / C_T}$

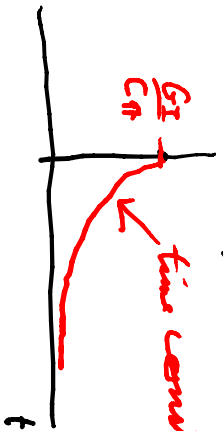

for small signal $v_i(t)$, $v(t) = \int_0^t \frac{G_I}{C_T} e^{-(t-\tau) \cdot G_I / C_T} \cdot v_i(\tau) d\tau$

$$V_1(t) = V_i \cdot 1(t) ; \quad f[V_1] = \frac{V_i}{s} ; \quad f[1(t)] = \int_0^{\infty} e^{-st} f(t) dt$$

$$\frac{dV_1}{dt} + \frac{G_{E1}}{C_{\pi}} V_1 = \frac{G_{E1}}{C_{\pi}} V_i$$

$$sV_1 + \frac{G_{E1}}{C_{\pi}} V_1 = \frac{G_{E1}}{C_{\pi}} V_i \cdot \frac{1}{s} \Rightarrow V_1 = \frac{1}{s} \cdot \frac{G_{E1}/C_{\pi}}{s + \frac{G_{E1}}{C_{\pi}}} V_i$$

$$= \left(\frac{R_{E1}}{s} + \frac{R_{E1}}{s + \frac{G_{E1}}{C_{\pi}}} \right) V_i = \left(\frac{1}{s} + \frac{-1}{s + \frac{G_{E1}}{C_{\pi}}} \right) V_i$$

$$\therefore f[V_1] = V_1(t) = V_i \cdot 1(t) - e^{-t \frac{G_{E1}}{C_{\pi}}} V_i \cdot 1(t)$$

Current mirror

