

Notation $x_Y = \text{total} = \text{bias} + \text{signal}$



$x_Y = \text{bias} = DC$


$x_g = \text{signal}$

$x_Y = x_Y + x_g$

pp. 557-558 table compares MOS & BJT

Biasing of

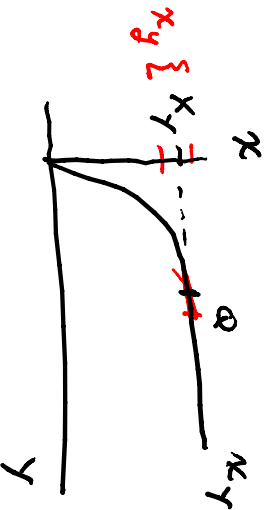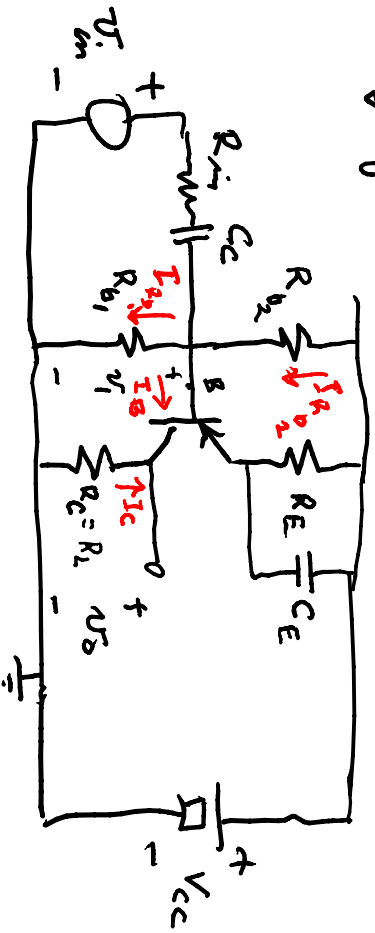

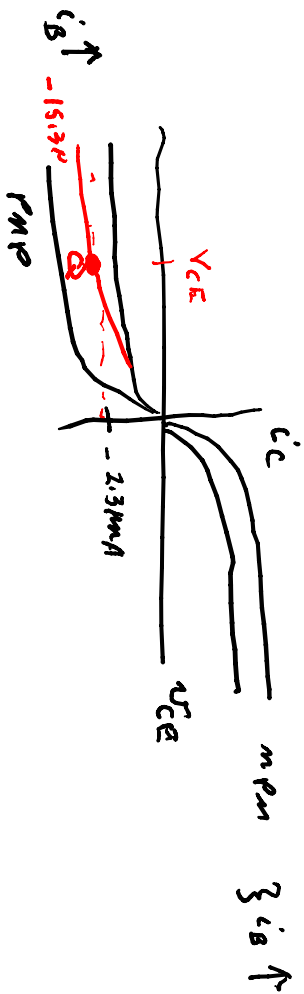

as all slopes are > 0 then get the same equivalent circuit for the MPP & mPP



Example given $A_v = -150$, $R_L = R_C = 1.5 k\Omega$

$$\frac{v_o}{v_i} = -g_m R_L \Rightarrow g_m = \frac{150}{1.5 \times 10^3} = \frac{1.5 \times 10^{-2}}{1.5 \times 10^3} = \frac{1}{10}$$

$$g_m = \frac{I_{CQ}}{V_T} \Rightarrow I_{CQ} \approx g_m V_T \quad \text{at room T}$$

$$= -\frac{1}{10} \times 23 \text{ mV} \times \frac{1}{10} = -2.3 \text{ mA}$$

assume

$\beta = 150$ is given

$$\therefore I_B = \frac{1}{\beta} I_C \Rightarrow I_B = - \frac{2.3 \times 10^{-3}}{1.5 \times 10^2} = -1.53 \times 10^{-5} = -15.3 \text{ nA}$$

DC voltage on $R_C \Rightarrow V_C = R_C (-I_C) = 1.5 \text{ k}\Omega \times 2.3 \text{ mA}$
 $= 3.45 \text{ V}$

$$\begin{array}{r} 2.3 \\ 1.5 \\ \hline 115 \\ 23 \\ \hline 3.45 \end{array}$$

assume from circuit $V_{CE} \approx 5 \text{ V}$

we need $V_{CE} > V_{CE} + V_C = 8.45$

assume get a 12V battery $\Rightarrow V_{CC} = 12 \text{ V}$

now know $V_{R_E} = V_{CE} + V_{CE} + V_{R_E} = 12 - 8.45 = 3.55$

$$= R_E \times I_E ; \quad \alpha I_E = -I_C ; \quad \alpha = \frac{\beta}{1+\beta} = 0.993$$

$$R_E = \frac{V_{R_E}}{I_E} \approx \frac{3.55}{(2.3/0.993) \times 10^{-3}} = 1.533 \text{ k}\Omega$$

$$V_{R_{B_2}} = V_{R_E} + 0.7 = 3.55 + 0.7 = 4.25 \text{ V}$$

$$V_{R_{B_1}} = V_{CC} - V_{R_{B_2}} = 12 - 4.25 = 7.75 \text{ V}$$

$$I_{R_0} = I_{R_{b_2}} - I_g = I_{R_{b_2}} - 15.3 \mu A$$

$$V_{R_{b_1}} = 7.75 = R_{b_1} (I_{R_{b_2}} - 15.3 \mu A)$$

$$V_{R_{b_2}} = 4.25 = R_{b_2} \cdot I_{R_{b_2}}$$

$$b_1) / b_2) \Rightarrow \frac{7.75}{4.25} = \frac{R_{b_1}}{R_{b_2}} \left(1 - \frac{15.3 \mu A}{I_{R_{b_2}}} \right)$$

$$= 1.824$$

$$\text{Here need } I_{R_{b_2}} > 0$$

$$\Rightarrow \frac{R_{b_1}}{R_{b_2}} > 1.824$$

$$\Rightarrow 15.3 \times 10^{-6} = I_{R_{b_2}} \left(\frac{R_{b_1}}{R_{b_2}} - 1.824 \right) \Rightarrow \text{choose } \frac{R_{b_1}}{R_{b_2}} = 3$$

$$= I_{R_{b_2}} (1.176)$$

$$\Rightarrow I_{R_{b_2}} = 13.01 \mu A$$

normally choose these
range, say $M\Omega$ a

$$\text{if choose } R_{b_2} = 1 \times 10^6 \Omega$$

$$R_{b_1} = 3 \times 10^6 \Omega$$

finishes the wiring (Turn to Spice for simulation
as desired).



for small signals we know g_m

$$g_{m\pi} = g_m = \frac{1}{\beta} = \frac{1}{10} \times \frac{1}{150} = \frac{1}{1.5 \times 10^3} = 0.7 \text{ milli S}$$


for g_o need $V_B = \text{Early voltage}$, assume $\approx 100V$


$$\text{Then } g_o \approx \frac{|I_C|}{V_A} = \frac{2.5 \times 10^{-3}}{100} = 2.5 \times 10^{-5} = 25 \times 10^{-6} = 25 \mu\text{S}$$

small signal equivalent

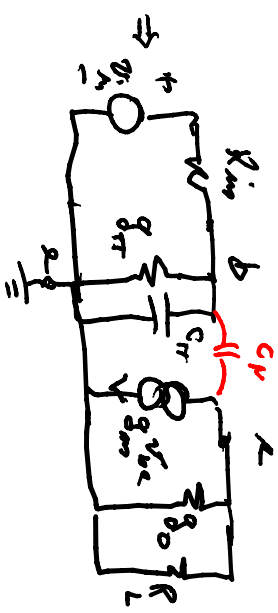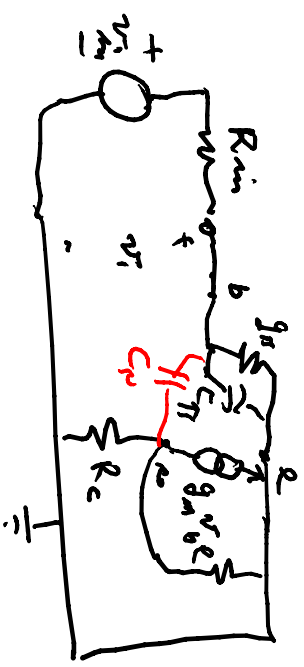

mid band

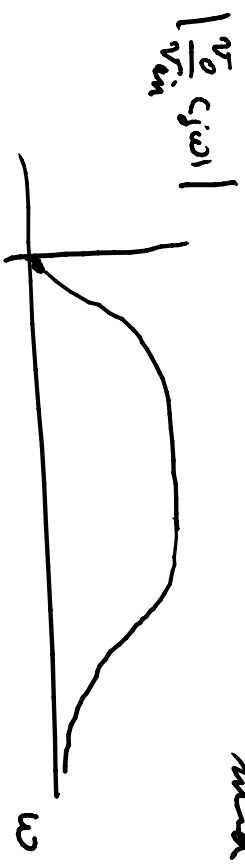

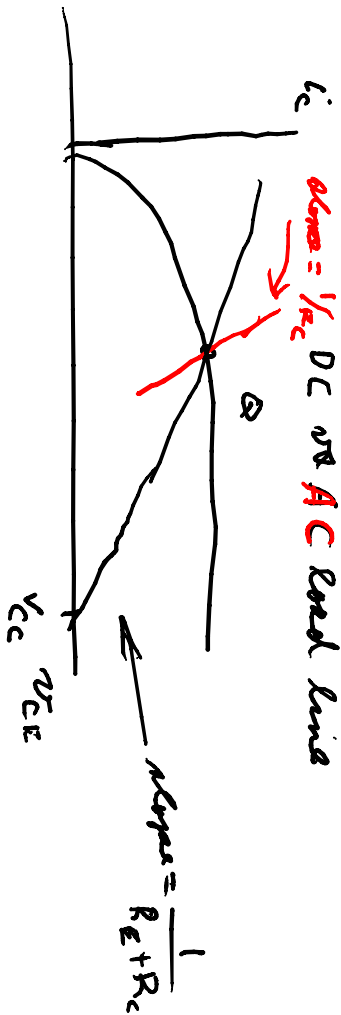

The emitter follower takes signal off of emitter resistor which gives a voltage gain less than 1.

Next topic differential pairs, p. 613

