

02/28/11
EE303 +


Exercise CM, P.538


on homework 4
 I_T value, can choose but
 a good choice is 8mA

1st present, 4min M 03/28, W 03/30, M 04/04
 (17/2011)


2nd present, 10min + 2, M 04/06 - W 05/04

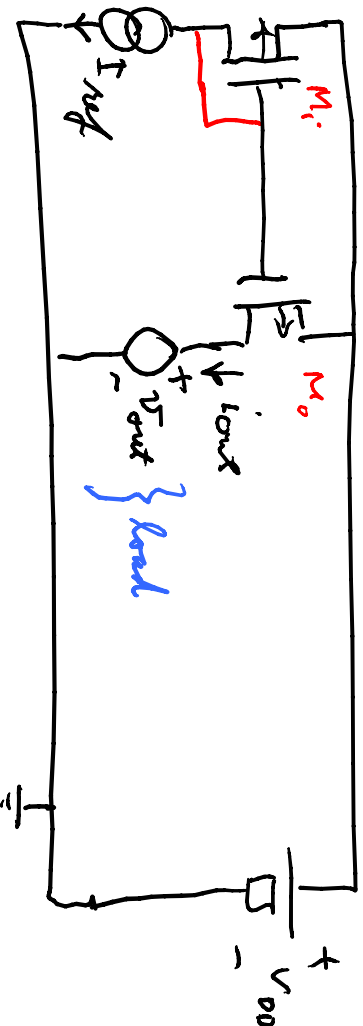For testing of an iut can make sure the transistors are properly biased




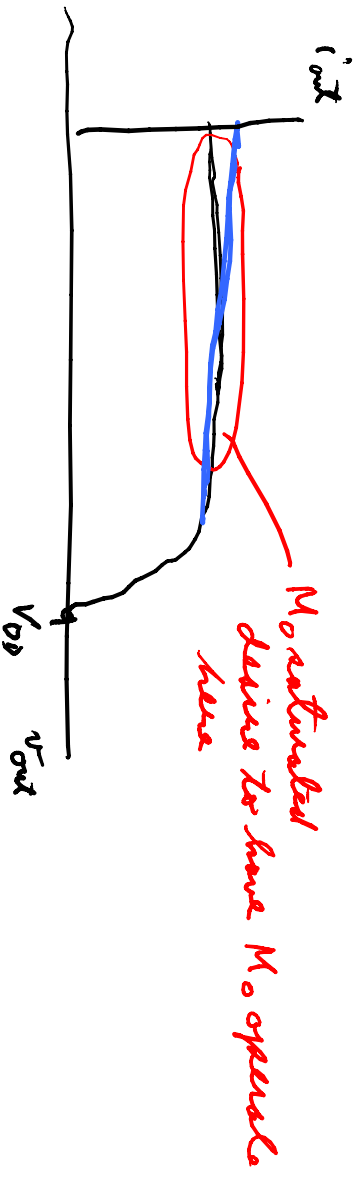


Cascode connection

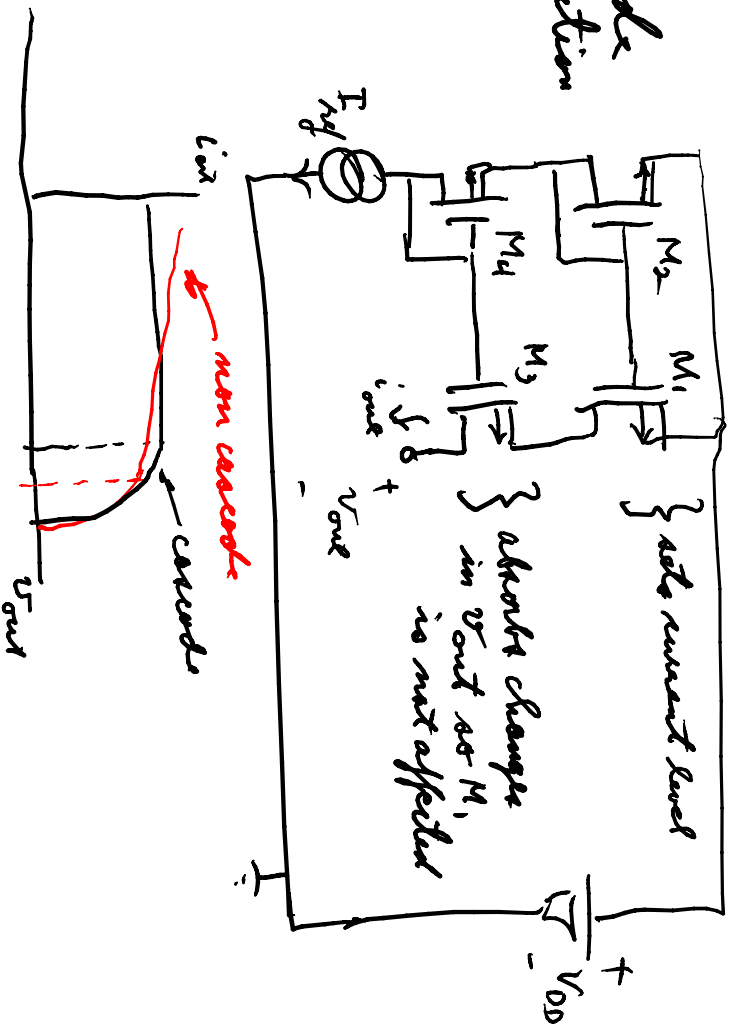

look at

for small signal

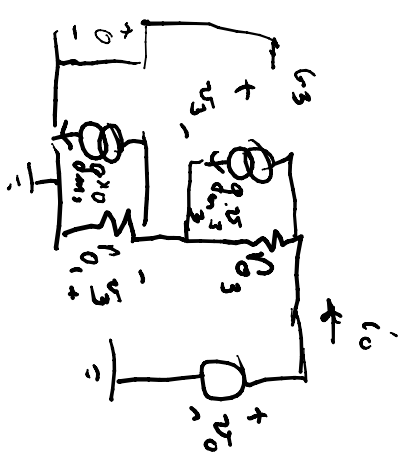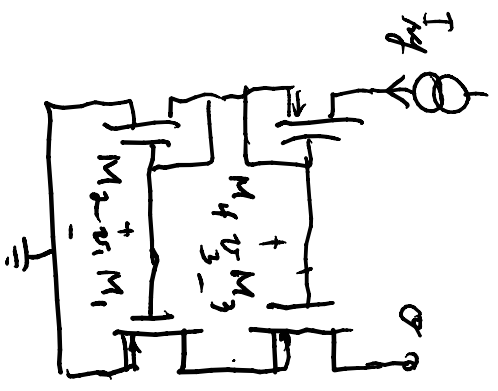


$$-v_3 = v_{o1} \cdot i_o, \quad i_o = i_{o3} + g_{m3} v_3 = i_{o3} + g_{m3} v_3 = i_{o3} - g_{m3} v_{o1} i_o$$

$$i_{o3} = (1 + g_{m3} v_{o1}) i_o, \quad v_3 = v_{o3} i_{o3} + v_{o1} \cdot i_o = [v_{o3} (1 + g_{m3} v_{o1}) + v_{o1}] i_o$$

$$\Rightarrow v_{o1} \Rightarrow v_{o1} + (1 + g_{m3} v_{o1}) v_{o3} \Rightarrow v_{o1}$$

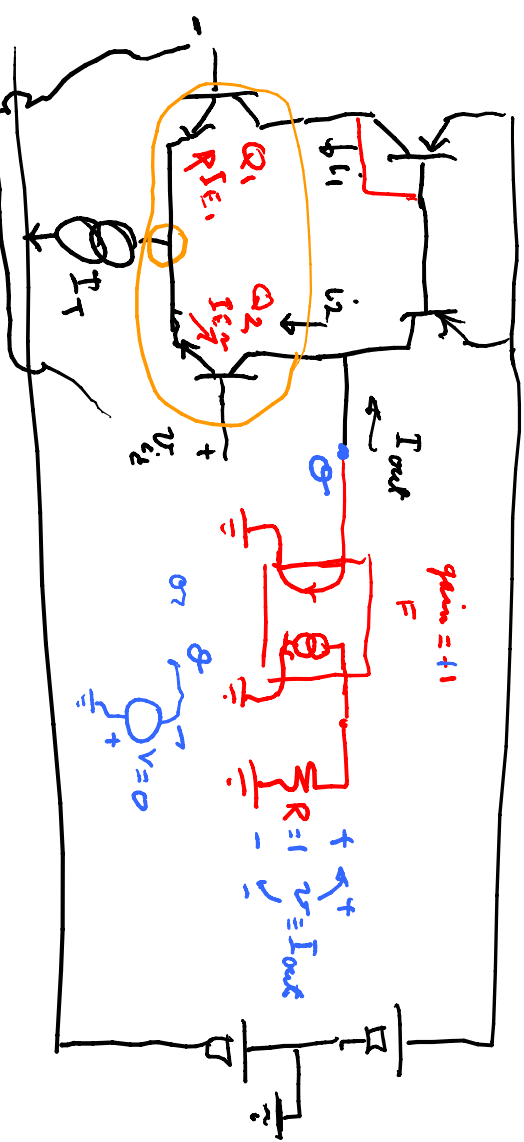$\frac{1}{\text{alpha}}$ \Rightarrow with cascode \Rightarrow without $\underbrace{\hspace{2cm}}$
 (acts as a better current source)




$$I_{out} = I_{c2} - I_{c1} = I_{c2} - I_{c1} = -\alpha I_{E2} + \alpha I_{E1}$$


KCL @ E_1

$$0 = I_{E1} + I_{R2} + I_{Tr}$$
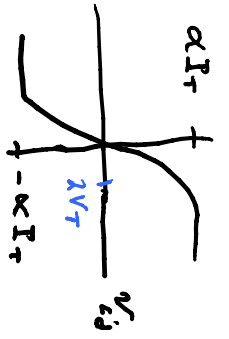
$$\Rightarrow I_{out} = \alpha I_{Tr} \tanh(\alpha / 2V_T)$$



MOS diff pair

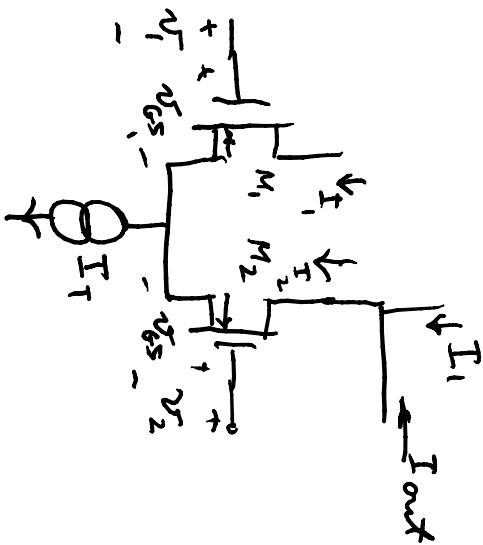

$$v_D = v_{I2} - v_{I1}$$

$$I_T = I_{I1} + I_{I2}$$

$$I_O = I_{out} = I_{I2} - I_{I1} = i_{I2} - i_{I1}$$

$$v_{D2} - v_{D1} = v_{GS2} - v_{GS1}$$

$$i_{I2} = I_O + i_{I1}$$

$$i_{I2} = I_T + i_{I1}$$

operating M_1 & M_2
in saturation

$$i_D = \frac{k_P}{2} \cdot \frac{W}{L} (v_{GS} - V_{th})^2 \Rightarrow v_{GS2} = V_{th} + \sqrt{\frac{i_{I2}}{\beta}} = v_D = \sqrt{\frac{i_{I2}}{\beta}} - \sqrt{\frac{i_{I1}}{\beta}}$$

$$= \beta_n (v_{GS} - V_{th})^2 \quad v_{GS1} = V_{th} + \sqrt{\frac{i_{I1}}{\beta}}$$

Answer: $v_D^2 = \frac{i_{I2}}{\beta} + \frac{i_{I1}}{\beta} - 2 \frac{i_{I1}}{\beta} \sqrt{\frac{i_{I2}}{\beta}} \Rightarrow \beta v_D^2 = I_T - 2 \sqrt{\frac{i_{I1}}{\beta}}$

$$I_T \cdot \beta v_D^2 = 2\sqrt{i_1(I_T - i_1)} \quad \text{square} \quad i_1 I_T - i_1^2 = \frac{1}{4} (I_T - 2v_D^2 \beta)^2$$

$$i_1 = \frac{I_T}{2} \pm \frac{1}{2} \sqrt{I_T^2 - 4 \times \frac{1}{4} (I_T - 2v_D^2 \beta)^2}$$

$$= \frac{I_T}{2} \pm \frac{1}{2} \sqrt{2 I_T v_D^2 \beta - v_D^4 \beta^2} = \frac{I_T}{2} \pm \frac{v_D}{2} \sqrt{I_T \beta} \sqrt{1 - \left(\frac{v_D \beta}{2 I_T}\right)^2}$$

$$i_1 = \frac{I_T}{2} - \frac{v_D}{2} \sqrt{I_T \beta} \sqrt{1 - \left(\frac{v_D \beta}{2 I_T}\right)^2}$$

$$i_2 = \frac{I_T}{2} + \frac{v_D}{2} \sqrt{I_T \beta} \sqrt{1 - \left(\frac{v_D \beta}{2 I_T}\right)^2}$$

not given $i_2 = I_T$
now