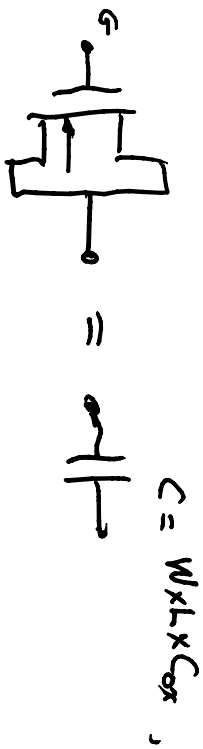


03/09/11
EE303

P. 704, Fig 9.5(a) & P. 706 Table 9.1
 & P. 325 & pp(5.107) (5.110, 5.111)
 = 4 terminal MOS small signal equivalent

P. 1218, Fig. 15.12 = SRAM
 from inverter, P. 1205, Fig. 15.1




$C = W \times L \times C_{ox}$


$C_{ox} = \frac{\epsilon_{SiO_2}}{t_{ox}}$


thickness of oxide
 t_{ox}

Ring of 2 inverters

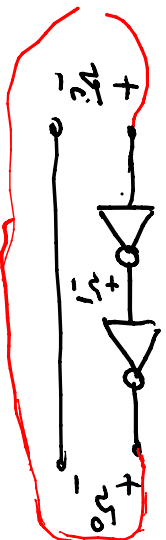


feedback


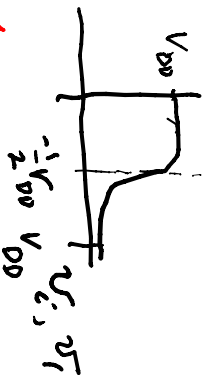


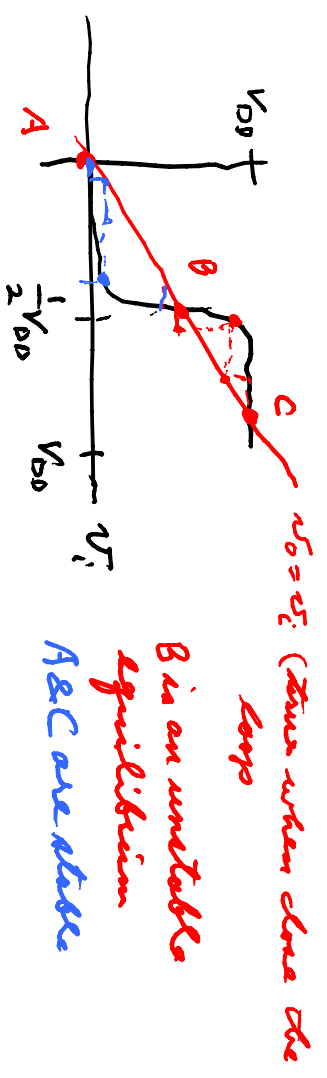

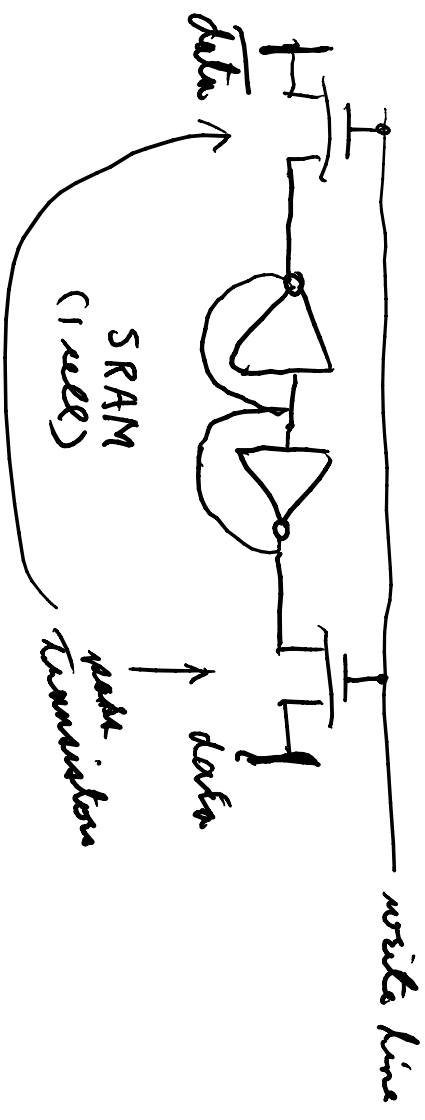gives the SRAM = static random access memory
 v. 1.2.18 $\Rightarrow V_1$ is complement of $V_0 = V_1$



P.1357, fig. 17.19 = Schmitt trigger

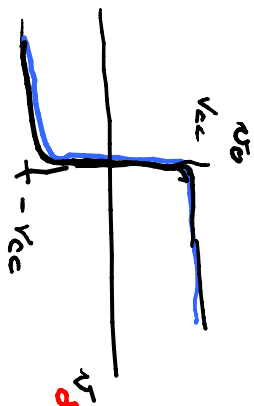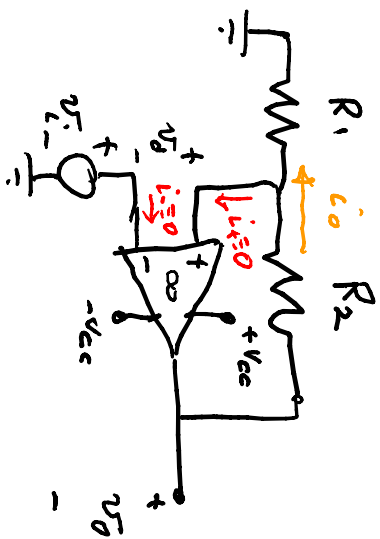

(unlike 4558 op amp)
 ≈ 1458

$$v_O = R_2 i_O + R_1 i_O = R_2 i_O + (v_D + v_I)$$



$$\Rightarrow \text{eliminate } i_O \Rightarrow i_O = \frac{v_O}{R_1 + R_2} \Rightarrow v_O = R_2 \left(\frac{v_O}{R_1 + R_2} \right) + v_D + v_I$$

$$\Rightarrow \left(1 - \frac{R_2}{R_1 + R_2} \right) v_O = v_D + v_I$$

$$a = \frac{R_2}{R_1}$$

$$2 \left(\frac{1}{1 + R_2/R_1} \right) v_O = v_D + v_I$$
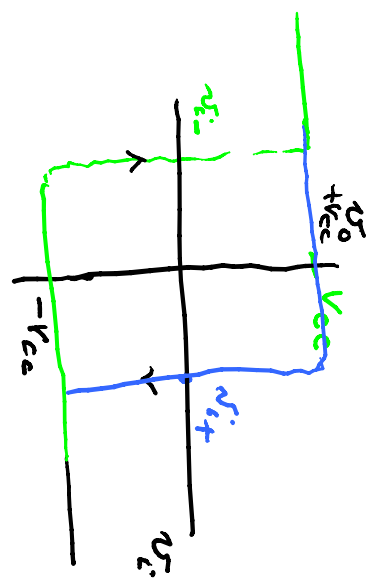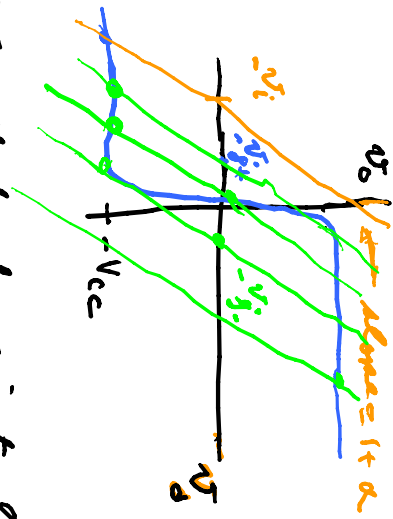
$$\Rightarrow v_O = (1+a)v_D + (1+a)v_I$$



Q_o get knee points occur when the line just hits V_{cc}

$$v_o = V_{cc} = (1+a)|v_i| + (1+a)v_i \Rightarrow$$

$v_i = 0$ v_i for jump down

$$\Rightarrow |v_i| = \frac{V_{cc}}{1+R_2/R_1} = -\frac{V_{cc}}{1+R_2/R_1}$$

jump down jump up


$$\text{hysteresis width} = v_i - (-v_i) = \frac{2V_{cc}}{1+R_2/R_1}$$

jump up jump down


gives design for hysteresis

Return to substrate as input

see p. 754

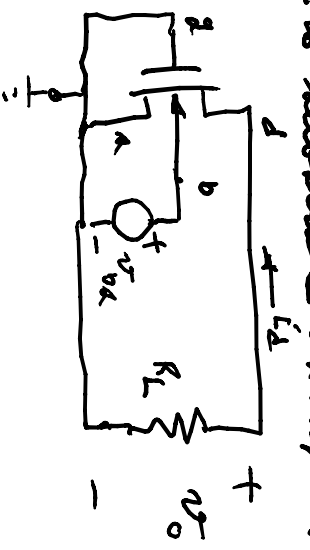
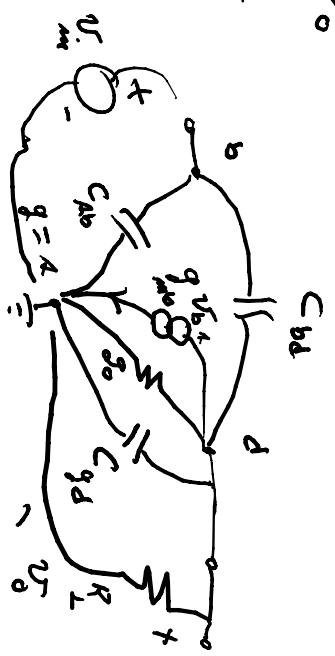
$$g_{mns} = \frac{\partial i_D}{\partial v_{gs}}$$



$$v_{th} = V_{T0} + \gamma \left(\sqrt{2\phi_s + V_{SB}} - \sqrt{2\phi_s} \right) \quad \text{eq. (5.107)}$$

$$i_D = \frac{K_P W}{2 L} \left(v_{GS} - v_{th} \right)^2 (1 + \lambda v_{DS})$$