
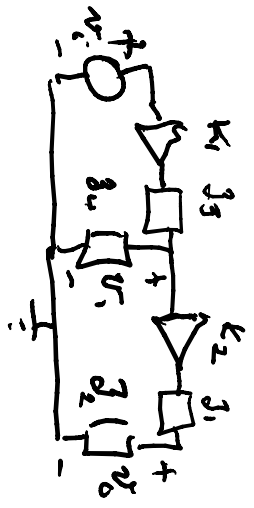


EE 303
05/09/11
updated

Note Title

5/9/2011

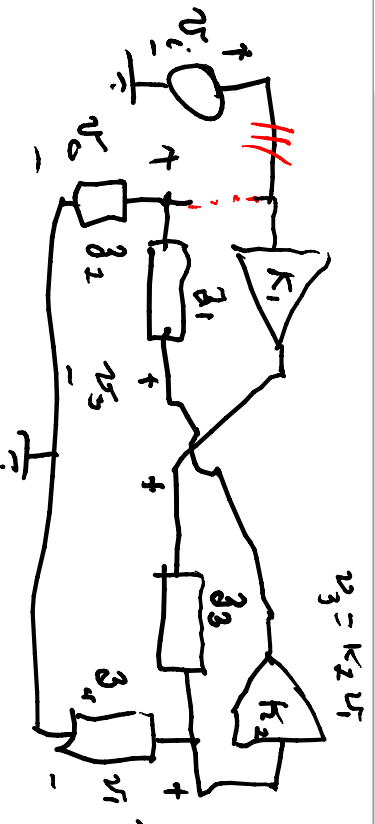

$$T(s) = \frac{V_o}{V_i} \Rightarrow V_o(s) = \frac{g_2}{g_1 + g_2} \cdot K_2 \cdot v_1$$

$$v_1 = \frac{g_4}{g_3 + g_4}, K_1 \cdot v_i \Rightarrow V_o = \frac{1}{1 + \frac{g_1}{g_2}} \cdot K_2 \cdot \frac{1}{1 + \frac{g_3}{g_4}} \cdot K_1 \cdot v_i$$

$$T(s) = \frac{K_1 K_2}{(1 + \frac{g_1}{g_2})(1 + \frac{g_3}{g_4})} = \frac{V_o(s)}{V_i} ; \text{ close the feedback loop}$$

$$V_o = \frac{K_1 K_2}{(1 + \frac{g_1}{g_2})(1 + \frac{g_3}{g_4})} \cdot v_i \Rightarrow (1 - \frac{K_1 K_2}{(1 + \frac{g_1}{g_2})(1 + \frac{g_3}{g_4})}) \cdot v_o = 0$$

for oscillations $\omega \neq 0$

$$P(s) = \left(1 + \frac{g_1}{s_2}\right) \left(1 + \frac{g_2}{s_1}\right) - k_1 k_2 = 0$$

\therefore Let $s = j\omega$ & the s den of $P(s) = 0$ ————— ω -axis



need an s in denominator of $P(s)$
 Let $\frac{g_1}{s_2} = \frac{G_1}{sC}$, $\frac{g_2}{s_1} = \frac{R_2 L}{R_2}$ (assume $s_1 = R_1, s_2 = R_2 L$)

$$\left(1 + \frac{G_1}{sC}\right) \left(1 + \frac{R_2 L}{R_2}\right) - k_1 k_2 = \frac{(sC + G_1)(R_2 + RL) - k_1 k_2 R_2 C}{R_2 C} = 0$$


$$sC R_2 + G_1 R_2 + R_2 L - k_1 k_2 R_2 C = 0 \quad s = j\omega_0$$

$$sC R_2 + (C R_2 + G_1 L - k_1 k_2 R_2 C) + G_1 R_2 = 0$$

$s = j\omega_0 \Rightarrow -\omega_0^2 LC + G_1 R_2 = 0$
 $j\omega_0 (C R_2 + G_1 L - k_1 k_2 R_2 C) = 0$ for $\omega_0 \neq 0$

$$K_1 K_2 = \frac{C R_2 + G_1 L}{R_2 C} ; \quad \omega_0 = \pm \sqrt{\frac{G_1 R_2}{LC}}$$

Now use OTA's

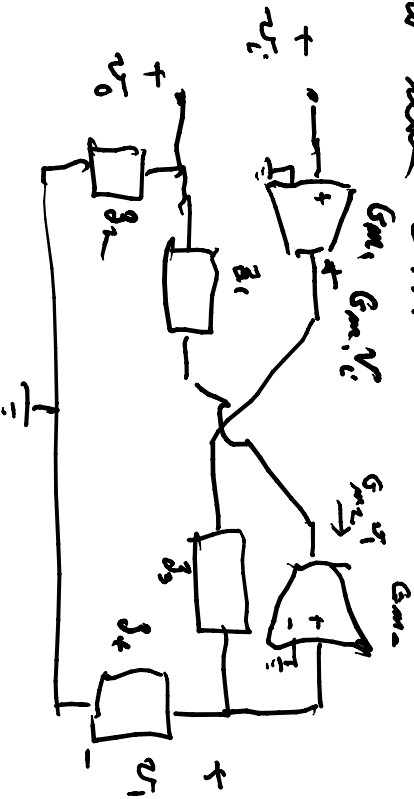

$$v_o = -g_2 G_{m2} v_i, \quad v_i = G_{m1} v_o (-g_4)$$


$$v_o = (-g_2 G_{m2}) (-g_4 G_{m1}) v_o = g_2 g_4 G_{m1} G_{m2} v_o$$

operating condition when close the loop



$$1 - g_2 g_4 G_{m1} G_{m2} = 0$$

can choose g_2 (a) & g_4 (a) to make an oscillator


Current mirror output

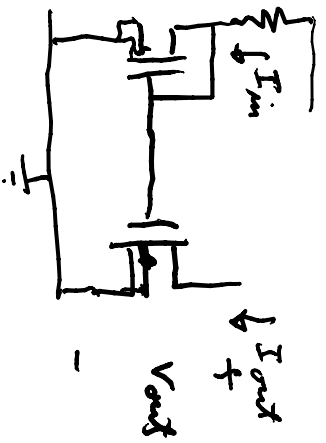

to raise output slope can cascade

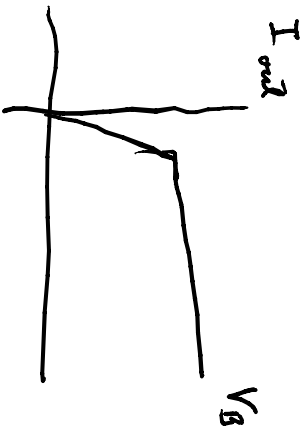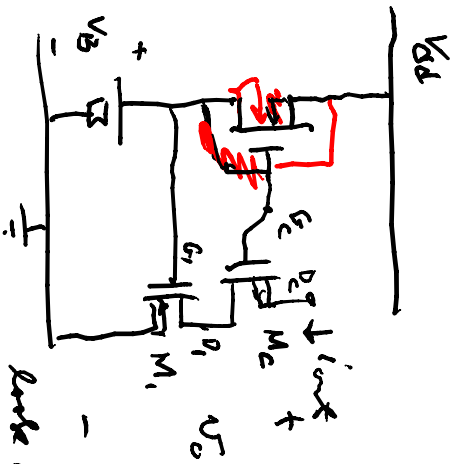

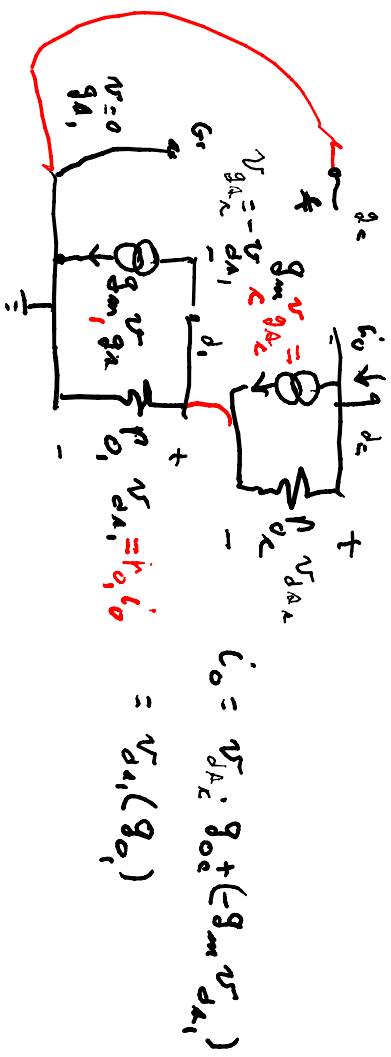look at small signal behavior for
AC V_{out}



$$v_o = v_{rc} + v_{d1} \Rightarrow v_{rc} = v_o - v_{d1}$$

$$i_o = (v_o - v_{d1}) g_{o1} + (-g_m v_{d1}) = v_o g_{o1} - (g_{o1} + g_m) g_{o1} v_o$$

$$= v_o g_{o1} - (g_{o1} + g_m) v_{d1} = g_{o1} v_o - (g_{o1} + g_m) r_{o1} i_o$$

$$i_o = g_{o1} v_o - (g_{o1} + g_m) r_{o1} i_o \Rightarrow i_o = \left(\frac{1}{1 + (g_{o1} + g_m) r_{o1}} \right) g_{o1} v_o$$

$$\Rightarrow i_o = \frac{1}{r_{o1} \left(1 + \frac{g_m r_{o1}}{g_{o1}} + \frac{g_{o1} r_{o1}}{g_{o1}} \right)} \cdot v_o$$

\Rightarrow Lower change in output current

$v_{d1} \Rightarrow v_{o1} + \frac{v_{o1}}{g_{o1}} (g_m r_{o1} + g_{o1}) \Rightarrow$ increased output resistance

\Rightarrow improved output current around Q point current

