

Some problems which may be of interest from Sedra/Smith 6<sup>th</sup> Edition.

1. Diode: P4.46 of page 222
2. MOS: P5.8 & P5.9 of page 329
3. MOS P5.18 & P5.24 of page 331
4. MOS differential pair: P5.61 of page 338
5. 2-port gain: P5.83 of page 342
6. MOS bias: D5.104 of page 344
7. 2-port high frequency gain: P9.34 of page 789
8. BJT beta & alpha: P6.8 of page 467
9. BJT ISE: P6.13 of page 467
10. 2-port  $R_{in}$ : P6.112 of page 4.81
11. BJT Current Mirror: P9.67 of page 793
12. MOS Current Mirror: P7.50 of page 577