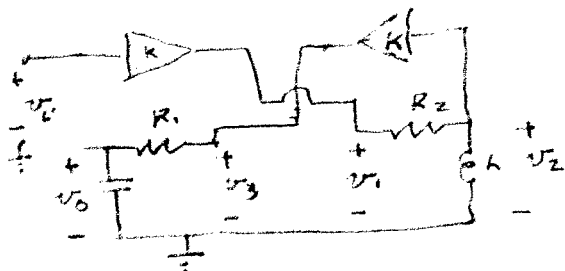


#1



$$v_1 = K v_2, \quad v_2 = \frac{\alpha L}{\alpha L + R_2} v_1 = \frac{\alpha L K}{\alpha L + R_2} v_2$$

$$v_3 = K v_2 = \frac{\alpha L K^2}{\alpha L + R_2} v_2, \quad v_0 = \frac{1/\alpha C}{1/\alpha C + R_1} v_3 = \frac{1}{\alpha R_1 C + 1} \cdot \frac{\alpha L K^2}{\alpha L + R_2} v_2$$

a) $\therefore T(\alpha) = \frac{\alpha L K^2}{(\alpha R_1 C + 1)(\alpha L + R_2)} = \frac{(K^2/R_1 C) \cdot \alpha}{(\alpha + C/R_1 C)(\alpha + (R_2/L))} = \frac{v_0}{v_i}$ poles: $\alpha = -1/R_1 C, -R_2/L$ zeros: $\alpha = 0, \infty$

For $v_0 = v_i$; $T(\alpha) = 1 \Rightarrow v_0 = T(\alpha) v_0 \Rightarrow (1 - \frac{\alpha L K^2}{(\alpha R_1 C + 1)(\alpha L + R_2)}) v_0 = 0$


$$\Rightarrow (\alpha R_1 C + 1)(\alpha L + R_2) - \alpha L K^2 = 0 \quad (\text{or } \alpha = \infty)$$

$$\equiv \alpha^2 R_1 C L + (R_1 C R_2 + L - L K^2) \alpha + R_2 = 0$$

For an oscillator $\alpha = j\omega_0 \Rightarrow -\omega_0^2 R_1 C L + R_2 = 0$ & $j\omega_0 (R_1 C R_2 + L - L K^2) = 0$

$$\Rightarrow \omega_0 = \pm \sqrt{\frac{R_2}{R_1 C L}}, \quad K^2 = 1 + \frac{R_1 R_2 C}{L} \equiv K = \pm \sqrt{1 + R_1 R_2 \frac{C}{L}}$$

#2

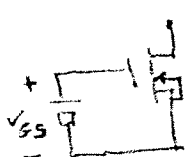

as a current source the transistor should be in saturation

$$\Rightarrow I_D = \beta (V_{GS} - V_{TO})^2 (1 + \lambda V_{DS}); \quad \beta = \frac{K_P W}{2 L}; \quad \text{as } \beta, I_D, \lambda, V_{DS} \text{ all known, find } V_{GS}$$

$$\Rightarrow V_{GS} = V_{TO} + \sqrt{\frac{I_D}{\beta (1 + \lambda V_{DS})}}$$

for 4007: $\beta = \frac{20.54 \times 10^{-6}}{2} \times \frac{144 \times 10^{-6}}{8 \times 10^{-6}} = 184.86 \times 10^{-6}$; $V_{TO} = 1.3$
 $\lambda = 15 \times 10^{-3}$; $V_{DS} = 5$

$$\therefore V_{GS} = 1.3 + \sqrt{\frac{2 \times 10^{-3}}{184.86 \times 10^{-6}}} \quad \text{if } \lambda = 0 = 4.589 = 1.3 + 3.289$$

$$V_{GS\lambda} = 1.3 + \sqrt{\frac{2 \times 10^{-3}}{184.86 \times 10^{-6} (1 + 15 \times 10^{-3})}} \quad \text{if } \lambda = 15 \times 10^{-3} = 4.472 = 1.3 + 3.172$$

so if λ is ignored V_{GS} will be slightly too big by 0.117V out of 4.5V

Also $V_{GS} - V_{TO} < 3.3 < V_{DS} = 5 \Rightarrow$ saturation, as a check