

Solution EE303 SIS Midterm Makeups

RWN
04/10/11

#1. a) From class notes, $-\infty < V_i < \infty$

$$I_o = \alpha I_T \tanh\left(\frac{V_i}{2V_T}\right) \Rightarrow G_m = \left. \frac{dI_o}{dV_i} \right|_{V_i=0} = \frac{\alpha I_T}{2V_T} \left(1 - \tanh\left(\frac{V_i}{2V_T}\right)\right) \Big|_{V_i=0}$$

$$= \frac{\alpha I_T}{2V_T} = \frac{\beta}{1+\beta} \frac{I_T}{2V_T}$$

$$\therefore G_m \Big|_{\substack{\text{BJT} \\ \text{OTA}}} = \frac{\beta}{1+\beta} \frac{I_T}{2V_T} = \frac{150}{151} \cdot \frac{5 \times 10^{-3}}{2 \times 26 \times 10^{-3}} = 0.0955 \text{ V} = 95 \text{ milli Mho}$$

b) From class notes, $-V_S < V_i < V_S = \sqrt{\frac{I_T}{2KP(W/L)}} \left[\text{which covers the bias point of } V_i = 0 \right]$

for which

$$I_o = G_o V_i \sqrt{1 - \frac{1}{2} (V_i/V_S)^2}; \quad G_o = \sqrt{2 I_T \frac{KP(W/L)}{2}}$$

$$\Rightarrow G_m = \left. \frac{dI_o}{dV_i} \right|_{V_i=0} = G_o \left(\sqrt{1 - \frac{1}{2} (V_i/V_S)^2} + V_i \cdot \frac{1}{2} \frac{1}{\sqrt{1 - \frac{1}{2} (V_i/V_S)^2}} \left(-\frac{1}{2} \times 2 \frac{V_i}{V_S} \right) \right) \Big|_{V_i=0}$$

$$= G_o$$

From the 4007 differential pair

$$b_1) \text{ NMOS, } G_m \Big|_{\substack{\text{OTA} \\ \text{NMOS}}} = \sqrt{\frac{2 \times 5 \times 10^{-3} \times 20.54 \times 10^{-6} \times \left(\frac{144 \times 10^{-6}}{8 \times 10^{-6}}\right)}{2}} = \sqrt{1.8486 \times 10^{-6}}$$

$$= 1.360 \times 10^{-3} \text{ V} = 1.36 \text{ milli Mho}$$

$$b_2) \text{ PMOS, } G_m \Big|_{\substack{\text{OTA} \\ \text{PMOS}}} = \sqrt{\frac{2 \times 5 \times 10^{-3} \times 10.32 \times 10^{-6} \times \left(\frac{328 \times 10^{-6}}{8 \times 10^{-6}}\right)}{2}} = \sqrt{2.1156 \times 10^{-6}}$$

$$= 1.455 \times 10^{-3} \text{ V} = 1.46 \text{ milli Mho}$$

#2. $G_m = \text{slope of } I_o \text{ versus } V_i \text{ in } -V_S \leq V_i \leq V_S$

$$= I_T/V_S$$

#9. a) (a) $v_e = v_{in} - v_a$, $i_o = C \frac{dv_e}{dt} = C \frac{d[v_{in} - v_a]}{dt} = -G_m v_a$

$$\Rightarrow C \frac{dv_a}{dt} + G_m v_a = C \frac{dv_{in}}{dt}$$

(b) $v_e = v_{in} - v_b$, $i_o = C \frac{dv_e}{dt} = C \frac{d[v_{in} - v_b]}{dt} = -G_m v_b$

$$\Rightarrow C \frac{dv_b}{dt} - G_m v_b = C \frac{dv_{in}}{dt}$$

b) $\frac{d}{dt} \Rightarrow s$, $\mathcal{L}[v_a] = V_a$, $\mathcal{L}[v_b] = V_b$, $v_{in} = s(t)$, $\mathcal{L}[v_{in}] = 1$

(a) $(sC + G_m) V_a = sC V_{in} = sC$

$$\Rightarrow V_a(s) = \frac{sC}{sC + G_m} = \frac{s}{s + (G_m/C)} = 1 + \frac{-(G_m/C)}{s + (G_m/C)}$$

$$\Rightarrow v_a|_{(t)} = s(t) - \frac{G_m}{C} e^{-(G_m/C)t} \mathcal{L}^{-1}\{1\}$$

$v_{in} = s$

(b) $(sC - G_m) V_b = sC$

$$\Rightarrow V_b(s) = \frac{sC}{sC - G_m} = \frac{s}{s - (G_m/C)} = 1 + \frac{+(G_m/C)}{s - (G_m/C)}$$

$$\Rightarrow v_b|_{(t)} = s(t) + \frac{G_m}{C} e^{+(G_m/C)t} \mathcal{L}^{-1}\{1\}$$

$v_{in} = s$

c) In (a) the OTA gives a positive resistor while in (b) it gives a negative one; for (a) the response $\rightarrow 0$ as $t \rightarrow \infty$ while for (b) the response $\rightarrow \infty$ as $t \rightarrow \infty$, an unstable circuit.

#4 a) $V_{GS} = \frac{R_{b2}}{R_{b1} + R_{b2}} \cdot V_{dd} = \frac{1}{2} \cdot 6 = 3V = \underline{V_{GS}}$

$$I_D = \frac{k_p W}{2 L} (V_{GS} - V_{T0n})^2 (1 + \lambda V_{DS}) \quad \text{if in saturation}$$

$$= \frac{20.54 \times 10^{-6}}{2} \cdot \frac{144}{8} (3 - 1.3)^2 (1 + 0.015 V_{DS})$$

$$= 5.342 \times 10^{-4} (1 + 0.015 V_{DS})$$

and a second equation in the two unknowns, I_D & V_{DS}
 $V_{DD} = R_L I_D + V_{DS}$

$$\Rightarrow 6 = 0.5342 (1 + 0.015 V_{DS}) + V_{DS}$$

$$\Rightarrow 6 - 0.5342 = (1 + 0.5342 \times 0.015) V_{DS} \Rightarrow 5.4658 = (1.008) V_{DS}$$

$$\Rightarrow \underline{V_{DS} = 5.42 V} \quad \Rightarrow V_{DS} = 5.42 > 3 - 1.3 = 2.7 = V_{GS} - V_{T0n} \Rightarrow \text{saturation}$$

$$\Rightarrow I_D = 5.342 \times 10^{-4} (1 + 0.015 \times 5.42) = 5.776 \times 10^{-4}$$

$$\Rightarrow \underline{I_D = 0.578 mA}$$

b) $g_m = \frac{\partial I_D}{\partial V_{GS}} \Big|_Q = \frac{2 I_D}{(V_{GS} - V_{T0n})} = 2 \frac{0.578 \times 10^{-3}}{(1.7)} = 0.68 mV$

$$g_o = \frac{\partial I_D}{\partial V_{DS}} \Big|_Q = \frac{2 I_D}{1 + \lambda V_{DS}} = \frac{0.015 \times 0.578 \times 10^{-3}}{1 + 0.015 \times 5.42} = 8.02 \times 10^{-6} = 8.02 \mu V$$

$$A_v = -g_m R_L = -0.68 \times 10^{-3} \times 1 \times 10^3 = -0.68$$